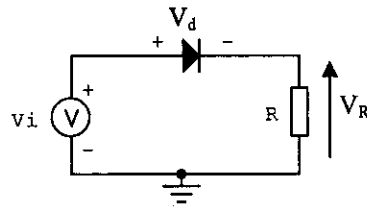


**UNIVERSITY OF SWAZILAND****MAIN EXAMINATION 2004/5****FACULTY OF SCIENCE****DEPARTMENT OF ELECTRONIC ENGINEERING****TITLE OF PAPER: SIGNALS I****COURSE NUMBER: E342****TIME ALLOWED: THREE HOURS****INSTRUCTIONS:**

1. Answer any FOUR (4) of the following five questions.
2. Each question carries 25 marks.

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION HAS  
BEEN GIVEN BY THE INVIGILATOR**

**THIS PAPER CONTAINS SIX (6) PAGES INCLUDING THIS PAGE**


**QUESTION 1****Fig. 1**

In Fig 1  $V_i = 2 \sin(\pi t)$

Sketch 2 periods of the following:

- |            |  |           |
|------------|--|-----------|
| <b>(a)</b> | (i) Input voltage $V_i$                      | [4 marks] |
|            | (ii) Voltage across diode, ( $V_a$ )         | [4 marks] |
|            | (iii) Voltage across resistance $R$ , $V_R$  | [4 marks] |
|            | (iv) Classify the type of circuit in Fig. 1. | [3 marks] |
| <b>(b)</b> | (i) Determine the average value of $V_R$     | [5 marks] |
|            | (ii) Determine the RMS value for $V_R$ .     | [5 marks] |

## QUESTION 2

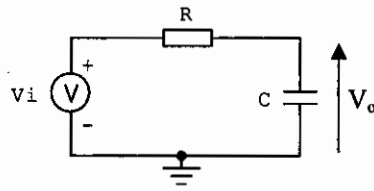

**Fig. 2**

Consider the circuit in Fig. 2.

- (a) Determine its transfer function  $\frac{v_o}{v_i} = G(j\omega)$  [5 marks]
- (b) Determine and sketch the phase and amplitude characteristics of the circuit of Fig. 2. [10 marks]
- (c) What type of filter does the figure represent? Elaborate on your response. [5 marks]
- (d) Of what significance is the resistor and capacitor in the circuit? And what are they usually known as? [5 marks]

### QUESTION 3

Given that

$$G(j\omega) = \frac{1}{1+j\omega RC} \quad (\text{Eq. 1})$$

and  $RC = 0.3 \text{ sec}$

- (a) Compute the magnitude and phase of  $G(j\omega)$  at  $\omega = 1$ . [6 marks]
- (b) The square wave shown in Fig. 3 is applied to the system whose transfer function is given in Eq. 1. The square wave has a period  $2\pi$  and amplitude unity.

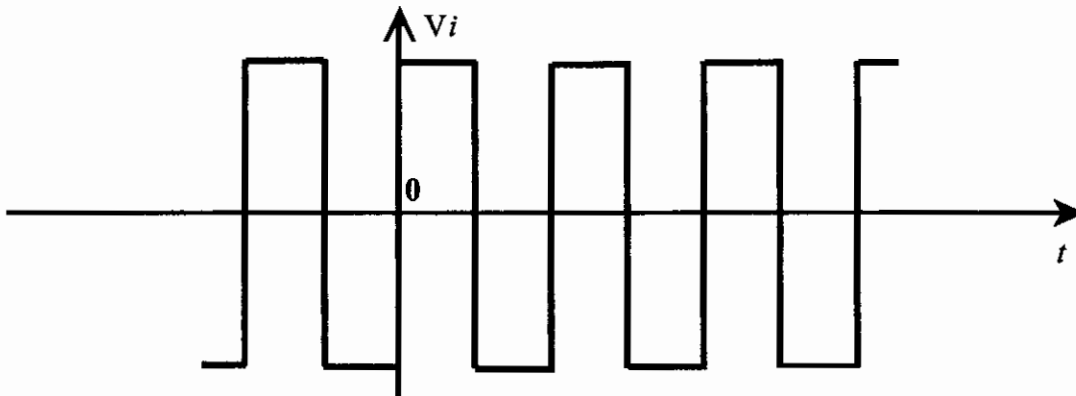


Fig. 3: Square wave with fundamental angular frequency 1 and amplitude 1.

- (i) State whether the square wave is odd or even and how this will assist in determining the Fourier coefficients. [3 marks]
- (ii) Sketch the output waveform after passing through the system described by Eq.1. [3 marks]
- (iii) Obtain an expression for the Fourier Coefficients of the square wave. [6 marks]
- (iv) Compute the **first three** Fourier coefficients. [3 marks]
- (v) Evaluate the gain and phase changes to these first three Fourier components as they pass through the system in Eq.1. [4 marks]

#### **QUESTION 4**

**(a)** Determine whether the following signal processing operations are linear or non-linear.

(i)  $y(t) = 2x(t) + d \frac{x(t)}{dt}$  [2 marks]

(ii)  $y(t) = 3 + \int 5x(t) dt$  [2 marks]

(iii)  $y(t) = 4x^2(t)$  [2 marks]

**(b)** Sketch the graphs of the following signals and determine the magnitude and period of each signal.

(i)  $x(t) = 2 \cos 2\pi t + 3 \cos 4\pi t$  [3 marks]

(ii)  $x(t) = |\sin 5\pi t|$  [3 marks]


**(c)** (i) Describe energy and power signals and give an example of each. [6 marks]

(ii) Find the average power developed across a  $1 \Omega$  resistor by the voltage signal:

$$v(t) = 2 + \cos t - \frac{2}{3} \sin 2t + \frac{1}{2} \cos 3t$$

(Hint: use Parseval's theorem)

[7 marks]

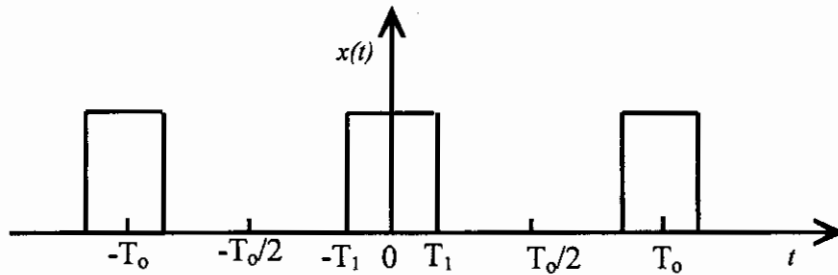**QUESTION 5****Fig. 4**

A periodic square wave shown in Fig. 4 above is defined as:

$$x(t) = \begin{cases} 1, & |t| < T_1 \\ 0, & T_1 < |t| < \frac{T_0}{2} \end{cases}$$

Determine the exponential Fourier series expansion of the wave.

[25 marks]