

SS

UNIVERSITY OF SWAZILAND
FACULTY OF SCIENCE
DEPARTMENT OF ELECTRONIC ENGINEERING

MAIN EXAMINATION 2005

TITLE OF PAPER: **ELECTRONICS I** (Paper I)

COURSE NUMBER: **E360**

TIME ALLOWED: THREE HOURS

INSTRUCTIONS: ANSWER **QUESTION 1** AND ANY OTHER **THREE QUESTIONS**

QUESTION 1 CARRIES 40 MARKS

QUESTION 2, 3, 4, AND 5 CARRY 20 MARKS EACH.

MARKS FOR DIFFERENT SECTIONS ARE SHOWN IN THE RIGHT-HAND MARGIN

THIS PAPER HAS 6 PAGES, INCLUDING THIS PAGE

DO NOT OPEN THE PAPER UNTIL PERMISSION HAS BEEN GIVEN BY THE
INVIGILATOR

Question 1

- a). Figure 1.A shows an electronic circuit used in a ship steering system. Determine the expression for the voltage V_m supplied to the motor in terms of the command voltage V_c and the feedback voltage V_f . (7 marks)

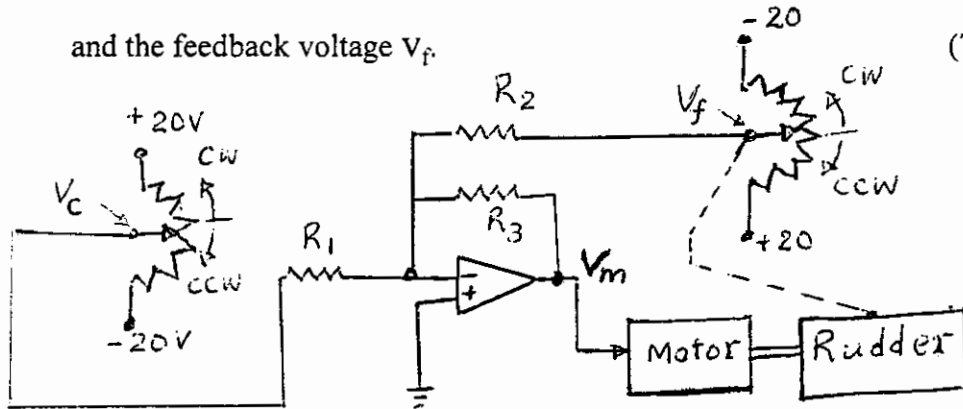


Figure 1 A

- b) How is stabilization achieved in a self-biasing circuit? (4 marks)
- c) In Figure 1.C, find the percentage change in the collector current if the current gain β is decreased by 50%. (10 marks)
- d) In the circuit shown in Figure 1.D, Q1 and Q2 are identical transistors having $r_{\pi} = 2k\Omega$ and $g_m = 0.1 \Omega^{-1}$
- Draw the equivalent circuit diagram (4 marks)
 - Find the input and output impedances, and the transfer ratio (12 marks)
 - State which type of basic amplifier this circuit approximate and draw it. (3 marks)

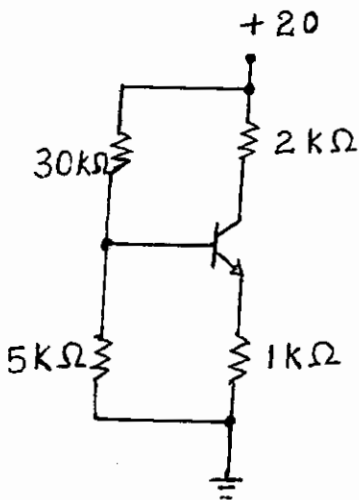


Figure 1 C

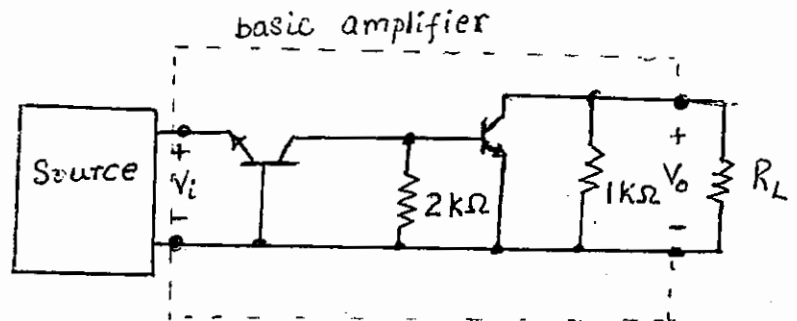


Figure 1 D.

Question 2

A fixed bias, common emitter, single stage amplifier is to have the following requirements:

1. voltage gain $A_v = -60$
2. Input impedance $R_i = 1.9937\Omega$ (as seen by the source)
3. Output impedance $R_o = 12k\Omega$ (as seen by the load resistor)
4. A 1 K resistor and a bypass capacitor are to be connected to the emitter of the transistor
5. The transistor when biased at room temperature have $r_\pi = 2k\Omega$, $g_m = 2k\Omega$ and a thermal voltage of 25 millivolts.
6. A capacitor C_1 couples the amplifier to the source and a capacitor C_2 couples the amplifier to the load resistor R_L .

If this amplifier is to be supplied by a 9 battery then

- (a) draw the circuit diagram and the equivalent circuit at midband . (5 marks)
- (b) obtain the following resistor values: base resistor R_B , collector resistor R_C and load resistor R_L . (6 marks)
- (c) obtain the Q-point voltages and currents (I_{CQ} , I_{BEQ} , V_{BEQ} , and V_{CEQ}) (9 marks)

Question 3

For the circuit shown in Figure 3, determine the open-loop gain A_{OL} , feedback transfer ratio β , return ratio T , and closed-loop gain A_F . (20 marks)

The BJT parameters are $g_m = 0.02$ and $r_\pi = 10k$

The FET parameters are $\mu = 40$ and $r_{ds} = 10k$

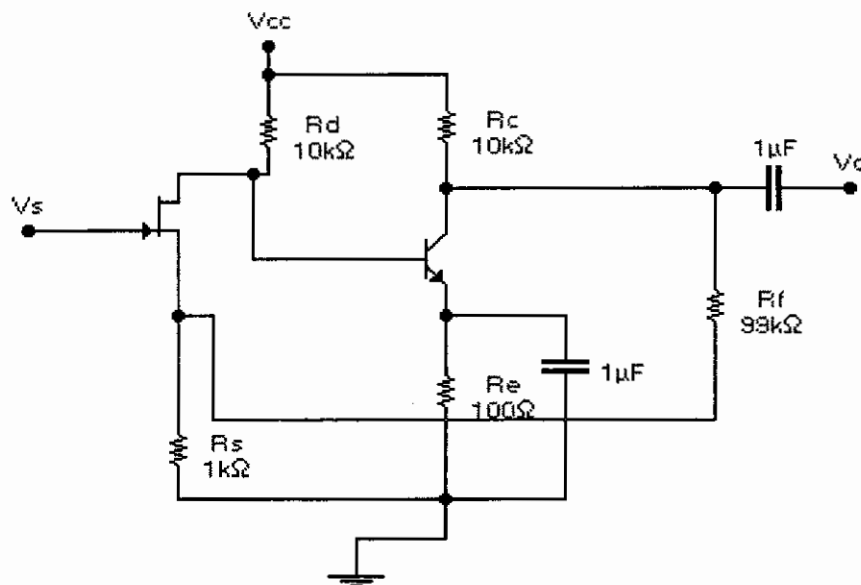


Figure 3

Question 4

a) State two conditions which must be satisfied by a circuit to sustain oscillation (4 marks)

b) A phase shift oscillator shown in Figure 4 has a return ratio given by

$$T(j\omega_n) = \frac{jA_v\omega_n^3}{1 - 6\omega_n^2 + j\omega_n(5 - \omega_n^2)}$$

Where $\omega_n = \omega RC$.

The FET has $g_m = 0.04\Omega^{-1}$ and $r_{ds} = 1k\Omega$.

Obtain

- (i) the frequency of oscillation in Hz [4 marks]
- (ii) the gain of the JFET [7 marks]
- (iii) the return ratio at the frequency of oscillation [5 marks]

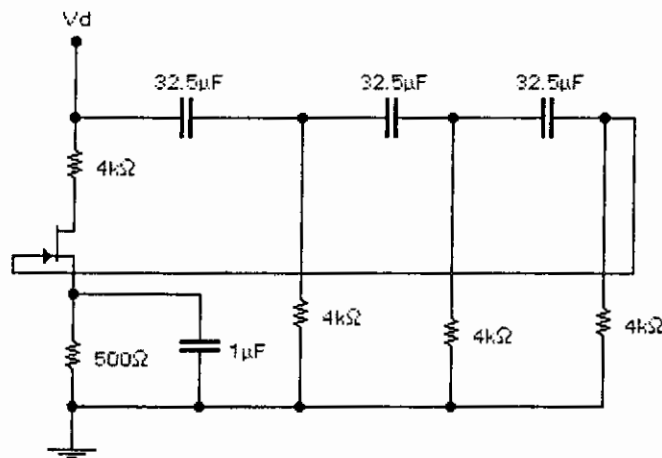


Figure 4

Question 5

For a simple transformer coupled class A power amplifier shown in Figure 5,
 $V_i = 0.02 \sin(2000\pi t)$, $h_{fe} = \beta = 100$, $h_{ie} = 100 \Omega$, and $V_{BE} = 0.6 \text{ V}$.

Obtain

- the power supplied by 12 volts dc supply [6 marks]
- the ac output power [10 marks]
- the conversion efficiency [2 marks]
- the power dissipated in the transistor [2 marks]

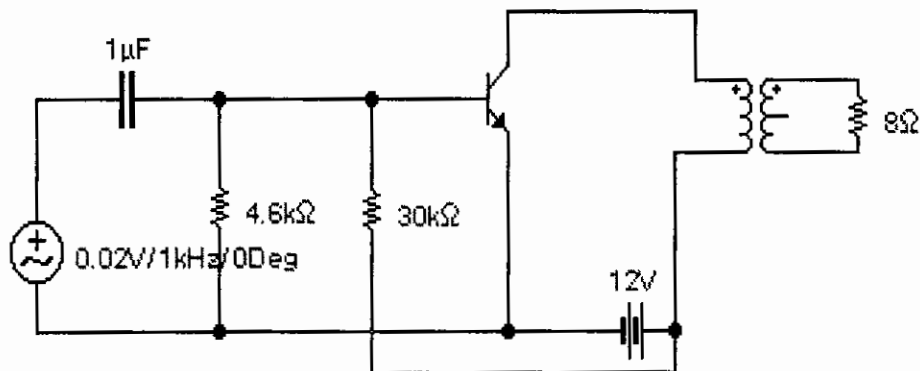


Figure 5