

UNIVERSITY OF SWAZILAND

MAIN EXAMINATION 2005/2006

FACULTY OF SCIENCE

DEPARTMENT OF ELECTRONIC ENGINEERING

TITLE OF PAPER: ELECTRIC CIRCUITS

COURSE CODE: E310

TIME ALLOWED: THREE HOURS

INSTRUCTIONS:


- 1. There are two Sections to this paper. SECTION A has questions 1 to 4 and SECTION B has Questions 5 to 6. Answer FOUR questions including AT LEAST ONE from SECTION B.**
- 2. Questions carry equal marks.**
- 3. Graph paper is provided.**

THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR

THIS PAPER CONTAINS SEVEN (7) PAGES INCLUDING THIS PAGE

SECTION A**QUESTION 1 - D.C. CIRCUITS (25 marks)**

- (a) (i) Suppose that Swaziland Electricity Board supplies a home with a 220-V, 35-A service, find the maximum power available to the home. Do you think the home can safely operate the following loads at the same time: a 5-hp motor, 3000-W dish washer, a 2400-W electric drill and a 1000-W steam iron? Explain. (Note: 1 hp = 746 W). (5 marks)
- (ii) What is the efficiency of a dryer motor that delivers 1 hp when the input current and voltage are 4 A and 220 V, respectively? (3 marks)
- (b) What is the total cost of using the following when a power company charges E0.34 per kilowatt-hour: a 110-W stereo set for 4 h, a 860-W air conditioner for 24 h, a 1800-W cloth dryer for 30 min, a 400-W washing machine for 1 h and a 1200-W dishwasher for 45 min? (5 marks)
- (c) Find V_{ab} with polarity for the circuit of Fig 1.1. Each box can contain a load or a power supply, or a combination of both. (4 marks)

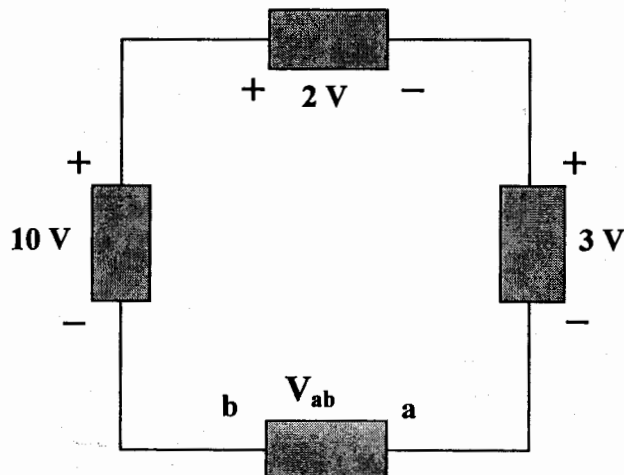**Fig. 1.1**

- (d) (i) Find the internal resistance of a battery that has a no load output of 60 V and supplies a current of 2 A to a load of 28 Ω . (4 marks)
- (ii) Determine the voltage regulation for the battery of problem (i) above. (4 marks)

QUESTION TWO – DC CIRCUITS (25 marks)

(a) For the network in Fig 2.1

- (i) Write the equations to solve for the branch currents. (7 marks)
- (ii) By substitution of Kirchhoff's current law, reduce the set of equations in (i) to three equations. (5 marks)
- (iii) Rewrite the equations in a format that could be solved using third-order determinants. (2 marks)
- (iv) Solve for the branch current I_3 through the resistor R_3 . (4 marks)

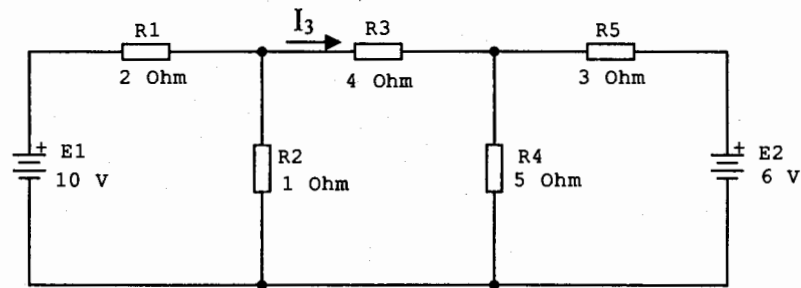


Fig. 2.1

- (b) (i) Convert the voltage sources of Fig 2.2 to current sources. (3 marks)
- (ii) Find the voltage V_{ab} and the polarity of the points a and b . (3 marks)
- (iii) Find the magnitude and direction of the current I through resistor R_3 . (1 mark)

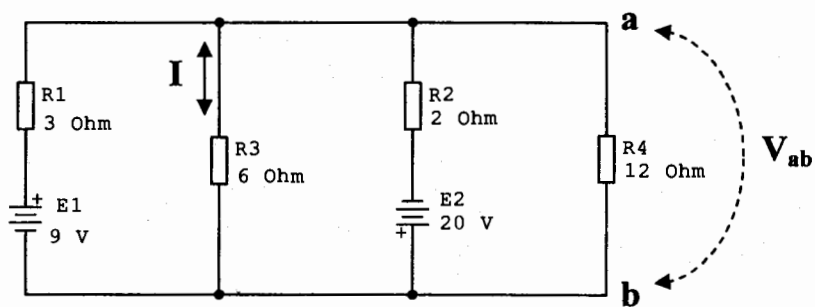
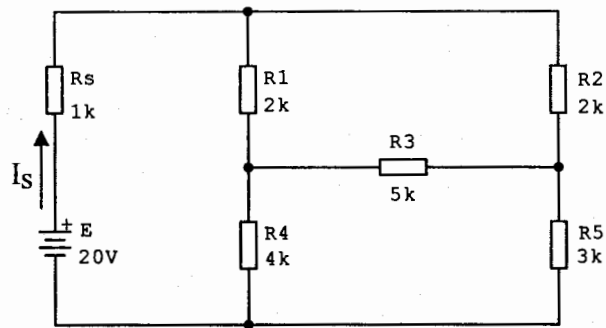



Fig. 2.2

QUESTION THREE - D.C. CIRCUITS (25 marks)

- (a) (i) In Fig 3.1, replace the Π -configuration that is composed of the $4\text{ k}\Omega$, $5\text{ k}\Omega$ and $3\text{ k}\Omega$ resistors with a T-configuration. (7 marks)
- (ii) Solve for the source current, I_S . (3 marks)


**Fig. 3.1**

- (b) For the bridge network of Fig 3.2,
- (i) Using the format approach, write the mesh equations. (6 marks)
- (ii) Determine the current through R_3 . (6 marks)
- (iii) Find out if the bridge (R_1 , R_2 , R_3 and R_4) is balanced or not. (3 marks)

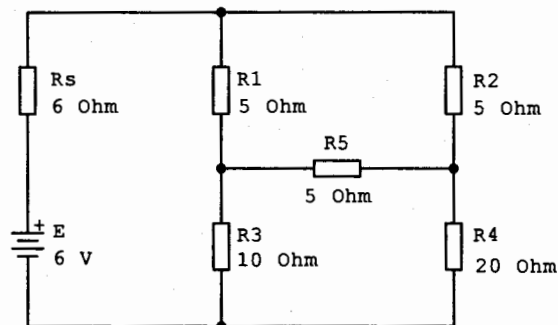
**Fig. 3.2**

QUESTION FOUR - TRANSIENTS (25 marks)

- (a) Refer to the circuit shown in Fig 4.1.
- Write the mathematical expression for $i(t)$ and $v_c(t)$ when the switch is placed in position 1. (2 marks)
 - Write down the mathematical expression for $i(t)$ and $v_c(t)$ when the switch is then placed in position 2, after having been in position 1 for 1 s. (5 marks)
 - Sketch $i(t)$ in parts (i) and (ii) using a single time axis. In your sketch mark horizontal and vertical axis values at all points of interest. (3 marks)
 - Repeat (iii) for $v_c(t)$. (3 marks)

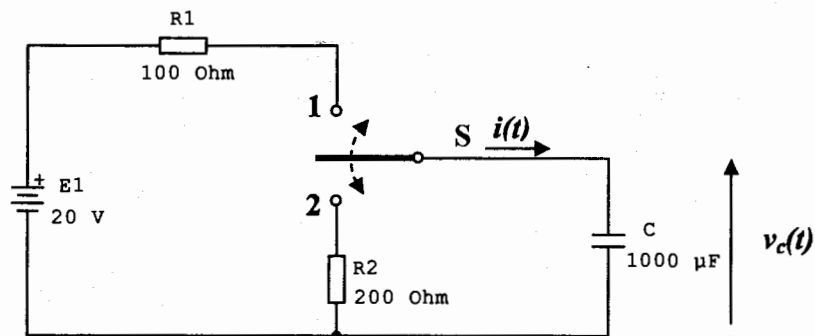**Fig 4.1**

- (b) Consider the circuit diagram shown in Fig 4.2. Switch S is closed at $t = 0$. Assume that all capacitors are initially uncharged.
- Find the initial current through the voltage source and the initial voltage across R_1 , R_2 and R_3 in the circuit. (6 marks)
 - Find the steady-state current through the source and the steady-state voltages across R_1 , R_2 and R_3 . (6 marks)

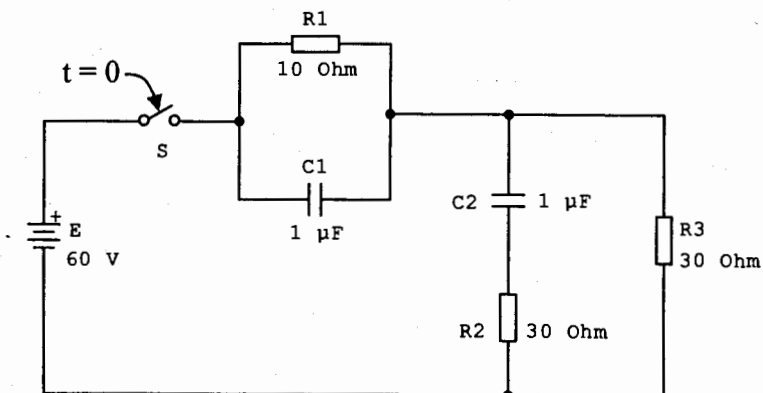**Fig. 4.2**

SECTION B**QUESTION FIVE - AC CIRCUITS (25 marks)**

For the circuit of Fig 5.1, the source voltage is $e(t) = 20\sqrt{2} \sin(377t + 40^\circ)$ volts.

Do the following:

- Determine I , V_R and V_C in phasor form. (14 marks)
- Calculate the total power factor and indicate whether it is leading or lagging. (3 marks)
- Calculate the average power delivered to the circuit. (2 marks)
- Sketch the impedance diagram. (3 marks)
- Sketch the phasor diagram of the voltages E , V_R and V_C , and the current I . (3 marks)

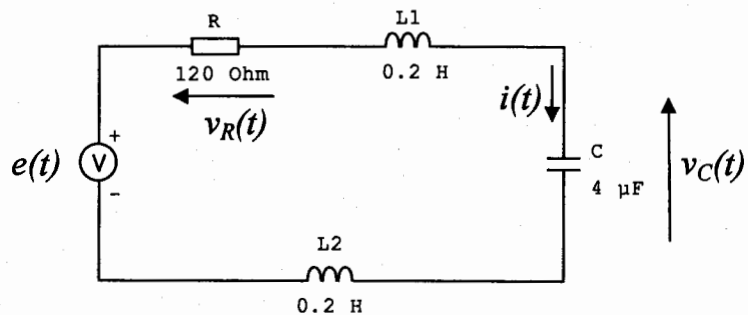


Fig. 5.1

QUESTION SIX - AC CIRCUITS (25 marks)

- (a) Using the general approach to mesh analysis, find the current I_1 in the network shown in Fig. 6.1. (10 marks)

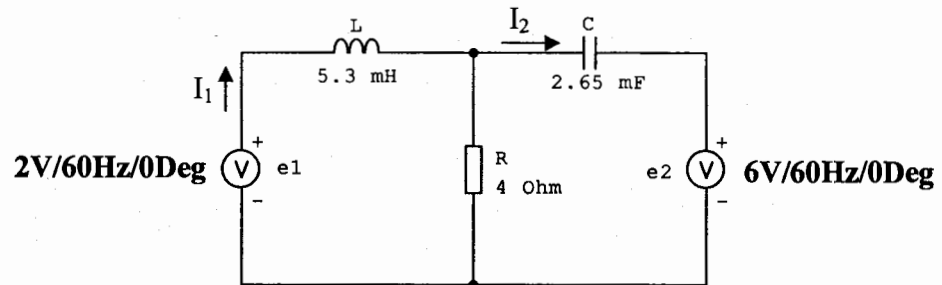


Fig. 6.1

- (b) Determine the nodal voltages for the circuit shown in Fig. 6.2 (15 marks)

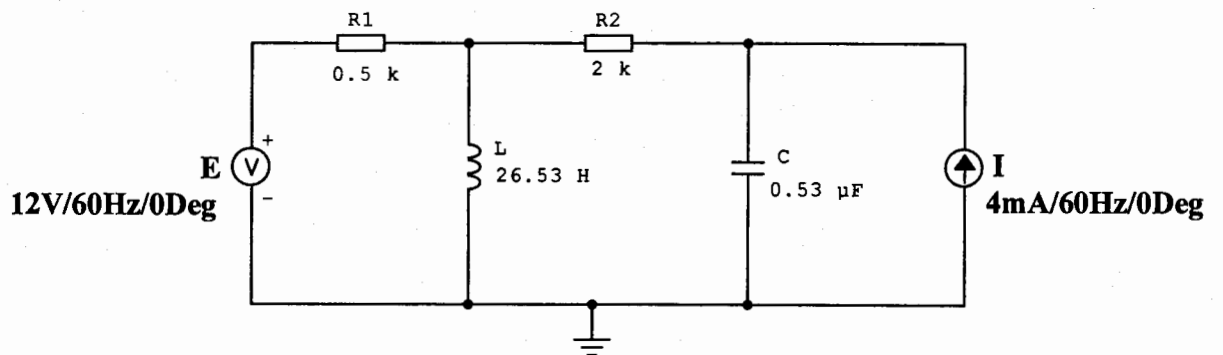


Fig. 6.2

===== END OF EXAMINATION PAPER =====