

**UNIVERSITY OF SWAZILAND**

**MAIN EXAMINATION 2005/2006**

**FACULTY OF SCIENCE**

**DEPARTMENT OF ELECTRONIC ENGINEERING**

**TITLE OF PAPER: ELECTRONICS III—PAPER 1**

**COURSE NUMBER: E510**

**TIME ALLOWED: THREE HOURS**

**INSTRUCTIONS:**

1. Answer any **FOUR (4)** of the following six questions.
2. Each question carries **25** marks.
3. Unless otherwise stated,  $V_{BE(ON)} = 0.7 \text{ V}$  and  $V_T = 0.026 \text{ V}$ .
4. If you think not enough data has been given in any question you may assume reasonable values.
5. In design, when necessary, use the following E24 range of values:  
10 11 12 13 15 16 18 20 22 24 27 30 33 36 39 43  
47 51 56 62 68 75 82 91

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR**

**THIS PAPER CONTAINS SEVEN (7) PAGES INCLUDING THIS PAGE**

**QUESTION 1**

- (a) Find the voltages  $V_1$  and  $V_2$ , and the currents  $I_1$ ,  $I_2$ , and  $I_3$  in the circuit of Fig. 1. Assume  $|V_{BE}| = 0.7 \text{ V}$  for all transistors and  $\beta = \infty$ .

[10 marks]

 


Fig. Q1a

- (b) The differential amplifier of Fig. Q1b utilizes a resistor connected to the negative power supply to establish the bias current  $I$ . Assume  $V_{BE} = 0.7 \text{ V}$  and  $V_A = 50 \text{ V}$ .

- (i) For  $v_{B1} = v_{id}/2$  and  $v_{B2} = -v_{id}/2$ , where  $v_{id}/2$  is a small signal with zero average, find the magnitude of the differential gain,  $|v_o/v_{id}|$ .
- (ii) For  $v_{B1} = v_{B2} = v_{icm}$ , find the magnitude of the common-mode gain,  $|v_o/v_{icm}|$ .
- (iii) Calculate the CMRR in dB.

[15 marks]

 


Fig. Q1b

**QUESTION 2**

Fig. 2 shows a circuit for a differential amplifier with active load. Here  $Q_1$  and  $Q_2$  form the differential pair while the current source transistors  $Q_4$  and  $Q_5$  form the active loads for  $Q_1$  and  $Q_2$ , respectively. The dc bias circuit that establishes an appropriate dc voltage at the drains of  $Q_1$  and  $Q_2$  is not shown. It is required to design the circuit to meet the following specifications:

- Differential gain  $A_d = 100V/V$ .
- $I_{REF} = I = 200 \mu A$ .
- The dc voltage at the gates of  $Q_6$  and  $Q_3$  is  $+1.3 V$ .
- The dc voltage at the gates of  $Q_7$ ,  $Q_4$  and  $Q_5$  is  $+1.3 V$ .

The technology available is specified as follows:  $k'_n = 3k'_p = 120 \mu A/V$ ;  $|V_{tn}| = |V_{tp}| = 0.5 V$ ;  $|V_{An}| = |V_{Ap}| = 20 V$ .

- (a) Specify the required value of  $R$ .
- (b) Specify  $W/L$  ratio,  $\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_6$  for transistors  $Q_3$  and  $Q_6$ .
- (c) Specify  $W/L$  ratio,  $\left(\frac{W}{L}\right)_7$  for transistor  $Q_7$ .
- (d) Specify  $W/L$  ratio,  $\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2$  for transistors  $Q_1$  and  $Q_2$ .
- (e) Specify  $W/L$  ratio,  $\left(\frac{W}{L}\right)_4 = \left(\frac{W}{L}\right)_5$  for transistors  $Q_4$  and  $Q_5$ .

For dc bias calculations you may neglect channel-length modulation. You may find the following formulae useful:

$$g_m = \frac{I}{V_{OV}} = \frac{I}{V_{GS} - V_t} \quad r_o = \frac{V_A}{I_D} \quad I_D = \frac{1}{2} k'_n \left(\frac{W}{L}\right) (V_{OV})^2$$

[25 marks]

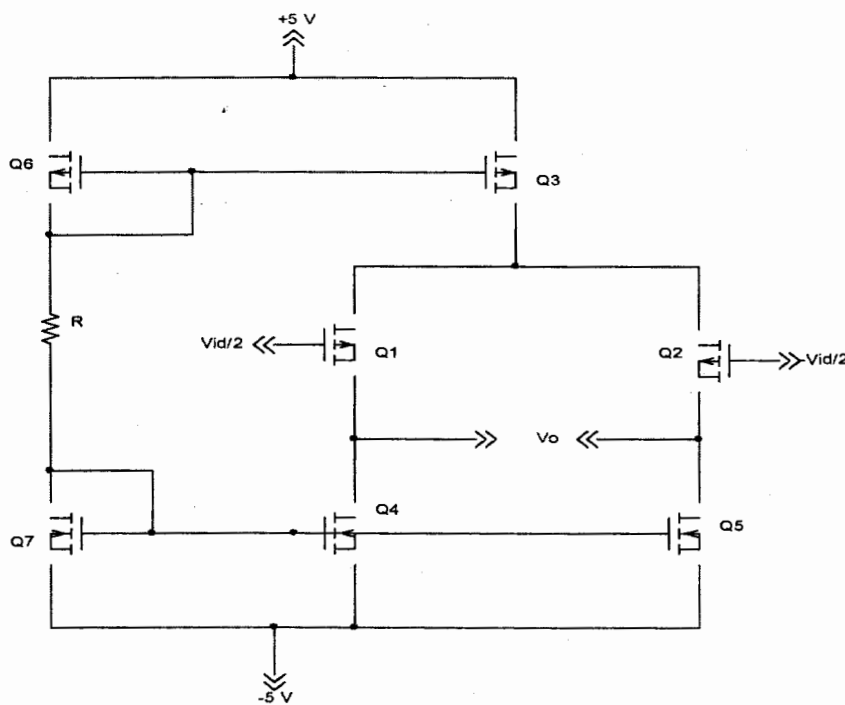


Fig. 2

**QUESTION 3**

Fig. 3 shows a class AB output stage with short-circuit protection. The output stage is meant to supply a maximum average power of 3.125 W to a 16- $\Omega$  speaker. The output transistors  $Q_1$  and  $Q_2$  both have minimum value of  $\beta = 50$ .

- (a) If a current of 2 mA must flow through the  $V_{BE}$  multiplier circuit when  $Q_1$  is supplying the peak load current, determine suitable value for  $I_{bias}$ . [9 marks]
- (b) Select suitable values for  $R_1$  and  $R_2$  so that the  $V_{BE}$  multiplier will provide  $V_{BB} = 1$  V for biasing the output transistors. Since minimum current through the  $V_{BE}$  multiplier is 2 mA, assume that current through  $R_1$  and  $R_2$  is 1 mA. Use  $V_{BE3} = 0.6$  V. [8 marks]
- (c) Select suitable value for  $R_{e1} = R_{e2}$  for short-circuit protection such that  $Q_4$  turns on and absorbs all of  $I_{bias}$  when the load current reaches 1.5 A. For  $Q_4$ ,  $I_s = 10^{-14}$  A. [8 marks]

 


Fig. 3

**QUESTION 4**

An IF amplifier for an AM radio receiver is to be designed with  $f_o = 455$  KHz and a 3-dB bandwidth of 10 KHz.

- (a) Using two stagger-tuned stages, find  $f_{o1}$ ,  $B_1$ ,  $f_{o2}$  and  $B_2$ .

[11 marks]

- (b) Using 500  $\mu$ H inductors, find C and R for each stage.

[14 marks]

**QUESTION 5**

- (a) In the current differencing amplifier of Fig. Q5a,  $v_i = 100$  mV. Calculate  $A_v$  and  $V_{o(AC)}$ .

[10 marks]

 


Fig. Q5a

- (b) Given a CA3080 operational transconductance amplifier (OTA) with a supply voltage  $\pm V = \pm 10$  V and an  $I_{ABC}$  of  $100 \mu\text{A}$ , find: (i) the OTA transconductance  $g_m$ ; (ii) the output voltage with an input of  $10$  mV and a load resistor of  $1$  K $\Omega$ ; (iii) the  $I_{ABC}$  needed to give a  $1$  V output with a  $120$  mV input and a load resistance of  $1$  K $\Omega$ .

For the CA3080 OTA,

$$g_m = \left( \frac{300}{V} \right) (I_{ABC})$$

[15 marks]

**QUESTION 6**

A PLL is needed with a capture range ( $f_c$ ) of 200 Hz, and a free running frequency ( $f_o$ ) of 10 KHz. The NE565 PLL IC is to be used.  $\pm 5$  V supplies are connected to the NE565, so that  $V_{net} = 10$ .

- (a) Determine the lock range ( $f_L$ ). [5 marks]
- (b) Choose component values,  $R_1$ ,  $C_1$ , and  $C_2$ , which when connected to the NE565 will give these parameters. [15 marks]
- (c) How would you reduce the lock range to 4000 Hz? [5 marks]

For the NE565 PLL:

$$f_o = \frac{1}{3.7R_1C_1}$$

$$f_L = \pm \frac{8f_o}{V_{net}}$$

$$f_c = \pm \sqrt{\frac{f_L}{2\pi(3600)(C_2)}}$$