

UNIVERSITY OF SWAZILAND

MAIN EXAMINATION 2005/2006

FACULTY OF SCIENCE

DEPARTMENT OF ELECTRONIC ENGINEERING

TITLE OF PAPER: ELECTRONICS III—PAPER 2

COURSE NUMBER: E510

TIME ALLOWED: THREE HOURS

INSTRUCTIONS:

- 1. Answer any FOUR (4) of the following six questions.**
- 2. Each question carries 25 marks.**
- 3. If you think not enough data has been given in any question you may assume reasonable values.**

THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR

THIS PAPER CONTAINS SEVEN (7) PAGES INCLUDING THIS PAGE

QUESTION 1

- (a) A three-phase, 400-V motor rated 75 KW is loaded at 80% of its rating. The motor is 90% efficient at this load and operates at a power factor of 0.85 lagging. What is the line current for the motor?
[9 MARKS]
- (b) A three-phase, Y-connected, 400 V, 1450 RPM, 60 KW induction motor has the following equivalent circuit parameters per phase: $R_s = 0.075 \Omega$, $R_r = 0.06 \Omega$, $X_s = 0.63 \Omega$, $X_r = 0.94 \Omega$, $X_m = 19.5 \Omega$.
- (i) Calculate the no-load current (assume $n_r = n_s$ at no-load).
[6MARKS]
- (ii) Calculate the line current when the motor develops rated KW at rated speed.
[10 MARKS]

QUESTION 2

- (a) A shunt field DC motor is rated 1000 W, 48 V, 2400 RPM, and draws 25 A when operating at rated conditions. The field rheostat is adjusted so that the stator flux per pole is reduced by 10%, and the load is adjusted so that the armature current is 18 A. Find the new operating speed of the motor. The shunt field has a resistance of 25 Ω , and the armature winding has a resistance of 0.5 Ω .

[11 MARKS]

- (b) The electrical specifications of a 230 V(ac), split-phase induction motor are as follows: $R_{mw} = 4 \Omega$, $R_{aw} = 8 \Omega$, $X_{mw} = j10 \Omega$, $X_{aw} = j12 \Omega$.

- (i) Calculate the magnitude and angle of the locked-rotor current.

[7 MARKS]

- (ii) Specify a capacitor that, when added to the auxiliary winding, will cause the motor to develop maximum starting torque.

[7 MARKS]

QUESTION 3

- (a) A permanent-magnet generator has 100 turns in the coil, and the permanent magnets provide a flux per pole of 0.05 Wb. What is the required rotational speed of the coil (in RPM) to generate 250 V_{rms}?

[10 MARKS]

- (b) A three-phase synchronous generator is connected to an infinite bus at 11 KV (line-to-line), 50 Hz. The generator has a synchronous reactance of 1.4 Ω per phase and negligible armature resistance. The machine is operating with an output of 75 MVA at 0.9 power factor, lagging. Find the internal generated voltage and power angle. Draw a phasor diagram showing the terminal voltage as the reference voltage, the generated voltage, the armature current, and the voltage drop across the synchronous reactance.

[15 MARKS]

QUESTION 4

- (a) The turn-on and turn-off current and voltage waveform on an IGBT switch with an inductive load are shown in Fig Q4a. The circuit is switched at 50% duty cycle at 40 KHz. The IGBT has $V_{CE(on)}$ rating of 2.5 V, $t_{d(on)} = 50$ ns, and $t_{d(off)} = 400$ ns. Determine the average power dissipation in the IGBT.

[15 MARKS]

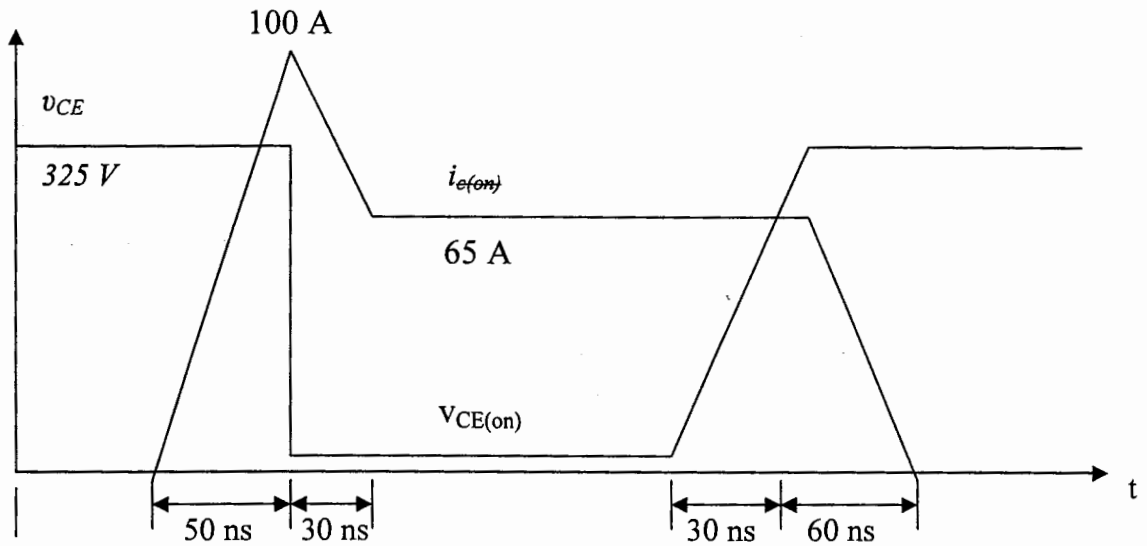


Fig Q4a

- (b) Select the components of the snubber circuit of Fig. Q4b. The supply voltage V_s is a step of dc voltage 350 V. The thyristor powers a 10- Ω resistive load R . R_s should limit the maximum current through the capacitor to 350 A. The maximum permitted values of di_T/dt and dv_T/dt are 250 A/ μ s and 350 V/ μ s respectively. Ignore the switching times.

[10 MARKS]

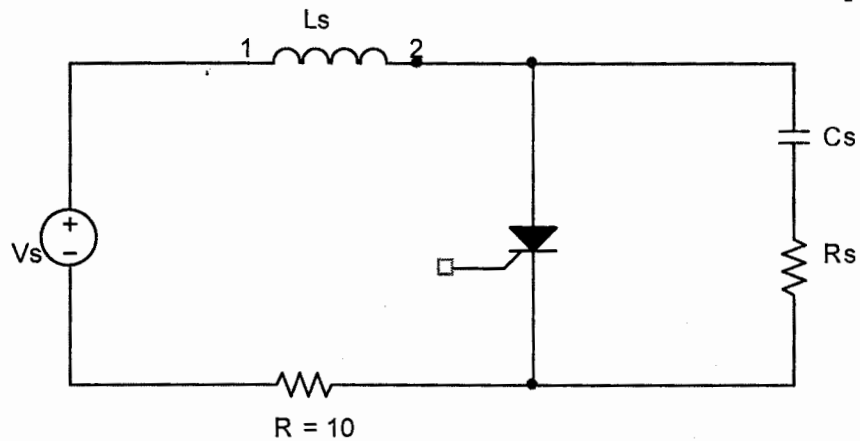


Fig Q4b

QUESTION 5

- (a) A boost converter operating in continuous conduction mode has the following parameters:

$$V_s = 5 \text{ V} \quad L = 300 \text{ } \mu\text{H} \quad R_L = 20 \text{ } \Omega \quad C = 330 \text{ } \mu\text{F} \quad f_s = 25 \text{ KHz} \quad D = 0.35$$

- (i) Determine V_o .
(ii) Sketch the inductor current i_L .
(iii) Determine the peak-to-peak voltage ripple in the output.

[12 MARKS]

- (b) In a full-bridge converter, the duty ratio is adjusted to regulate the output voltage to 12 V. The input dc voltage varies in the range 20 V to 30 V. The converter is switched at 80 KHz. Find the range of pulse width of the switching waveform applied at the switch.

[13 MARKS]

QUESTION 6

- (a) A full-bridge inverter with square-wave switching operates with $D = 0.8$, $f_s = 50$ Hz, $V_s = 400$ V, provides power to a load of 10Ω in series with 10 mH. Determine the voltage transfer ratio.

[10 MARKS]

- (b) A three-phase, 50 Hz induction motor is rated 50 KW, 1460 RPM. The motor is driven by a variable-frequency drive. What are the rated torque and power for the motor when operating at 20 Hz? What would the expected full-load speed be?

[15 MARKS]

