

**UNIVERSITY OF SWAZILAND**  
**FIRST SEMESTER EXAMINATION 2006/2007**  
**FACULTY OF SCIENCE**

**DEPARTMENT OF ELECTRONIC ENGINEERING**

**TITLE OF PAPER: ELECTRICAL CIRCUITS**

**COURSE NUMBER: E310**

**TIME ALLOWED: THREE HOURS**

**INSTRUCTIONS:**

1. Answer any FOUR (4) of the following six questions.
2. Each question carries 25 marks.

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR**

**THIS PAPER CONTAINS SIX (6) PAGES INCLUDING THIS PAGE**

**QUESTION 1**

- (a) Using the format approach (that is, by inspection) write the mesh equations in matrix form for the network of Fig.1. Using determinants (Cramer's rule), solve for the current THROUGH  $R_3$ .

[12 marks]

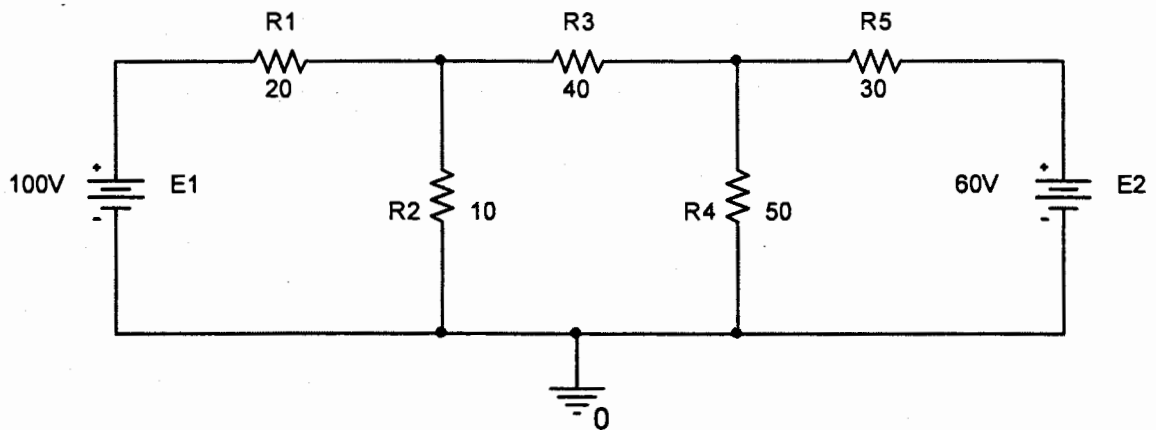


Fig. 1

- (b) Using the format approach (that is, by inspection) write the nodal equations in matrix form for the network of Fig.2. Using determinants (Cramer's rule), solve for the node voltages  $V_1$  and  $V_2$ .

[13 marks]

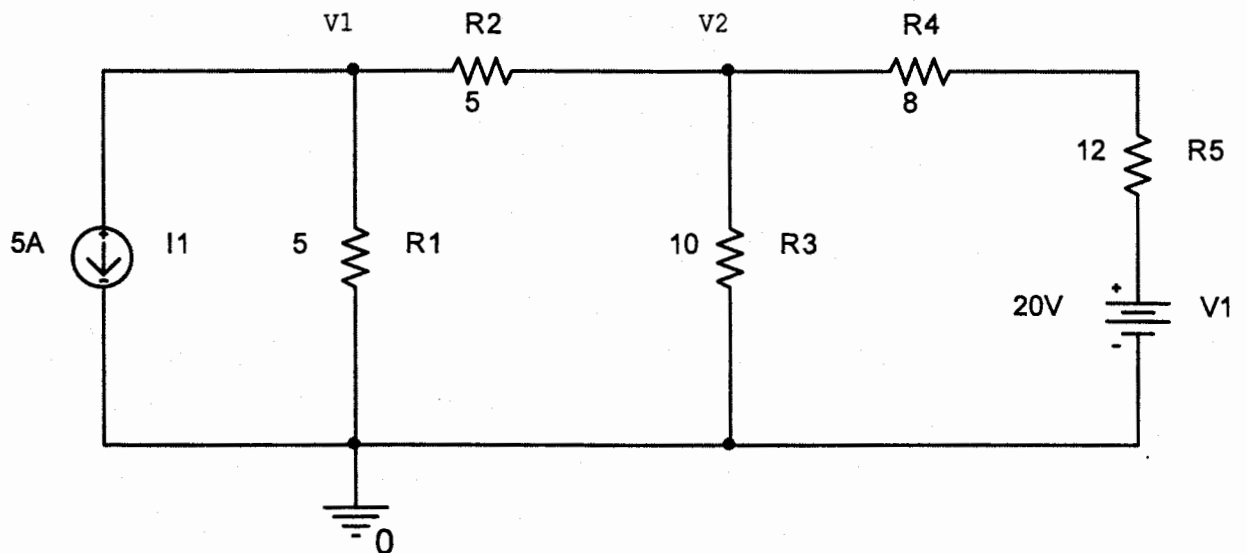


Fig. 2

**QUESTION 2**

- (a) Find the Norton equivalent circuit for the network external to the resistor  $R$  for the circuit of Fig. 3.

[15 marks]

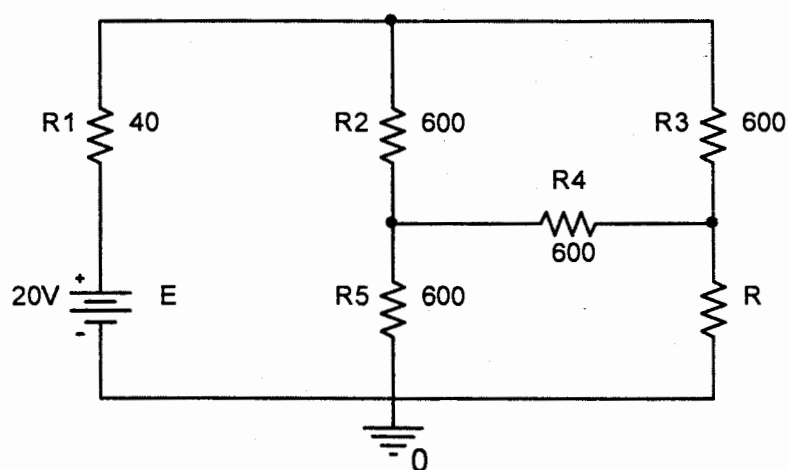


Fig. 3

- (b) For the circuit of Fig. 4, find the value of  $R$  for maximum power to  $R$ . Determine the maximum power to  $R$ .

[10 marks]

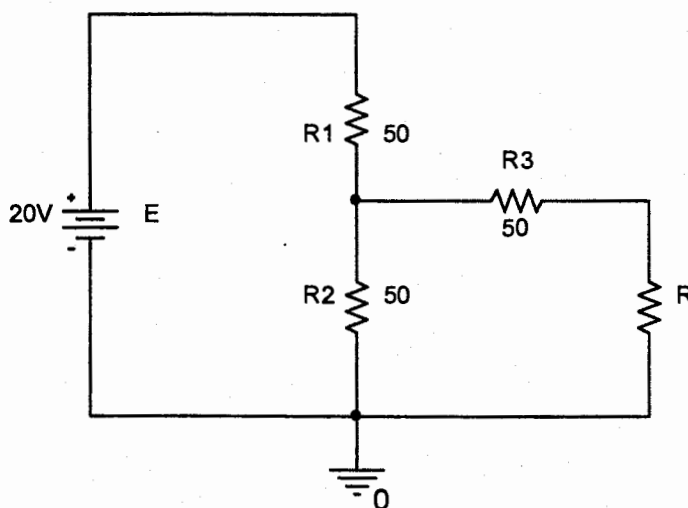
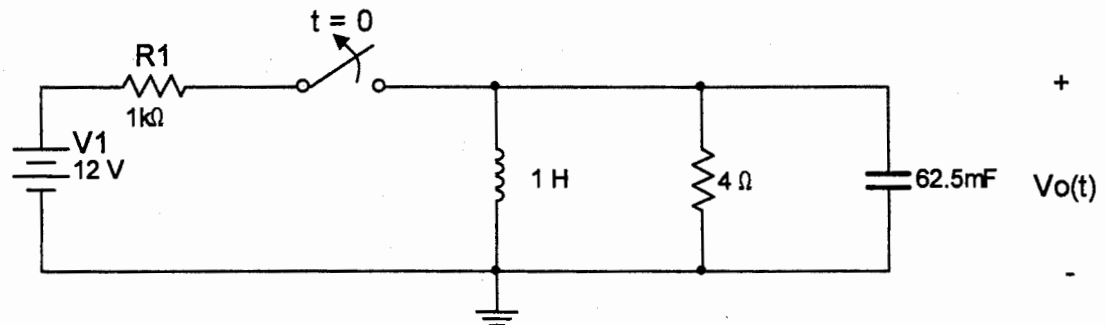


Fig. 4

**QUESTION 3**

In the circuit of Fig. 5, the switch is opened at  $t = 0$ . Find  $v_c(t)$  for  $t > 0$ . Assume steady state conditions exist at  $t = 0^-$ .

[25 marks]

**QUESTION 4**

(a) For the parallel circuit of Fig. 6, find a series circuit that will have the same total impedance.

[10 marks]

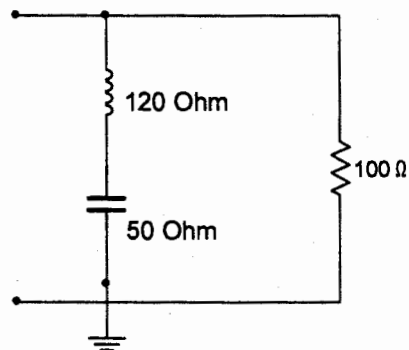


Fig. 6

(b) A single-phase motor draws 5 KW at a power factor of 0.88 when 230 V is applied.

- (i) Calculate the apparent and reactive power drawn by the motor and the power factor angle.
- (ii) Draw the power triangle.
- (iii) Calculate the current drawn by the motor.

[15 marks]

**QUESTION 5**

- (a) Three impedances each  $Z = (24 + j12) \Omega$ , are connected in delta to a 400 V three-phase source. Calculate the line current, power factor, and total three-phase real and reactive power.

[13 marks]

- (b) For the circuit of Fig. 7:

- (i) Find the value of  $X_C$  at resonance ( $f_p$ ).  
 (ii) Find the total impedance  $Z_T$  at resonance ( $f_p$ ).  
 (iii) Find the currents  $I_L$  and  $I_C$  at resonance ( $f_p$ ).  
 (iv) Find  $Q_p$ .

[12 marks]

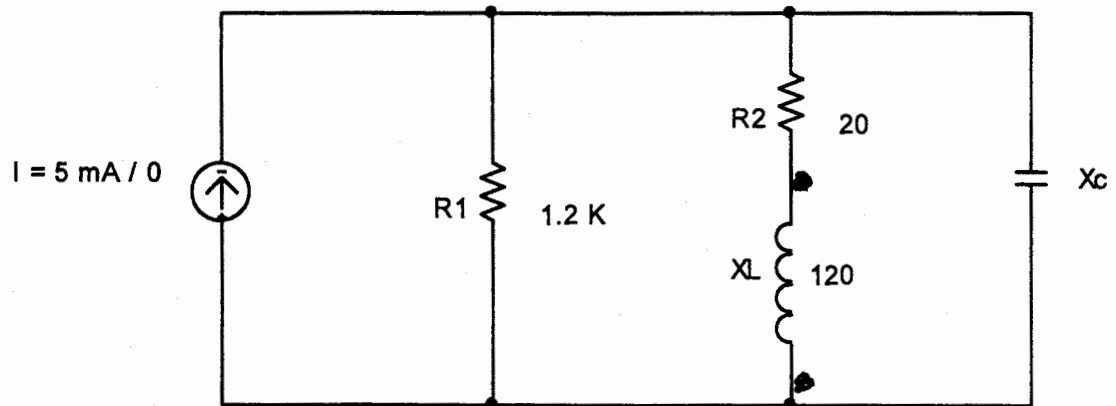


Fig. 7

**QUESTION 6**

- (a) For the circuit of Fig. 8, find the transformation ratio required to deliver maximum power to the speaker. Find the maximum power delivered to the speaker.

[10 marks]

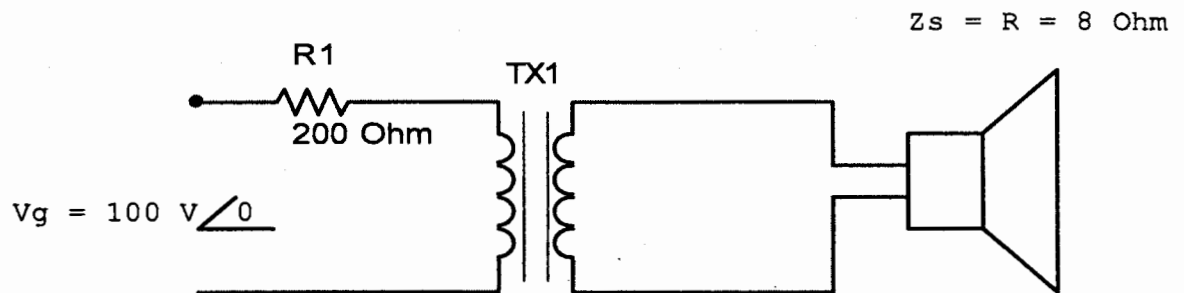


Fig. 8

- (b) A magnetic core with an airgap is configured as shown in Fig. 9. The cross-sectional area is  $7.5 \text{ cm}^2$ , the gap length is  $0.065 \text{ cm}$ , the mean core length is  $28 \text{ cm}$ , there are 400 turns and the relative permeability is  $10^5$ . Ignore fringing and leakage flux. In order to maintain a flux density of  $1.8 \text{ T}$  in the core, calculate the coil current and the magnetic field intensity (H) in the core and the gap.

[15 marks]

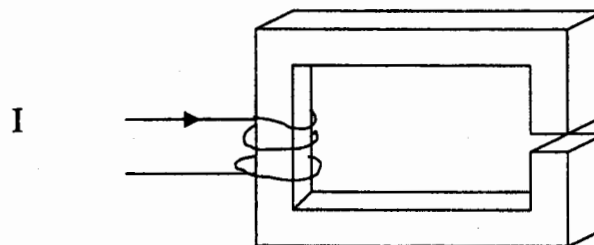


Fig. 9