

**UNIVERSITY OF SWAZILAND  
MAIN EXAMINATION DECEMBER 2006**

**FACULTY OF SCIENCE**

**DEPARTMENT OF ELECTRONIC ENGINEERING**

**TITLE OF PAPER: ANALOGUE ELECTRONICS III**

**COURSE NUMBER: E511**

**TIME ALLOWED: THREE HOURS**

**INSTRUCTIONS:**

1. Answer any **FOUR (4)** of the following six questions.
2. Each question carries 25 marks.
3. Unless otherwise stated,  $V_{BE(ON)} = 0.7 \text{ V}$  and  $V_T = 0.025 \text{ V}$ .
4. If you think not enough data has been given in any question you may assume reasonable values.
5. A sheet containing some useful equations is attached at the end of the examination paper.


**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION  
HAS BEEN GIVEN BY THE INVIGILATOR**

**THIS PAPER CONTAINS EIGHT (8) PAGES INCLUDING THIS PAGE**

**QUESTION ONE**

(a) A diode has  $v_D = 0.7 \text{ V}$  at  $1 \text{ mA}$  and is characterized by  $n = 2$ . It is connected in series with a  $150\text{-}\Omega$  resistor to a  $1.2 \text{ V}$  dc supply. Using iterative analysis and the exponential diode model, give an accurate (to 3 significant figures) estimate of the current through the diode. (10 marks)

(b) Using basic principles of ideal opamp circuits (such as  $i_{in} = 0$ ) and the diode exponential model obtain the relationships between the output and input voltages in each of the three circuits in Fig. Q1b. Specify the range of validity of the input voltages. (7 marks)

 


**Fig. Q.1b**

(i)

(ii)

(iii)

(c) Use the results obtained in (b) to show that the circuit in Fig. Q.1c is a multiplier of the voltages  $v_1$  and  $v_2$ . Assume that all diodes are matched and the resistors are equal. Specify the range of validity of these voltages. (8 marks)

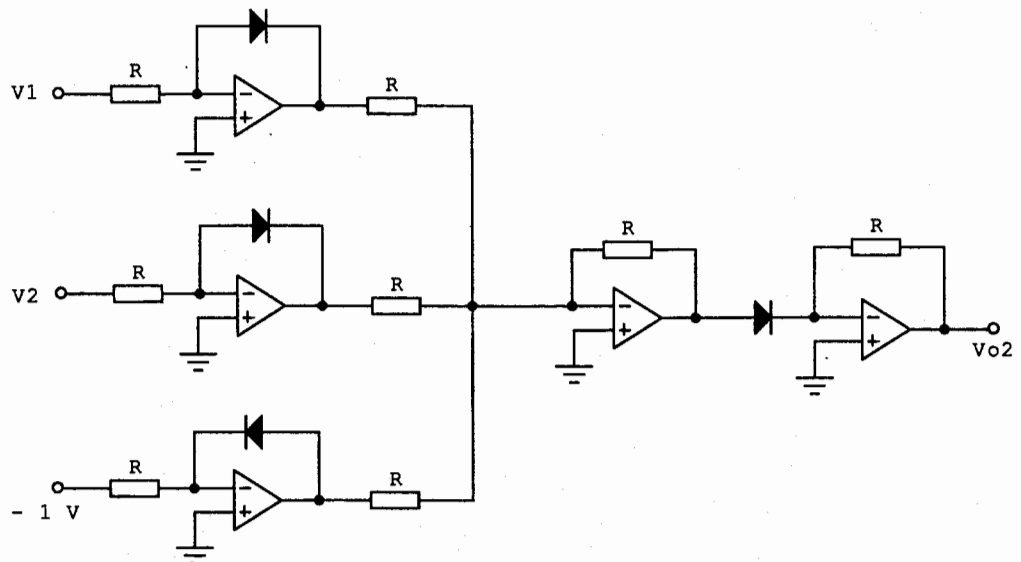

**Fig. Q.1c**

## QUESTION TWO

- (a) A circuit designer has produced the current mirror circuit shown in Fig. Q2a. Transistors Q1 and Q2 may be assumed to be matched. On testing the circuit it is found that it does not work as expected. What is wrong with the circuit and how would you correct the mistake? (5 marks)

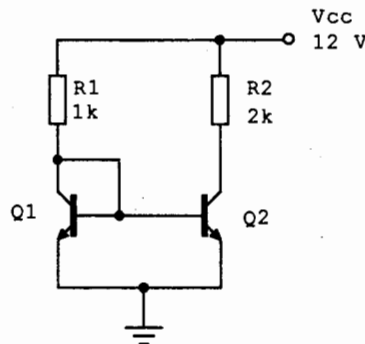


Fig.Q2a

- (b) For the Widlar current source circuit shown in Fig. Q.2b, the transistors are matched and  $\beta$  may be assumed to be  $\gg 1$  unless otherwise stated.

- (i) Show that  $I_o = \frac{V_T}{R_E} \ln \left( \frac{I_{ref}}{I_o} \right)$  (5 marks)
- (ii) Design the current source so that  $I_o = 400 \mu\text{A}$  using  $\pm 15 \text{ V}$  supplies. Resistor values used should not exceed  $20 \text{ k}\Omega$ . (5 marks)
- (iii) What is the maximum load resistance that can be connected to your current source in (ii)? (4 marks)
- (iv) Calculate the output resistance of your current source when the transistors used have  $\beta=100$  and  $V_A = 100 \text{ V}$ . (6 marks)

 


Fig.Q2b

**QUESTION THREE**

- (a) (i) Derive an expression which can be used to calculate the input offset voltage due to mismatch in the collector resistors of a basic BJT differential amplifier, assuming that  $\alpha = 1$  and that all transistors are matched.. (5 marks)
- (ii) Use your expression to evaluate the mismatch in a BJT differential amplifier with a total bias current of  $500 \mu\text{A}$  when collector resistors have tolerances of  $\pm 2\%$ . (2 marks)
- (iii) If emitter degeneration resistors with  $R_E = 8r_e$  are added what input offset voltage results? (4 marks)

(b) Figure Q.3b shows a differential amplifier whose gain is controlled by a dc voltage  $V_c$ .

- (i) Using the exponential I-V equation of a BJT in active mode and the relationships between the currents and voltages shown in the diagram, show that under steady state conditions the current  $I_3$  is given by

$$I_3 = \frac{V_o}{R_1} - \frac{V_{BE4}}{2R_2} + \left( \frac{1}{2R_2} - \frac{1}{R_1} \right) V_c \quad (5 \text{ marks})$$

- (ii) Explain how the voltage  $V_c$  controls the gain of the amplifier. (3 marks)
- (iii) Using the relationship in (i) explain how can the output voltage can be made independent of  $V_c$  while the amplifier is stabilizing after a change in  $V_c$ ? (2 marks)
- (iv) Obtain expressions for the  $g_m$  and gain of the amplifier in terms of  $V_c$  and the circuit parameters. (4 marks)

 


Fig. Q.3b

## QUESTION FOUR

- (a) A MOSFET with constant  $V_{GS}$  operating in the saturation region is found to have  $i_D = 1.8 \text{ mA}$  at  $v_{DS} = 5 \text{ V}$  and  $i_D = 1.85 \text{ mA}$  at  $v_{DS} = 7 \text{ V}$ . Using a sketch of output characteristics ( $i_D$  vs  $v_{DS}$ ) of a MOSFET use this data to calculate the corresponding values of  $r_o$ ,  $V_A$  and  $\lambda$  for this MOSFET. (4 marks)
- (b) A MOSFET biased as shown in Fig. Q.4b has  $k_n' \left( \frac{W}{L} \right) = 1 \text{ mA/V}^2$ .
- (i) What value of  $R_S$  should be used to get  $v_D = 2 \text{ V}$ . Specify  $R_S$  to 1 significant digit. (6 marks)
- (ii) Find the actual value of  $v_D$  when the resistor accurate to 1 significant digit found in (i) is used. (6 marks)

 


Fig Q.4b

- (c) Determine the output current at  $V_o = 5 \text{ V}$  for the MOS current mirror given in Fig. Q.4c. The transistors used have  $V_{t1} = V_{t2} = 1 \text{ V}$ ,  $\lambda_1 = \lambda_2 = 0.02 \text{ V}^{-1}$ , and  $k_n' \left( \frac{W}{L_1} \right) = 200 \text{ } \mu\text{A/V}^2$ ,  $k_n' \left( \frac{W}{L_2} \right) = 300 \text{ } \mu\text{A/V}^2$ . (9 marks)

 


Fig Q.4c

## QUESTION FIVE

- (a) Figure Q.5a shows a simplified input stage of the NE592 video amplifier. This input stage is followed by another differential stage and emitter followers so that the overall gain of the IC with terminals G1A and G1B connected is  $g_m k R_L' = 400$  where  $g_m$  is transconductance of the input stage,  $R_L'$  is the effective differential load impedance on the input stage and  $k$  is the gain of the subsequent stages after the input stage. Through use of the gain select terminals G1A, G1B, G2A and G2B the gain can be varied between 0 (minimum) and 400 (maximum) by shorting, open-circuiting or connecting external R or RLC circuits to terminals G1A and G1B, or G2A and G2B. In summary, the gain depends on the  $g_m$  of the input stage.
- What is the gain when all gain select terminals are left open? (2 marks)
  - What is the gain of the amplifier when terminals G1A and G1B are shorted. (2 marks)
  - Estimate the gain of the amplifier when terminals G2A and G2B are shorted (6 marks)
  - Estimate the gain of the amplifier when a resistor of 1 k $\Omega$  is connected between G2A and G2B. (2 marks)
  - The series RLC circuit shown in Fig. Q.5a is connected between G1A and G1B. Find an expression for the  $g_m$  of the input stage and the variation of the gain of the amplifier with frequency. Sketch the gain-frequency characteristic. (6 marks)

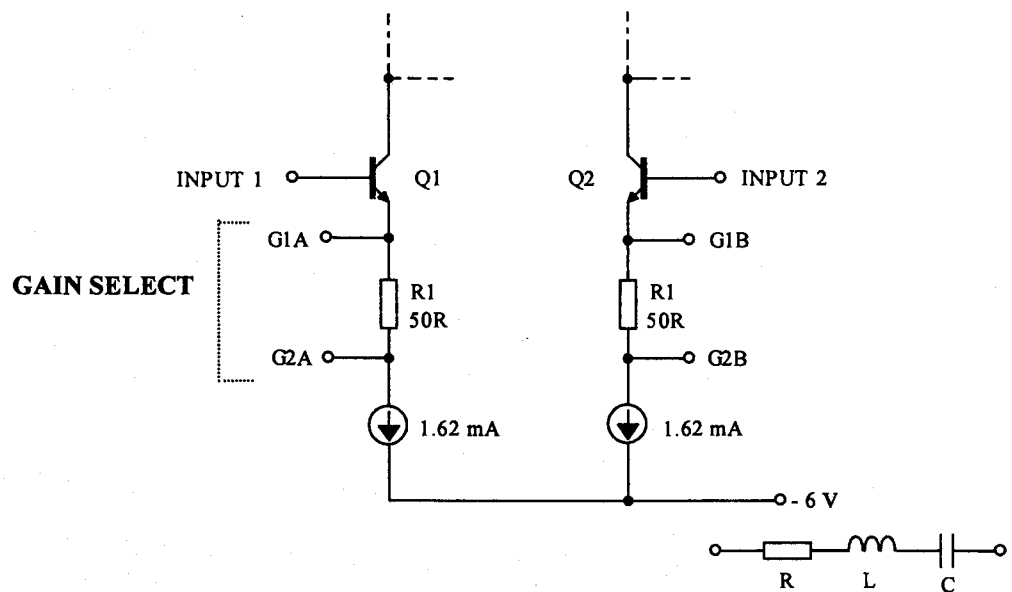


Fig. Q.5a

**Question 5 continued**

- (b) (i) Sketch a CMOS logic gate realization of the function

$$Y = A + B(C + D)$$

*(5 marks)*

- (ii) How many transistors does it need?

*(2 marks)*

===== END OF EXAMINATION PAPER =====

**SOME USEFUL MOSFET EQUATIONS**

$$i_D = k'_n \frac{W}{L} \left[ (v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right] \text{ in triode region}$$

$$i_D = \frac{1}{2} k'_n \frac{W}{L} (v_{GS} - V_t)^2 \text{ in saturation region}$$

$$i_D = \frac{1}{2} k'_n \frac{W}{L} (v_{GS} - V_t)^2 (1 + \lambda v_{DS}) \text{ in saturation region with Channel Modulation effect}$$

**BJT EBERS-MOLL EQUATIONS**

$$i_E = \frac{I_s}{\alpha_F} (e^{v_{BE}/V_T} - 1) - I_s (e^{v_{BC}/V_T} - 1)$$

$$i_C = I_s (e^{v_{BE}/V_T} - 1) - \frac{I_s}{\alpha_R} (e^{v_{BC}/V_T} - 1)$$

$$i_B = \frac{I_s}{\beta_F} (e^{v_{BE}/V_T} - 1) + \frac{I_s}{\beta_R} (e^{v_{BC}/V_T} - 1)$$