

**UNIVERSITY OF SWAZILAND**  
**FIRST SEMESTER EXAMINATION 2006/2007**  
**FACULTY OF SCIENCE**

**DEPARTMENT OF ELECTRONIC ENGINEERING**

**TITLE OF PAPER: POWER ELECTRONICS AND DRIVES**

**COURSE NUMBER: EIN510**

**TIME ALLOWED: THREE HOURS**

**INSTRUCTIONS:**

1. Answer any **FOUR (4)** of the following six questions.
2. Each question carries 25 marks.
3. If you think not enough data has been given in any question you may assume reasonable values.

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR**

**THIS PAPER CONTAINS FIVE (5) PAGES INCLUDING THIS PAGE**

**QUESTION 1**

- (a) The data sheets of a switching device specify the following switching times corresponding to the linearized characteristics shown in Fig. Q1a for clamped inductive switchings:

$$t_{d(on)} = 40 \text{ ns} \quad t_{ri} = 80 \text{ ns} \quad t_{fv} = 40 \text{ ns} \quad t_{rv} = 80 \text{ ns} \quad t_{fi} = 160 \text{ ns} \quad t_{d(off)} = 100 \text{ ns}$$

Calculate the switching device power loss if the switch is operated at 100 kHz, assuming  $V_d = 400 \text{ V}$ ,  $I_o = 10 \text{ A}$ ,  $V_{on} = 2.5 \text{ V}$  and 50% duty ratio.

[15 MARKS]

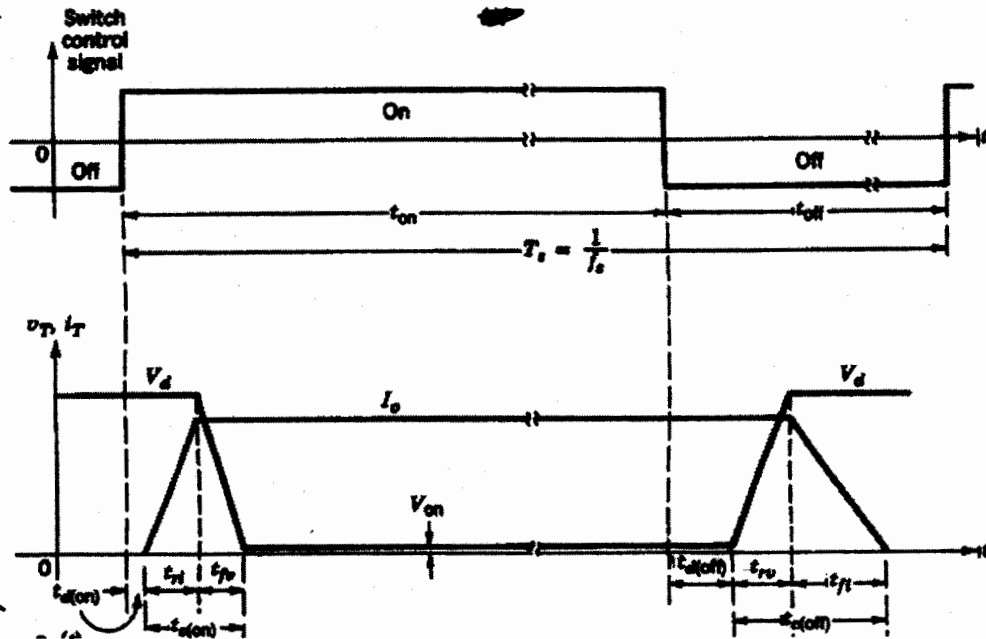


Fig. Q1a

- (b) Select the components of the snubber circuit of Fig. Q1b. The supply voltage  $V_s =$  a step of dc voltage 350 V. The thyristor powers a 10- $\Omega$  resistive load R.  $R_s$  should limit the maximum current through the capacitor to 50 A. The maximum permitted values of  $di_T/dt$  and  $dv_T/dt$  are 100 A/ $\mu$ s and 350 V/ $\mu$ s respectively. Ignore the switching times.

[10 MARKS]

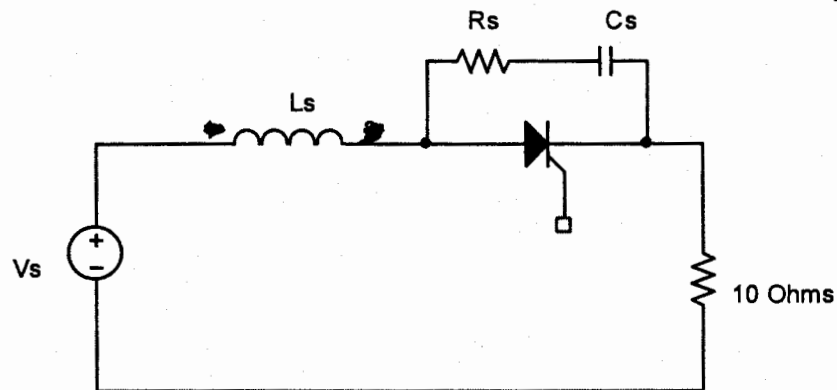


Fig Q1b

**QUESTION 2**

Design a power converter for the following specifications:

$$V_s = 20 \text{ V} \sim 30 \text{ V}$$

$$V_o = 48 \text{ V}$$

$$f_s = 100 \text{ kHz}$$

$$R_L = 8 \Omega$$

- (a) Draw the circuit diagram of a suitable power converter.

[5 MARKS]

- (b) Select values for L and C such that

(i) the input current ripple  $\Delta i_L$  is 20 mA and

(ii) the peak output voltage ripple  $\Delta v_o$  is 2% of  $V_o$ .

[20 MARKS]

**QUESTION 3**

- (a) In a full-bridge converter, the duty ratio is adjusted to regulate the output voltage to 15 V. The input dc voltage varies in the range 20 V to 30 V. The converter is switched at 100 kHz. Find the range of pulse width of the switching waveform applied at the switch.

[9 MARKS]

- (b) In a single-phase full-bridge SPWM inverter, the input dc voltage varies in a range of 283 to 325 V.

(i) What is the highest  $V_{o1}$  (rms) that can be obtained and stamped on its nameplate as its voltage rating?

(ii) Find the range of maximum duty cycle of the SPWM switching waveform.

[16 MARKS]

**QUESTION 4**

- (a) The full-bridge converter shown in Fig. Q4a is fed with an input voltage of 230 V at 50 Hz. It is required to provide a dc current of 20 A to a coil of inductance 0.5 H and resistance 3  $\Omega$ .
- Find the phase delay angle  $\alpha$ .
  - If transistors replace the SCRs in the full-bridge circuit and PWM control is used, determine the pulse width  $\delta$ .

[9 MARKS]

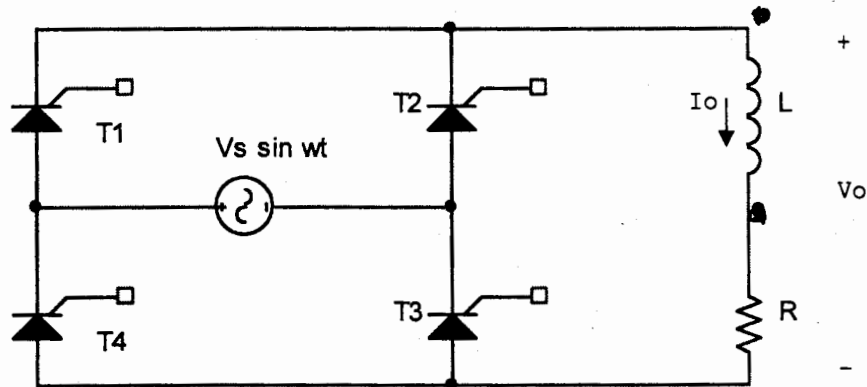


Fig. Q4a

- (b) A 400 V three-phase full-bridge converter is connected to a 400 V DC grid. Find the firing angle  $\alpha$ .

[16 MARKS]

**QUESTION 5**

- (a) Develop the averaged model and obtain the transfer function for a dc-dc Buck converter in which the source voltage is 48 Vdc and the output voltage is 24 Vdc operating in the continuous conduction mode. Other components are  $L = 1$  mH and  $C = 220$   $\mu$ F.
- (b) For the Buck converter in (a), determine the transient response of the output voltage when the duty ratio undergoes a step change to 0.7 (in the next switching period) with output current  $I_o = 5$  A.

[10 MARKS]

[15 MARKS]

**QUESTION 6**

- (a) A dc motor with a voltage rating of 400 V for both armature and field is used as a separately excited motor. The field is supplied at the rated voltage. The armature is supplied by a thyristor bridge from a three-phase, 400 V, 50 Hz ac bus. The inductance per phase of the ac bus is 200  $\mu$ H. The armature is rated for 100 A and has a resistance of 0.2  $\Omega$ . The no-load speed is 1200 RPM. Determine the delay angle required to achieve a speed of 800 RPM at the rated current in the armature. [Hint: For a 3-phase full-bridge converter with source inductances,

$$V_o = \frac{3\sqrt{2}}{\pi} V_{LL} \cos \alpha - \frac{3\omega L_s}{\pi} I_o \quad ]$$

[14 MARKS]

- (b) A three-phase, 50 Hz induction motor is rated 400 V, 1460 RPM. How much dc voltage should a variable-frequency drive provide to the motor at 35 Hz?

[11 MARKS]