

UNIVERSITY OF SWAZILAND
FACULTY OF SCIENCE
DEPARTMENT OF ELECTRONIC ENGINEERING

MAIN EXAMINATION, MAY 2008

Title of the Paper: **DIGITAL ELECTRONICS I**
Course Number: **E362**
Time Allowed: **Three Hours.**

Instructions:

1. Answer any FIVE (5) of the six questions.
2. Each question carries 20 marks, distributed as shown next to the right hand margin

DO NOT OPEN THIS PAPER UNTIL PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR.

THIS PAPER HAS 7 PAGES, INCLUDING THIS PAGE

QUESTION 1

- a) Using the tabulation method, simplify the following Boolean function F:

$$F(v, w, x, y, z) = \Sigma(0, 2, 4, 6, 10, 11, 12, 14, 15, 16)$$

(hex numbers in the brackets of the above function) [10]

- b) Implement the Boolean function below using only NAND gates. Assume that complement inputs are available only at the input terminals and nowhere else. The implementation must have its function support.

$$F(A, B, C, D, E) = (\overline{A} + B)(C\overline{D} + \overline{E})$$
 [10]

QUESTION 2

- a) Using a minimum number of NOR gates only, implement the circuits for the expressions below. Assume that both normal and complement inputs are available.

(i) $F_1 = A \oplus B \oplus C$ [5]

(ii) $F_2 = (A + BC)(A + B + CD + \bar{A}C)$ [5]

- b) Using the block diagram transformation method, implement the function below with NOR gates only. The circuit diagram should be multi-level. Assume that both normal and complement inputs are available, and show all necessary working.

$F = C(B + AD) + A(\bar{B} + C\bar{D})$ [10]

QUESTION 3

- a) (i) Implement the sum S of a Binary Full Adder with AND, OR and NOT gates. [5]
- (ii) Verify that the sum S for a full adder can be put in the form $S = A \oplus B \oplus C_{in}$, and implement this form in gates. [10]
- b) Implement the function F with an 8-to-1 Multiplexer. You may make x , y and z selectors.

$$F = \bar{w}\bar{x}\bar{y}\bar{z} + \bar{w}x\bar{y}z + \bar{w}xy\bar{z} + \bar{w}xyz + w\bar{x}\bar{y}\bar{z} + w\bar{x}\bar{y}z + wx\bar{y}\bar{z} + wxyz$$


[5]

QUESTION 4

- a) Using a three-bit message code, show how an even-parity generator can be implemented using gates. ***(The final circuit implementation must be in XOR and/or XNOR gates. Show all necessary working)*** [6]
- b) Do a parity check on the message generated by the even parity generator in (a), and show that the expression for the even parity checker function, C , can be written in XOR/XNOR operations only. [7]
- c) Create a 4-bit reflected (Gray) code from the start byte, 1001. [7]

QUESTION 5

- a) Three 4-to-1 Multiplexers are available. Arrange the three Multiplexers into a larger Multiplexer with the largest number of inputs possible and least number of address-bits (*variables of the selector lines*). How many address bits and how many inputs are in your solution? Show a clearly labeled diagram and list the address of each input. [10]
- b) The 16x4 ROM together with the 2^0 line as shown in the figure below is to be used to convert a 4-bit binary number to its corresponding 2-digit BCD number. Specify the truth table for the ROM. (Hint: binary 1111 converts to BCD 1, 0101=15_{dec.}). [10]

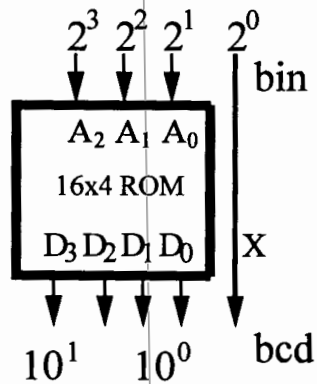

QUESTION 6

Design a PLA that implements the following set of logic functions:

$$X = abc + a\bar{b}c + \bar{a}bc + \bar{a}\bar{b}\bar{c}$$

$$Y = ab\bar{c} + a\bar{b}c + \bar{a}b\bar{c}$$

$$Z = ab\bar{c} + \bar{a}b\bar{c} + \bar{a}\bar{b}\bar{c}$$

[20]