

UNIVERSITY OF SWAZILAND

MAIN EXAMINATION 2007/2008

FACULTY OF SCIENCE

DEPARTMENT OF ELECTRONIC ENGINEERING

TITLE OF PAPER: ANALOG ELECTRONICS II

COURSE NUMBER: E442

TIME ALLOWED: THREE HOURS

INSTRUCTIONS:

- 1. Answer any FOUR (4) of the following five questions.**
- 2. Each question carries 25 marks.**

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION HAS
BEEN GIVEN BY THE INVIGILATOR**

THIS PAPER CONTAINS SIX(6) PAGES INCLUDING THIS PAGE

QUESTION 1

For the circuit in Fig. 1

- (a) Find the frequency and gain condition for oscillation to take place. [15 marks]
- (b) Select suitable components so that the circuit will oscillate at a frequency of 5 kHz. [10 marks]

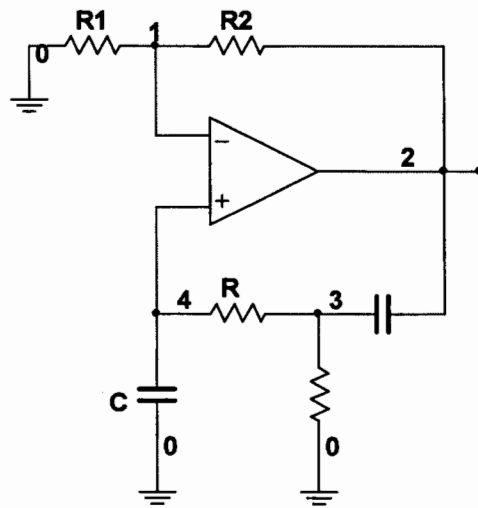


Fig. 1

QUESTION 2

(a) Given a CA3080 operational transconductance amplifier (OTA) with a supply voltage $\pm V = \pm 10$ V and an I_{ABC} of $100 \mu\text{A}$, find:

(i) the OTA transconductance g_m ;

[5 marks]

(ii) the output voltage with an input of 10 mV and a load resistor of 1 K Ω ;

[7 marks]

(iii) the I_{ABC} needed to give a 1 V output with a 120 mV input and a load resistance of 1 K Ω .

[7 marks]

For the CA3080 OTA,

$$g_m = \left(\frac{300}{V} \right) (I_{ABC})$$

(b) What is the purpose of input diode linearization in the internal circuit of an OTA?

[6 marks]

QUESTION 3

- (a) An analog signal in the range 0 to +5 V is to be converted to a 12-bit digital signal.
- (i) What is the resolution of the conversion in volts?
 - (ii) What is the digital representation of an input of 3.25 V?
 - (iii) What is the error made in the conversion of 3.25 V in absolute terms and as a percentage of the input?
 - (iv) What is the largest possible quantization error as a percentage of full scale?
[20 marks]
- (b) What is the maximum resistor ratio required by an 8-bit DAC utilizing a binary-weighted resistor network?
[5 marks]

QUESTION 4

- (a) The full-bridge converter shown in Fig. Q4a is fed with an input voltage of 230 V at 50 Hz. The thyristors are triggered at a firing angle of 70° . If $R = 56 \Omega$, find the average current through R.

[12 marks]

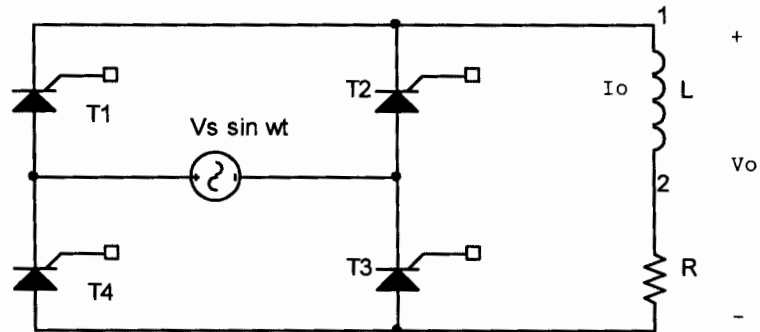


Fig. Q4a

- (b) In Fig. Q4b, the diac has a breakover voltage of 32 V and an ON voltage of 1 V. If the triac has a trigger voltage of 0.7 V, what is the current through the $1.5 \text{ k}\Omega$ resistor just after the diac breaks over?

[13 marks]

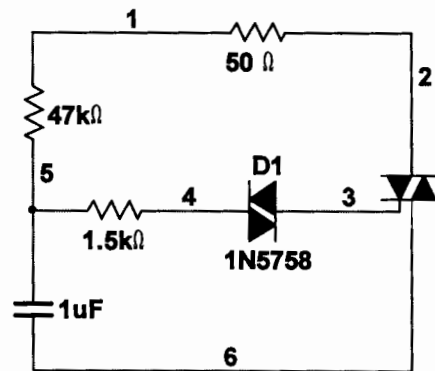


Fig. Q.4b

QUESTION 5

In Fig. Q5, the wiper is at the middle of its range. Assume $V_{BE} = 0.7 \text{ V}$ for all transistors.

- What is the output voltage of the regulator?
- What is the load current when current limiting starts?
- What is the minimum load resistance where regulation is lost?
- What is the power dissipation of the pass transistor when the load resistor is shorted?

[25 marks]

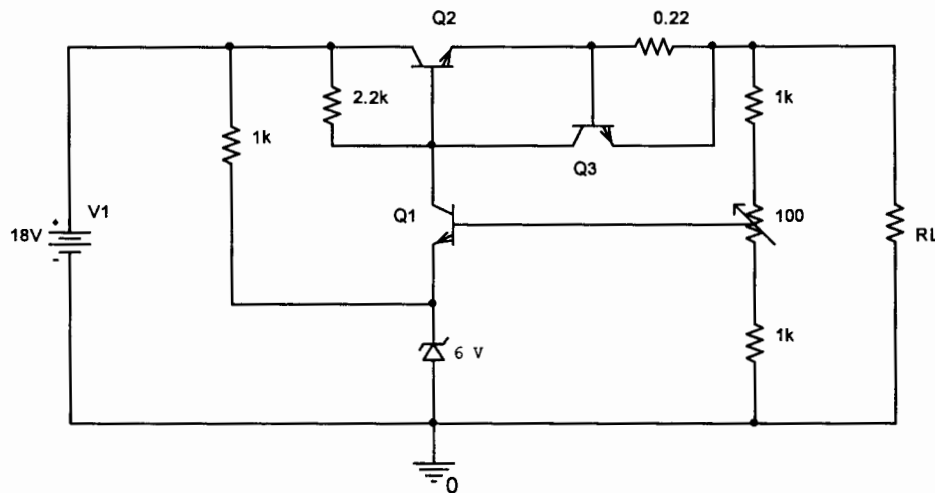


Fig. Q5