

UNIVERSITY OF SWAZILAND
FIRST SEMESTER EXAMINATION DECEMBER, 2008

FACULTY OF SCIENCE

DEPARTMENT OF ELECTRONIC ENGINEERING

| | |
|------------------------|----------------------------|
| TITLE OF PAPER: | ELECTRICAL CIRCUITS |
| COURSE CODE: | E310 |
| TIME ALLOWED: | THREE HOURS |

INSTRUCTIONS:

- 1. Answer any FIVE (5) of the following SIX questions.**
- 2. Each question carries 20 marks.**
- 3. Calculators capable of solving simultaneous equations with three variables may be used.**
- 4. If you think not enough data has been given in any question you may assume reasonable values**

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION
HAS BEEN GIVEN BY THE INVIGILATOR**

THIS PAPER CONTAINS EIGHT (8) PAGES INCLUDING THIS PAGE

QUESTION ONE (20 marks)

- (a) Find the voltage V_X and current I_X in the circuit shown in Fig.Q1a. (8 marks)

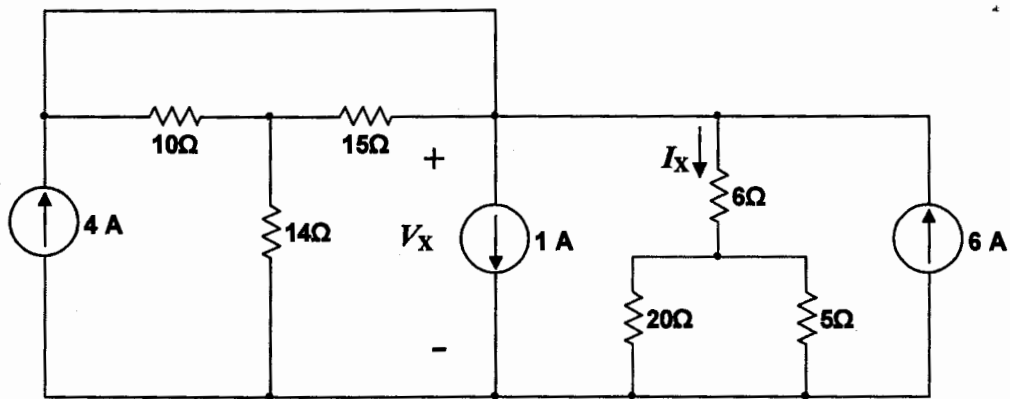


Fig.Q1a

- (b) In the circuit shown in Fig.Q1b which features a voltage-dependent voltage source, find the voltage at Node A and the voltage V_X . (12 marks)

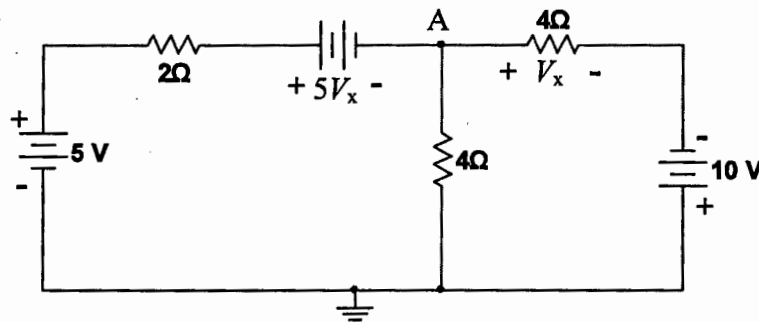


Fig. Q1b

QUESTION TWO (20 marks)

For the circuit shown in Fig. Q2,

- (a) Find the Thevenin's equivalent circuit looking into the circuit from terminals A and B. (16 marks)
- (b) Hence obtain the values of the passive components that could be used to represent the Thevenin equivalent circuit. (4 marks)

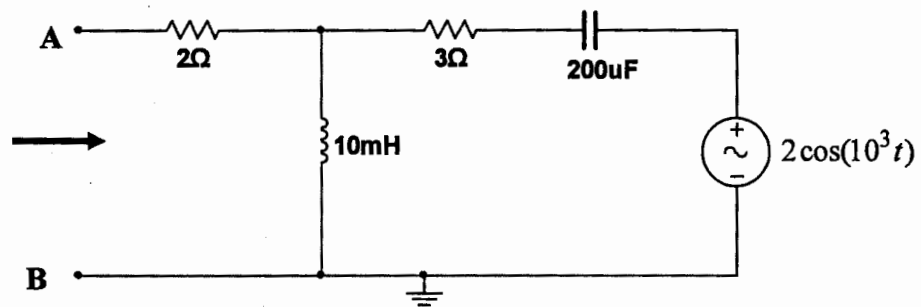


Fig.Q2

QUESTION THREE (20 marks)

An a.c. voltage source $e(t) = 25 \sin(314t + 45^\circ)$ supplies an inductive load whose impedance at the working frequency is $Z_L = 10 + j5 \Omega$. Determine:

- (a) An expression for the instantaneous power at any time t . Simplify your expression as much as possible. (11 marks)
- (b) The apparent power delivered to Z_L . (3 marks)
- (c) The reactive power delivered to Z_L . (3 marks)
- (d) The average power delivered to Z_L . (3 marks)

QUESTION FOUR (20 marks)

(a) For the circuit shown in Fig.Q4a find:

(i) The value of Z_L for maximum power to be delivered to it. (10 marks)

(ii) The average power dissipated by Z_L when maximum power is delivered. (3 marks)

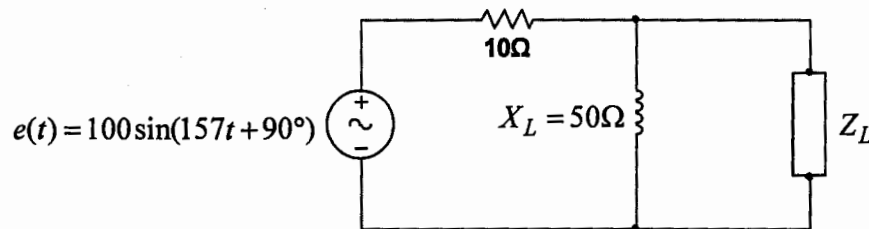


Fig.Q4a

(b) Given a circuit with applied voltage of $v = 150 \sin(\omega t + 10^\circ)$ and current of

$i = 5 \sin(\omega t - 50^\circ)$. Determine

(i) The average power (2 marks)

(ii) The reactive power (2 marks)


(iii) The apparent power (1 mark)

(iv) The power factor (2 marks)

QUESTION FIVE (20 marks)


Assume that the switch S in Fig.Q5 has been open for a long time. At time $t = 0$ it is closed.

- (a) Obtain equations for $v_C(t)$ and $i(t)$ and sketch them. (16 marks)
- (b) Use your equations to evaluate $v_C(t)$ and $i(t)$ at the instant when the capacitor voltage is 9 V. (4 marks)

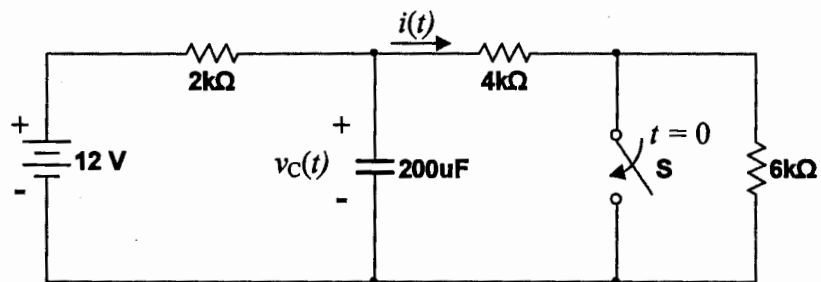**Fig.Q5**

QUESTION SIX (20 marks)

Using mesh analysis or otherwise find the voltages at nodes A, B, C and D in the circuit shown in Fig.Q6.

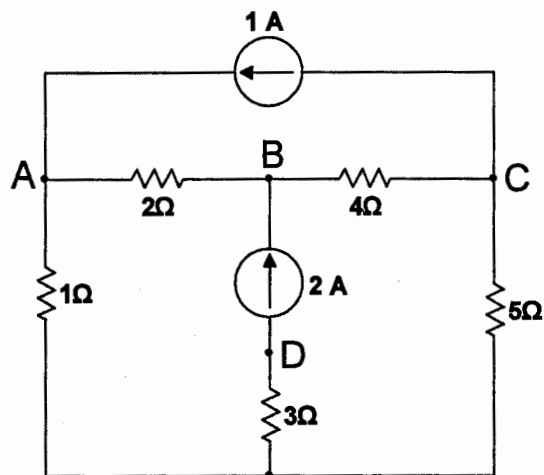**Fig.Q6**

QUESTION SEVEN (20 marks)

- (a) For the circuit shown in Fig.Q7a, find the current in the $4\ \Omega$ resistor. (10 marks)

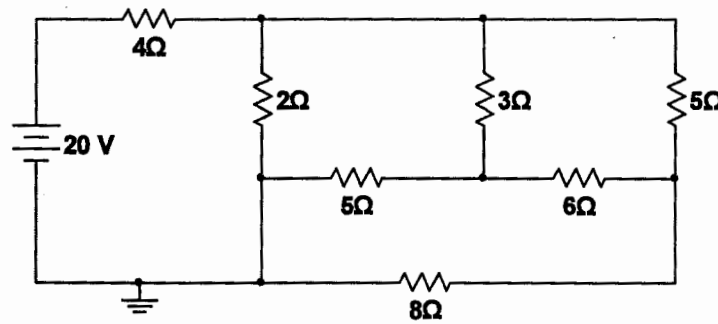


Fig. Q.7a

- (b) Three loads each of resistance $3\ \Omega$ and inductive reactance $4\ \Omega$ in series are connected in star. Find the equivalent loads connected in delta that would represent the star-connected loads. (10 marks)