

UNIVERSITY OF SWAZILAND
MAIN EXAMINATION, SECOND SEMESTER MAY 2009

FACULTY OF SCIENCE

**DEPARTMENT OF ELECTRICAL AND ELECTRONIC
ENGINEERING**

TITLE OF PAPER: ANALOGUE ELECTRONICS II

COURSE CODE: E442

TIME ALLOWED: THREE HOURS

INSTRUCTIONS:

- 1. There are six questions in this paper. Answer any FIVE questions. Each question carries 20 marks.**
- 2. If you think not enough data has been given in any question you may assume any reasonable values.**
- 3. Show all your steps clearly in any calculations.**

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION
HAS BEEN GIVEN BY THE INVIGILATOR**

THIS PAPER CONTAINS SEVEN (7) PAGES INCLUDING THIS PAGE

QUESTION ONE (20 marks)

Consider the Schmitt trigger circuit shown in Fig. Q1.

- (a) Defining any symbols you use, derive general equations for the triggering thresholds of the circuit. (10 marks)

- (b) If $V_{ref} = 3\text{ V}$, $R_2 = 2R_1 = 20\text{ k}\Omega$ and the opamp saturates at $\pm 12\text{ V}$ evaluate the thresholds and sketch the voltage transfer characteristic (v_o vs v_{in}).

(10 marks)

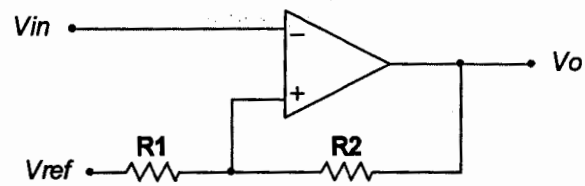


Fig. Q1

QUESTION TWO (20 marks)

A circuit of a Wien bridge oscillator is shown in Fig. Q2.

- (a) Derive the conditions required for sustained oscillations. (10 marks)
- (b) Given that $R_1 = 120 \text{ k}\Omega$, $R_2 = 12 \text{ k}\Omega$, $C_1 = 10 \text{ nF}$, $C_2 = 100 \text{ nF}$, find:
- (i) The frequency of oscillation. (5 marks)
- (ii) Suitable values of R_3 and R_4 for sustained oscillations to occur. (5 marks)


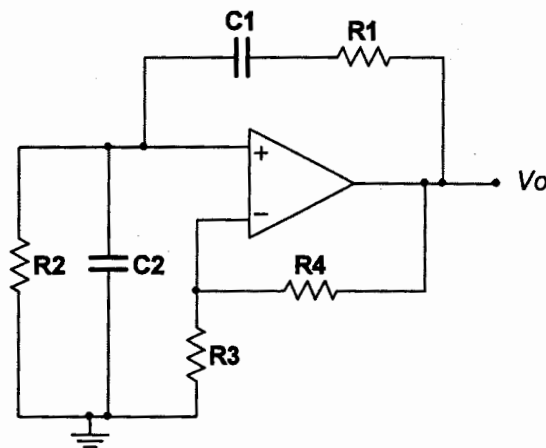


Fig. Q2

QUESTION THREE (20 marks)

Figure Q3 shows a circuit of a simple FET-based Colpitts oscillator.

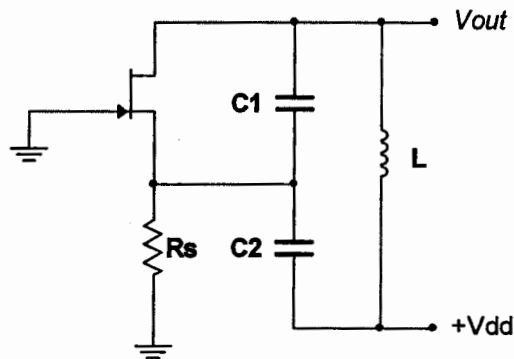- (a) Draw its equivalent circuit and derive expressions for
- The oscillating frequency. (10 marks)
 - The voltage gain required to maintain steady oscillations in the circuit. (5 marks)
- (b) If $C_1 = 100 \text{ pF}$ and $C_2 = 1000 \text{ pF}$, calculate value of the inductance L and the minimum voltage gain required to maintain steady oscillation at a frequency of 10 MHz.



(5 marks)

Fig. Q3

QUESTION FOUR (20 marks)

a) Define the following terms as used regulated power supplies:

- i. Regulation;
- ii. Ripple factor;
- iii. Peak Inverse Voltage and
- iv. Transformer utilization factor.

[4]

b) Prove that:

- i. The ripple factor of a half-wave rectified signal is approximately = 1.21
- ii. The ripple factor of a full-wave rectified signal is approximately = 0.483

[8]


c) Design a power supply with the following specifications:

- Average value of load voltage = 20V;
- Maximum value of load current = 100mA;
- With a ripple factor not exceeding 0.01;
- Voltage regulation of 2.5%, and
- The power line frequency of 50Hz.

[8]

QUESTION FIVE (20 marks)

- a) The figure 1 below shows a simple series regulator. Describe and explain how this circuit works.

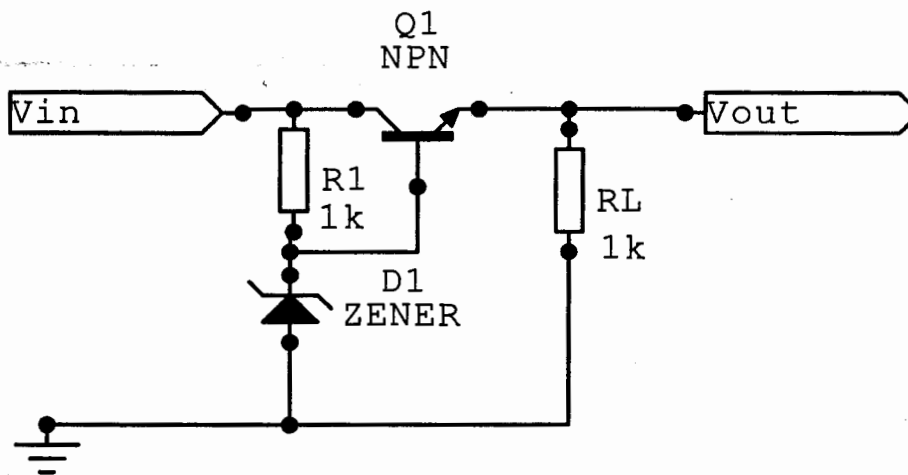**Fig. 1****[6]**

- b) Design a switching regulator with the following specifications:

Average value of load voltage = 5V;

Average value of load current = 1A;

Switching frequency at full load = 25 KHz;

Maximum peak to peak ripple should not exceed 0.08V, and

Unregulated supply is = 25V.

[14]

QUESTION SIX (20 marks)

- a) With the aid of relevant diagram(s), describe the principles of operation of a binary weighted resistor DAC (digital to analogue converter). Given that a three-bit binary weighted resistor DAC has $R = 2 \text{ k}\Omega$ with a reference voltage of 10V.

What would the output voltage be;

- (i) if all switches were set to logic 1?
(ii) if only the least significant bit switch is at logic 1?

[6]

- b) With the aid of relevant diagram(s), describe the principles of operation of the R-2R ladder DAC (digital to analogue converter). Given that, the reference voltage is 10V, calculate the output voltage of a three-bit R-2R ladder network if $S_0 = 1$, $S_1 = 0$ and $S_2 = 1$.

[6]

- c) With the aid of relevant diagram(s), describe the principles of operation of a three-bit parallel (flash) comparator ADC (analogue to digital converter). Show clearly the encoding tables for the ADC circuit.

[8]