

UNIVERSITY OF SWAZILAND
MAIN EXAMINATION, SECOND SEMESTER MAY 2009

FACULTY OF SCIENCE

**DEPARTMENT OF ELECTRICAL AND ELECTRONIC
ENGINEERING**

TITLE OF PAPER: ANALOGUE ELECTRONICS IV

COURSE CODE: E512

TIME ALLOWED: THREE HOURS

INSTRUCTIONS:


- 1. There are six questions in this paper. Answer any FOUR questions.
Each question carries 25 marks.**
- 2. Unless otherwise stated, $V_{BE(ON)} = 0.7 \text{ V}$ and $V_T = 0.025 \text{ V}$.**
- 3. If you think not enough data has been given in any question you may assume any reasonable values.**
- 4. A sheet containing some useful equations is attached at the end of this examination paper.**
- 5. Calculators capable of doing multiplication and division of complex numbers may be used.**

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION
HAS BEEN GIVEN BY THE INVIGILATOR**

THIS PAPER CONTAINS EIGHT (8) PAGES INCLUDING THIS PAGE

QUESTION ONE (25 marks)

- (a) Briefly discuss the requirements for a good quality power output stage. (7 marks)
- (b) For the power output stage shown in Fig.Q1 assume that $I = 100 \text{ mA}$, $V_{CEsat} = 0.3 \text{ V}$ and $V_{CC} = 15 \text{ V}$.
- (i) For a load resistance R_L of 120Ω , determine the maximum undistorted input signal that can be applied to the input and calculate the power conversion efficiency under this condition. Note that the power dissipation in Q3 and R is not negligible. (10 marks)
- (ii) Determine a value of R_L which gives maximum efficiency. (4 marks)
- (iii) Hence evaluate the maximum efficiency of the circuit. (4 marks)

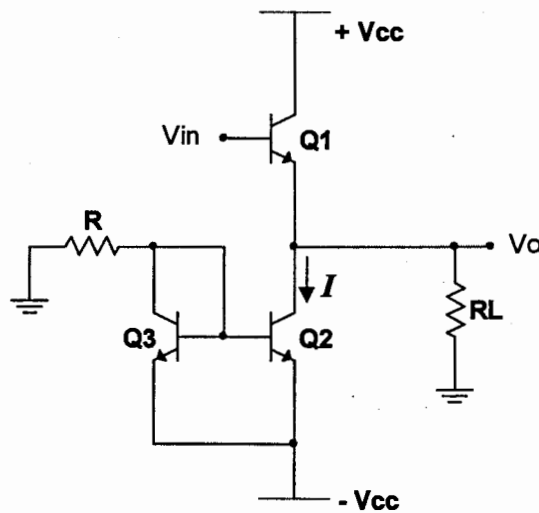**Fig Q1**

QUESTION TWO (25 marks)

You are required to design the biasing circuit for the class AB output stage shown in Fig. Q2.

The following relevant data are given:

$$I_{C1} = I_{C2} = 0.6 \text{ mA under quiescent conditions.}$$

Q_1, Q_2, Q_3 and Q_4 are similar but Q_1, Q_2 have 3 times the junction areas of Q_3, Q_4 .

$$I_S = 10^{-12} \text{ mA for } Q_3, Q_4.$$

$$V_{CC} = 20 \text{ V.}$$

$$\text{Maximum load current} = 20 \text{ mA.}$$

Find:

- The required current in Q_3 and Q_4 . (5 marks)
- Determine suitable values of R_1 and R_2 that ensure that all transistors are always operating in the active region. You must verify the validity of your values under all worst case conditions. (15 marks)
- Find the quiescent power dissipation all the transistors in the circuit. (5 marks)

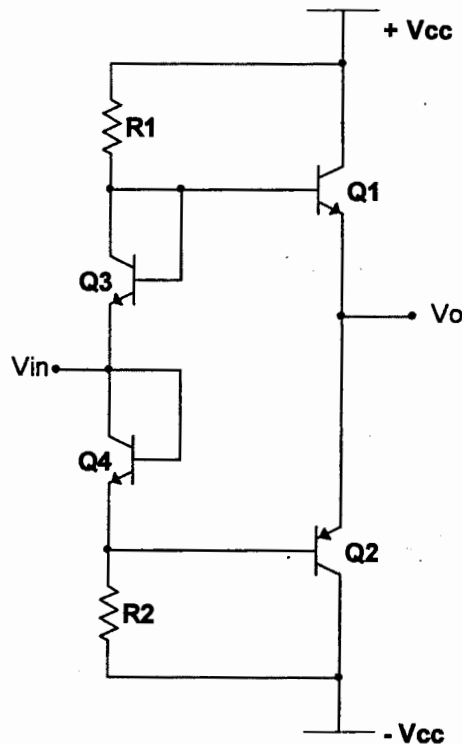


Fig. Q2

QUESTION THREE (25 marks)

- (a) With the aid of a suitable illustration briefly discuss the factors which limit the safe operating area of a bipolar junction power transistor. (5 marks)
- (b) A BJT with a maximum junction temperature of 175°C and thermal resistance $\theta_{JC} = 2.5^{\circ}\text{C/W}$ is bonded to a washer of thermal resistance $\theta_{JC} = 0.45^{\circ}\text{C/W}$. The transistor is then fixed to a heat sink of $\theta_{SA} = 1^{\circ}\text{C/W}$ per cm length. Determine the length of heat sink required for the transistor to safely dissipate 40 W of power at an ambient temperature of 40°C ? (6 marks)
- (c) The full power rating of 100 W for a given transistor is available up to 25°C and its maximum junction temperature is 150°C .
- (i) Estimate its thermal resistance. (2 marks)
- (ii) What maximum power would you allow the device to dissipate without a heat sink at an ambient temperature of 60°C . (2 marks)
- (iii) State any assumptions you have made in your calculations. (1 mark)
- (d) Two possible amplifier configurations are shown in Fig. Q.3d.
- (i) Show that both of them have equal signal gains. (5 marks)
- (ii) Compare their noise performances and comment on the practical implications of the better one of the two. (4 marks)

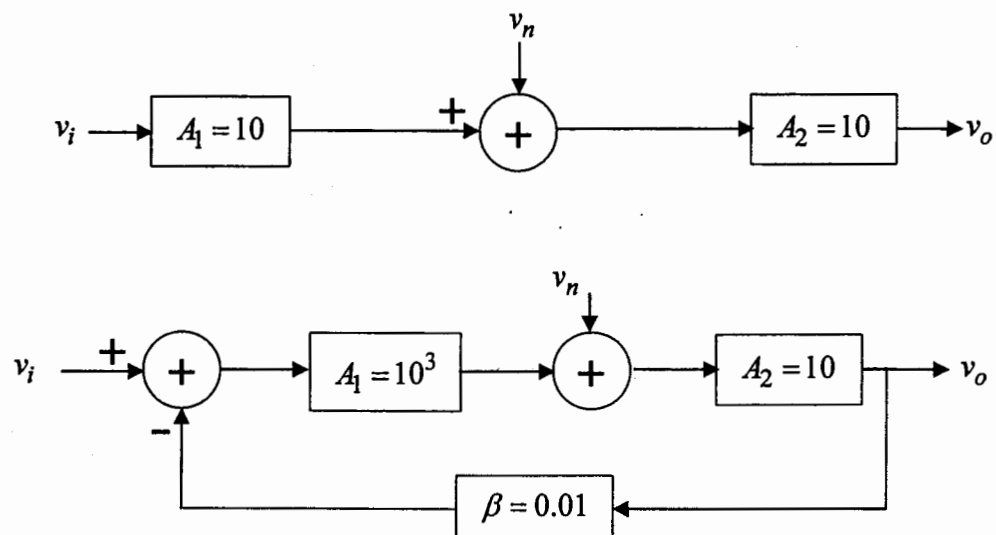


Fig. Q3d

QUESTION FOUR (25 marks)

- (a) Determine the components of a lossless L-section to match a $50\ \Omega$ source to a $75\ \Omega$ load at 400 MHz. (7 marks)
- (b) A $50\text{-}\Omega$ source is to be matched to a high frequency amplifier whose input admittance at 500 MHz is $8 - j12\ \text{mS}$. Determine the components of a lumped L-section network suitable for the match. A Smith Chart may be used. (18 marks)

QUESTION FIVE (25 marks)

The 2N5943 transistor biased at $V_{CE} = 15$ V and $I_c = 5$ mA has the following common emitter y-parameters at 300 MHz:

$$y_{11} = 25.34 + j7.05 \text{ mS}$$

$$y_{12} = 0.035 - j3.952 \text{ mS}$$

$$y_{21} = 4.378 - j142.3 \text{ mS}$$

$$y_{22} = 1.321 + j11.452 \text{ mS}$$

- (a) Determine whether the transistor is unconditionally stable or not under these bias conditions and frequency. (5 marks)
- (b) What maximum possible power gain obtainable from this transistor at these bias conditions and frequency? (5 marks)
- (c) If the device is fed from a $50\text{-}\Omega$ source and the load is $75\ \Omega$, determine:
- (i) Whether the circuit is stable under these conditions. (5 marks)
 - (ii) The expected voltage gain. (5 marks)
 - (iii) The input admittance of the circuit. (5 marks)

QUESTION SIX (25 marks)

Consider the circuit of a boost converter is shown in Fig. Q6.

- (a) With the aid of appropriate sketches explain the operation of the circuit. (9 marks)
- (b) Calculate the output voltage expected. (2 marks)
- (c) Calculate the average value of the load current. (2 marks)
- (d) Calculate the power delivered to the load. (2 marks)
- (e) Find the supply current. (2 marks)
- (f) Determine the minimum and maximum values of the inductor current. (8 marks)

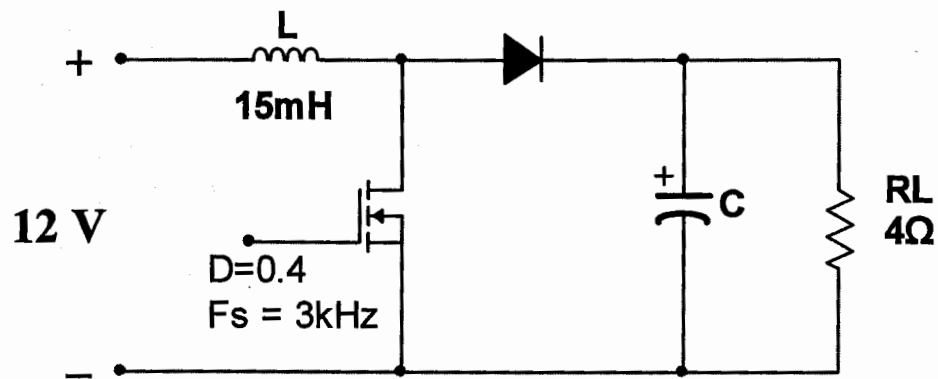


Fig. Q6

SOME RF CIRCUIT DESIGN EQUATIONS

$$C = \frac{|y_f y_r|}{2g_i g_o - \operatorname{Re}(y_f y_r)}$$

$$\text{MAG} = \frac{|y_f y_r|^2}{4g_i g_o}$$

$$K = \frac{2(g_i + G_S)(g_o + G_L)}{|y_f y_r| + \operatorname{Re}(y_f y_r)}$$

$$1 + Q^2 = \frac{R_p}{R_s} \quad \text{where} \quad Q = \frac{R_p}{X_p} = \frac{X_s}{R_s}$$