

UNIVERSITY OF SWAZILAND
MAIN EXAMINATION, SECOND SEMESTER MAY 2010

FACULTY OF SCIENCE

**DEPARTMENT OF ELECTRICAL AND ELECTRONIC
ENGINEERING**

TITLE OF PAPER: ANALOGUE ELECTRONICS II
COURSE CODE: E442

TIME ALLOWED: THREE HOURS

INSTRUCTIONS:

- 1. There are six questions in this paper. Answer any FIVE questions. Each question carries 20 marks.**
- 2. If you think not enough data has been given in any question you may assume any reasonable values.**
- 3. A sheet containing some useful equations is attached at the end of this examination paper.**

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION
HAS BEEN GIVEN BY THE INVIGILATOR**

THIS PAPER CONTAINS FOUR (4) PAGES INCLUDING THIS PAGE

- Q.1**
- a) What is the Barkhausen Criterion and why is it required? (2 marks)
 - b) For Hartley oscillator, determine the value of total inductance L_T and mutual inductance M , when it is operating at a frequency of 10 kHz with $C = 10$ nF, and $L_1 = L_2 = 4$ mH. (7 marks)
 - c) For the Wien bridge oscillator, determine the value of resistance R required for it to operate at a frequency of 1 kHz with $C = 0.1$ μ F. What is the condition required to sustain oscillations? (5 marks)
 - d) What is the advantage of a Crystal oscillator? Explain its operation with suitable diagrams. (6 marks)
- Q.2**
- a) What is the advantage and disadvantage of a Dual-Slope A/D converter? Explain its operation with neat diagrams. (8 marks)
 - b) Determine the number of counts for dual slope ADC, when $V_{ref} = -1$ V and $V_{in} = 2$ V and fixed counts = 1000. (2 marks)
 - c) With the aid of a relevant diagram, describe the principles of operation of the 4-bit binary R-2R ladder DAC. (5 marks)
 - d) Determine the out put voltage and resolution for an 8-bit DAC (R-2R network) when the input data is 10010101, and reference voltage is 10 V. (5 marks)

- Q.3 a)** For a series voltage regulator employing a series pass transistor
- Define voltage regulation, (1 mark)
 - With the aid of suitable diagrams, explain its working principle. (6 marks)
 - Determine the value of feed back resistance R_F required to obtain a constant output voltage 10V when the zener voltage is 5 V and $R_1 = 10 \text{ k}\Omega$.
Determine also the voltage gain? (3 marks)
- b)** In the circuit of Fig.Q.3b, which employs a fixed voltage 5V regulator LM340K-5, V_{in} varies from 15 to 20 V, $I_Q = 4 \text{ mA}$, $R_1 = 2 \text{ k}\Omega$, and R_2 is a 1-k Ω variable resistance.
- Calculate V_{out} when $R_2 = 1 \text{ k}\Omega$. (2 marks)
 - Calculate V_{out} when $R_2 = 500 \Omega$. (2 marks)
 - Find the maximum power that the regulator chip dissipates assuming the load draws up to 200 mA of current. (3 marks)

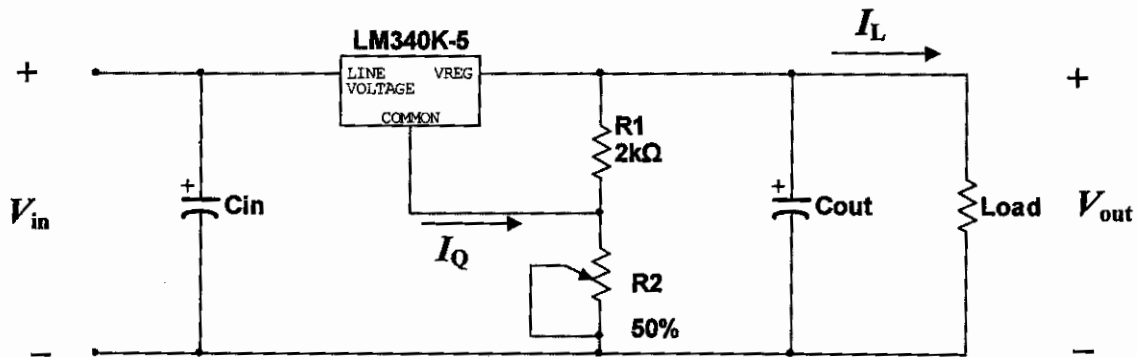


Fig. Q.3b

- c)** What is the advantage of SMPS over series voltage regulator and explain briefly (3 marks)
- Q.4 a)** Sketch and clearly label the output and transfer characteristics of an IGBT. (5 marks)
- b)** Describe the characteristics of an SCR and explain one of its applications. (10 marks)
- c)** Sketch and clearly label the output and transfer characteristics of an enhancement MOSFET. (5 marks)

- Q.5** (a) Define the slew rate of an opamp. How does it limit the operation of an opamp used in linear applications and in non-linear applications? (8 marks)
- (b) Design a simple opamp based function generator to generate a square wave and a triangular wave of 1 kHz. State any assumptions you make. (12 marks)

Q.6 Consider the circuit shown in Fig. Q.6 and answer the following questions.

- (a) Derive expressions for the two threshold voltages for positive going signals and negative going signals. (8 marks)
- (b) If $V_{\text{ref}} = 2\text{V}$, $R_1 = 10\text{ k}\Omega$, $R_2 = 250\ \Omega$, and $V_{\text{omax}} = \pm V_{\text{sat}} = \pm 12\text{ V}$, evaluate the threshold voltages. (6 marks)
- (c) Sketch and clearly label the voltage transfer characteristic, v_o vs v_{in} based on the values given in (b). (3 marks)
- (d) If $v_{\text{in}} = 3 \sin(2\pi \cdot 10^3 \cdot t)$ V and components values are as given in (b), sketch v_{in} and v_o versus t on the same time axis. (3 marks)

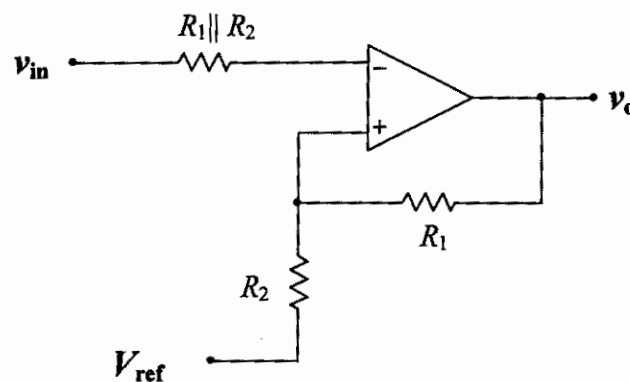


Fig. Q.6