

**UNIVERSITY OF SWAZILAND**  
**MAIN EXAMINATION, SECOND SEMESTER MAY 2010**

**FACULTY OF SCIENCE**

**DEPARTMENT OF ELECTRICAL AND ELECTRONIC  
ENGINEERING**

**TITLE OF PAPER: ANALOGUE ELECTRONICS IV**  
**COURSE CODE: E512**

**TIME ALLOWED: THREE HOURS**

**INSTRUCTIONS:**

- 1. There are five questions in this paper. Answer any FOUR questions.  
Each question carries 25 marks.**
- 2. If you think not enough data has been given in any question you may  
assume any reasonable values.**

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION  
HAS BEEN GIVEN BY THE INVIGILATOR**

**THIS PAPER CONTAINS SIX (6) PAGES INCLUDING THIS PAGE**

**QUESTION ONE (25 marks)**

(a) Figure Q.1a shows a class A emitter follower biased with a constant current source.

Assume that  $\beta = \infty$ ,  $V_{BE} = 0.7 \text{ V}$  and  $V_{CEsat} = 0.3 \text{ V}$ .

- (i) Find the value of  $R$  that will produce maximum out signal swing. (7 marks)
- (ii) Find the minimum and maximum values of the emitter current of  $Q_1$ . (2 marks)
- (iii) Calculate the power conversion efficiency of the circuit at maximum output voltage swing. (6 marks)

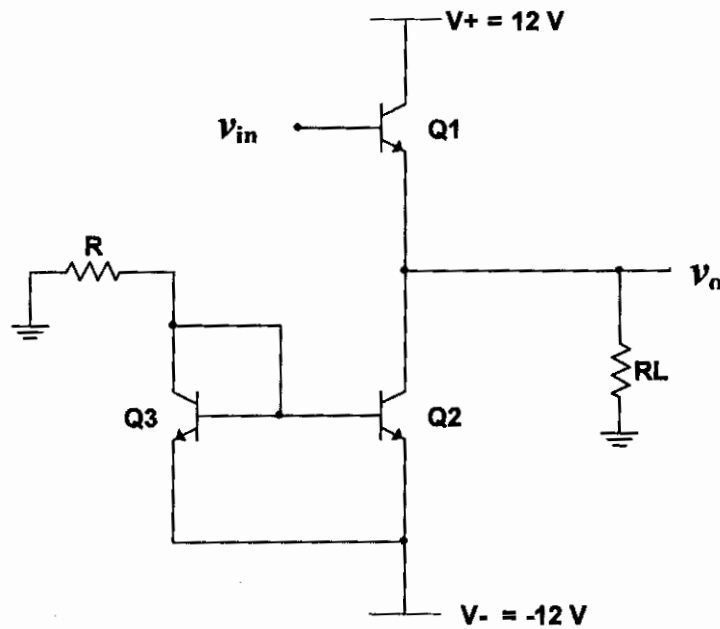


Fig. Q.1a

(b) With the aid of an illustration briefly discuss the Safe Operating Area of a Power BJT.

How does this area differ from that of a power MOSFET?

(10 marks)

**QUESTION TWO (25 marks)**

(a) Consider the class B output stage with complementary MOSFETs shown in Fig. Q.2a.

The MOSFET parameters are:

$$V_{tp} = V_{tn} = 0\text{V}, \quad \frac{1}{2}k'_n \frac{W}{L} = \frac{1}{2}k'_p \frac{W}{L} = 0.2 \text{ mA/V}^2$$

$$i_D = \frac{1}{2}k' \frac{W}{L} (V_{GS} - V_t)^2 \text{ in saturation region.}$$

$$i_D = k' \frac{W}{L} \left[ (v_{GS} - V_t)v_{DS} - \frac{1}{2}v_{DS}^2 \right] \text{ in triode region}$$

(i) At what voltage  $v_{GS}$ , does the NMOSFET just enter saturation? (1 mark)

(ii) Find the maximum output voltage with  $Q_n$  remaining in saturation region. (9 marks)

(iii) Find the values of  $i_L$  and  $v_{in}$  for maximum output voltage. (2 marks)

(iv) Find the power conversion efficiency for a sinewave of maximum peak-to-peak value. (5 marks)

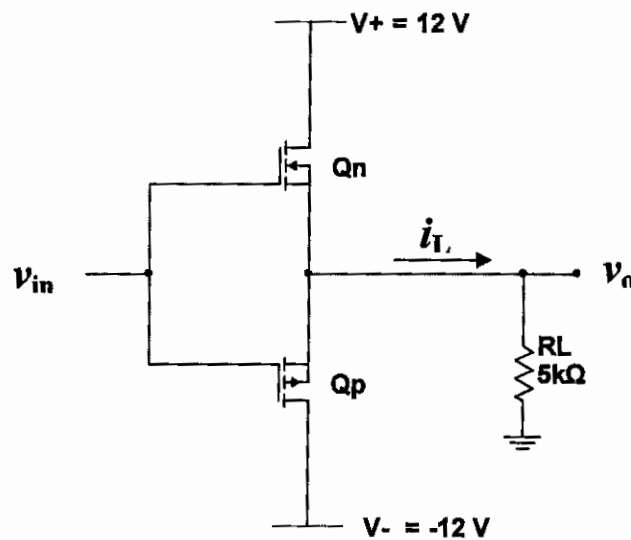


Fig. Q2a

(b) A power MOSFET is used at an ambient temperature of  $30^\circ\text{C}$ . The specifications of the MOSFET are  $T_{J\max} = 175^\circ\text{C}$ ,  $\theta_{JC} = 1.8^\circ\text{C/W}$  and  $\theta_{CA} = 50^\circ\text{C/W}$ .

(i) What maximum power dissipation should be allowed for the MOSFET under this condition? (2 marks)

(ii) If the MOSFET is mounted on a heatsink with  $\theta_{CS} = 1.2^\circ\text{C/W}$  and  $\theta_{SA} = 4^\circ\text{C/W}$ , by what factor can the dissipation of the MOSFET be increased? (3 marks)

(iii) What will be the temperature of the heatsink in (ii) when the MOSFET is dissipating maximum allowable power? (3 marks)

**QUESTION THREE (25 marks)**

(a) Figure Q.3a shows a class AB amplifier stage. For the diodes  $I_S = 2 \times 10^{-14}$  A and for the transistors  $I_S = 5 \times 10^{-14}$  A.

(i) Calculate  $V_{BB}$ ,  $i_{e1}$  and  $i_{e2}$  when  $v_{in} = 0$ . (9 marks)

(ii) Calculate  $V_{BB}$ ,  $i_{e1}$  and  $v_o$  when  $v_{in} = +5$  V (6 marks)

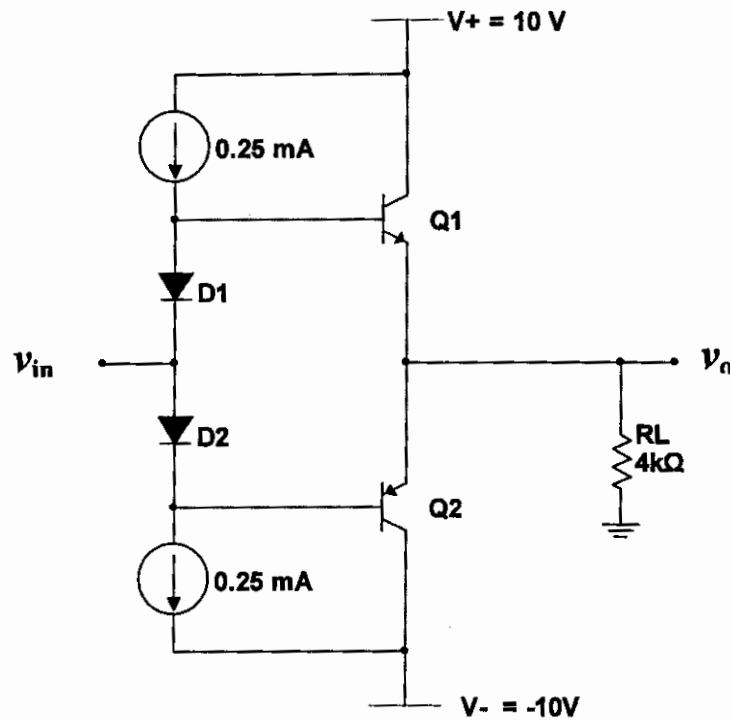


Fig. Q.3a

(b) Design a  $V_{BE}$  multiplier to be used in a class AB push-pull output stage to give  $V_{BB} = 1.157$  V. The transistor used has  $I_S = 10^{-14}$  A,  $\beta = \infty$  and  $I_C = 0.9I_{BIAS}$  where  $I_{BIAS}$  is a constant current source of  $180 \mu\text{A}$  supplying the  $V_{BE}$  multiplier. (10 marks)

**QUESTION FOUR (25 marks)**

A 500-MHz source of 500- $\Omega$  source impedance is to be matched to a 10- $\Omega$  load using a lossless network.

- (a) Using the Q-method design a d.c. blocking L-section matching network. (10 marks)
- (b) Using a virtual (intermediate) resistance equal to the geometric mean of the source and load impedances, design a double L-section matching network. (15 marks)

**QUESTION FIVE (25 marks)**

An RF transistor with proper bias point has the following common emitter S-parameters:

$$S_{11} = 0.6 \angle 56^\circ$$

$$S_{12} = 0.09 \angle 70^\circ$$

$$S_{21} = 4.4 \angle 75^\circ$$

$$S_{22} = 0.11 \angle -164^\circ$$

- (a) Test the device for stability at this operating point. (8 marks)
- (b) Find the Maximum Available Gain, MAG, expected when narrowband conjugate matching is employed. (2 marks)
- (c) If the source and load impedances are both 50  $\Omega$ , and the reverse transmission coefficient is neglected, give a complete simple design of the RF amplifier for a narrow band match at 1 GHz. A Smith Chart may be used. (15 marks)

**SOME SELECTED USEFUL RF DESIGN FORMULAE**

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|^2}$$

$$\text{where } |\Delta| = |S_{11}S_{22} - S_{12}S_{21}|$$

$$\text{MAG} = 10 \log \left| \frac{S_{21}}{S_{12}} \right| + 10 \log \left| K - \text{sgn}(B_1) \sqrt{K^2 - 1} \right| \text{ dB}$$

$$\text{where } B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2$$