

UNIVERSITY OF SWAZILAND

MAIN EXAMINATION - SEMESTER I NOV/DEC 2010

FACULTY OF SCIENCE

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

TITLE OF THE PAPER: ANALOG ELECTRONICS III

COURSE CODE: E511

TIME ALLOWED: 3 HOURS

INSTRUCTIONS:

- 1. THERE ARE SIX QUESTIONS IN THIS PAPER. ANSWER ANY FIVE OF THEM. EACH QUESTION CARRIES 20 MARKS**
- 2. IF YOU THINK NOT ENOUGH DATA HAS BEEN GIVEN IN THE QUESTION YOU MAY ASSUME ANY REASONABLE VALUES.**

**THIS PAPER SHOULD NOT BE OPE UNTIL
PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR**

THIS PAPER CONTAINS SIX PAGES INCLUDING THIS PAGE.

Q 1

- A) What is the tunneling phenomenon? Draw the I-V characteristics and energy band diagrams of a tunnel diode. Mention some applications of a tunnel diode.

10 Marks

- B) Discuss Opto couplers and isolators. What are they used for in practice?

6 marks

- C) What is the significance of CMRR in opamps? An opamp has a CMRR of 1000.

One set of signals $v_1 = +60 \mu\text{V}$, $v_2 = -60 \mu\text{V}$ and another set $v_1 = 1060 \mu\text{V}$, $v_2 =$

$940 \mu\text{V}$ are applied separately to its input. By what factor does the output

voltage change for the two sets of input signals?

4 Marks

Q 2

- A) A MOSFET has a drain circuit resistance $R_d = 100 \text{ k}\Omega$ and operates at 25 kHz.

Calculate the voltage gain of this device as a single stage and then as the first transistor in a cascade consisting of two identical stages and determine the value of C_i . The MOSFET parameters are:

$$g_m = 1.6 \text{ mA/V}, r_d = 45 \text{ k}\Omega, C_{gs} = 3.0 \text{ pF}, C_{ds} = 1.0 \text{ pF}, \text{ and } C_{gd} = 2.8 \text{ pF}.$$

14 marks

- B) The amplifier of Fig. 2B, utilizes an n-channel FET for which $V_p = -2 \text{ V}$ and $I_{DSS} = 1.7 \text{ mA}$. It is required to bias the circuit at $I_D = 0.9 \text{ mA}$, using $V_{DD} = 24 \text{ V}$. Assume $r_D \geq R_d$. Find V_{GS} , g_m , R_s , and R_d , such that the voltage gain is at least 20 db, with R_s bypassed with a very large capacitance C_s .

6 marks

 


Figure 2 B Source self bias circuit

Q 3

- A) Name the two basic types of photodetector diodes. With the aid of a suitable diagram explain the operation of any one of them. **4 marks**
- B) Determine the cutoff frequency and wavelength for InGaAsP, given that photon energy $E_{ph} = E_g = 0.89$ eV, and Plank's constant $h = 6.626 \times 10^{-34}$. **4 marks**
- C) Sketch the circuit diagrams of CMOS and TTL NAND and NOR logic gates and explain their operation. **7 marks**
- D) For the circuit shown in Fig. Q.3D derive, giving explanations, the Boolean expression for the output Q in terms of the logic inputs variables X_1 and X_2 . **5 marks**

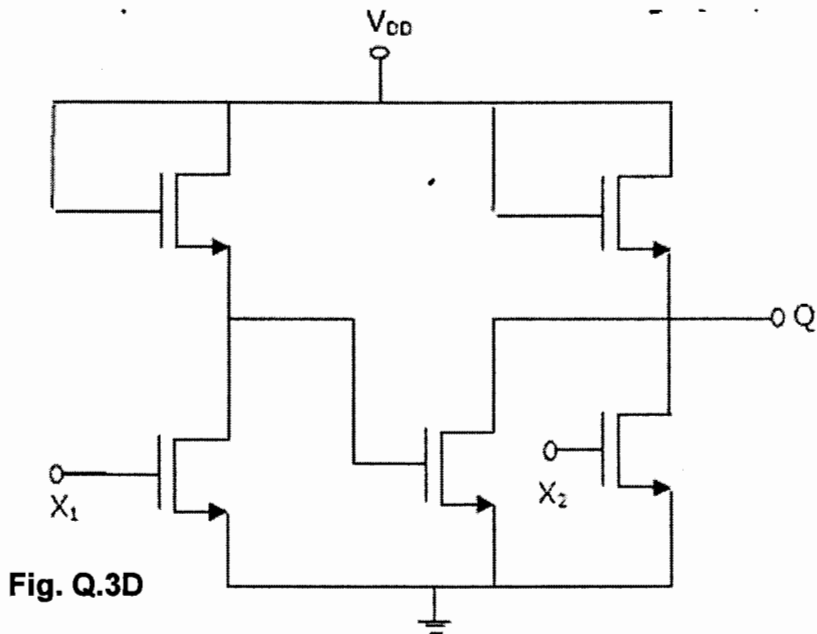


Fig. Q.3D

Q 4

- A) For the circuit of Fig. Q4 A determine the value of resistance R_2 to provide constant current $I=10\text{ mA}$ in the load, when $V_z=6\text{V}$ and supply voltage $V = 12\text{ V}$ and give some applications. 6 marks


 


Figure Q4.A

- B) Draw the circuit diagram of a basic BJT current mirror. Derive an exact equation relating the two currents being mirrored. What is the effect of the Early Voltage on the expression you have derived? **6 marks**
- C) For a Darlington Emitter follower circuit, determine the input resistance, the current gain and the voltage gain of the overall circuit. The transistors used are identical with parameters: $R_e = 4 \text{ k}\Omega$, $h_{fe} = 50$, $h_{ie} = 1100 \text{ k}\Omega$, $h_{oe} = 24 \text{ }\mu\text{A/V}$. **8 marks**

Q 5

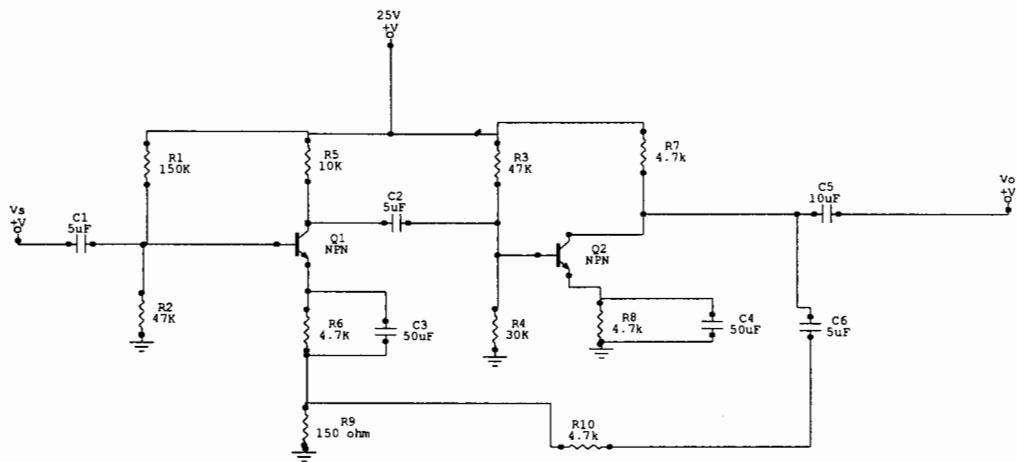- A) An amplifier is given with a voltage gain of $A_v = 10$. An engineer manages, with suitable feedback connection to raise the voltage gain to $A_v = 100$. Is the connection used a positive or a negative feedback? How much is the loop gain of this connection? Explain your answer. **3 marks**
- B) An opamp has the following parameters: $A_{VOL} = 2 \times 10^5$, $r_{in} = 2 \text{ M}\Omega$ and $r_o = 75 \text{ }\Omega$. Design an inverting voltage amplifier with an input resistance of at least $1 \text{ k}\Omega$ and output resistance of less than $0.01 \text{ }\Omega$. You may make any reasonable assumptions in your design.
- What would be the largest gain obtainable with these specifications? Justify your answer. **9 marks**
- C) For the circuit shown Fig. 5C, calculate A_{VF} , R_{OF} , and R_{IF} , assume $R_s = 0$, $h_{fe} = 50$, $h_{ie} = 1.1 \text{ K}$, $h_{re} = h_{oe} = 0$, and identical transistors. **8 marks**



1/2

Figure Q.5C Second collector to first emitter feed back pair.

Q 6

- A) Why CMOS technology is preferred to design ICs? **2 marks**
- B) What are the steps involved in fabricating a monolithic integrated circuit, explain briefly with neat diagrams. **10 marks**
- C) Mention different types of CCDs and how charges can be stored and transferred between potential wells? Explain with suitable diagrams

8 marks