

**UNIVERSITY OF SWAZILAND**  
**MAIN EXAMINATION – SEMESTER II MAY 2011**  
**FACULTY OF SCIENCE**  
**DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING**

**TITLE OF THE PAPER: ANALOG ELECTRONICS IV**

**COURSE CODE: E512**

**TIME ALLOWED: 3 HOURS**

**INSTRUCTIONS:**

1. Answer any FOUR (4) of the six questions. Each question carries 25 marks.
2. If you think not enough data has been given in any question you may assume any reasonable values.
3. A sheet with useful RF design formulae is attached at the end of the paper.
4. Impedance-Admittance (Z-Y) Smith Charts are provided.

**THIS PAPER SHOULD NOT BE OPENED UNTIL  
PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR**

**THIS PAPER CONTAINS NINE (9) PAGES INCLUDING THIS PAGE.**

**QUESTION ONE (25 Marks)**

- (a) (i) What are the requirements of a good quality audio power amplifier output stage?  
(2 marks)
- (ii) Does a common-emitter stage meet the requirements you have mentioned in (i)?  
Briefly discuss your answer. (3 marks)
- (b) A power BJT is specified to have  $T_{Jmax} = 175^{\circ}\text{C}$  and  $P_{Dmax} = 130\text{ W}$  for  $T_C \leq 25^{\circ}\text{C}$ . For  $T_C \geq 25^{\circ}\text{C}$ ,  $\theta_{JC} = 1.2^{\circ}\text{C/W}$ . The device is required to dissipate 60 W while operating at an ambient temperature of  $25^{\circ}\text{C}$ .
- (i) Find the thermal resistance of a suitable heat sink that must be used assuming that  $\theta_{CS} = 0.5^{\circ}\text{C/W}$ . (4 marks)
- (ii) Determine the case temperature of the BJT. (2 marks)
- (c) Consider the emitter follower output stage shown in Fig. Q.1c.
- (i) Explain why there are two limits for the negative swing of the output voltage. (4 marks)
- (ii) With a sinusoidal input signal the circuit is required to deliver 2W into a  $100\text{-}\Omega$  load resistance  $R_L$ . Design the circuit specifying appropriate supply voltages and resistor R. You may neglect transistor saturation voltages in your design. (6 marks)
- (iii) Calculate the power conversion efficiency of the circuit designed in (ii) when delivering its rated output power. (4 marks)

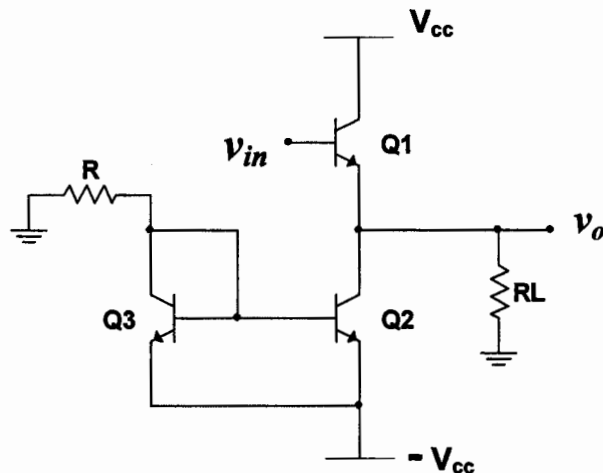


Fig. Q.1c

**QUESTION TWO (25 Marks)**

A circuit of a Class AB amplifier output stage is shown in Fig. Q.2. Assume that transistors  $Q_1$  and  $Q_2$  are matched, as are  $Q_3$  and  $Q_4$ .

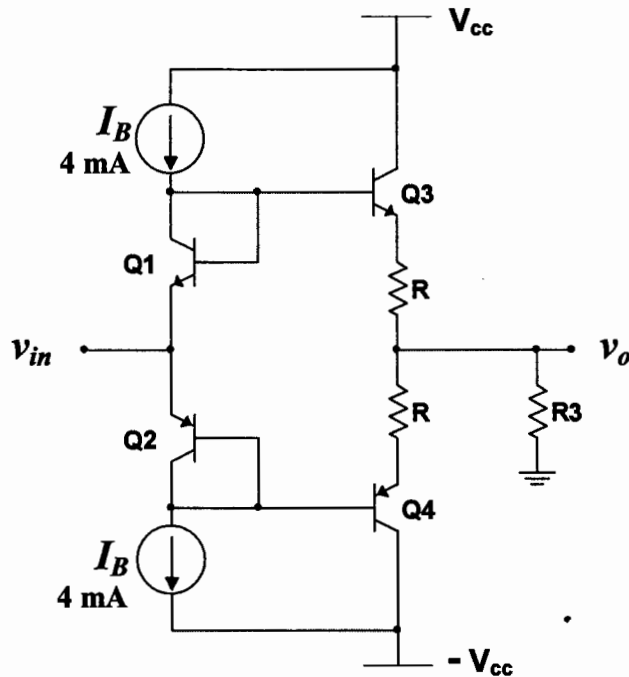


Fig. Q.2

- (a) Explain the purpose of transistors  $Q_1$  and  $Q_2$ . (2 marks)
- (b) Using the basic large-signal equation,  $I_c = I_s e^{v_{BE}/V_T}$ , consider the upper half of the circuit and neglect the base currents. Show that at quiescent conditions (i.e.  $v_{in} = 0$ ) the currents  $I_B$  and  $I_{c3}$  are related by


$$I_B = \left( \frac{I_{s1}}{I_{s3}} \right) I_{c3} e^{(I_{c3}R)/V_T}$$

**Hint:** When  $v_{in} = 0$ ,  $v_o = 0$ . Why is this so? (6 marks)

- (c) If  $I_{s1} = 0.3 \text{ pA}$  and  $I_{s3} = 4.5 \text{ pA}$  find the value of resistor  $R$  required to give a quiescent current of 5 mA in the output transistors. (4 marks)
- (d) When the output stage is delivering 150 mA into the load and  $\beta = 100$  for all transistors:
- Calculate the base-emitter voltage of  $Q_3$  assuming that  $Q_4$  is carrying negligible current. (4 marks)
  - Calculate also the emitter voltages of  $Q_1$ ,  $Q_2$  and  $Q_4$ . (5 marks)
  - Hence show that the assumption in (i) is valid. (4 marks)


**QUESTION THREE (25 Marks)**

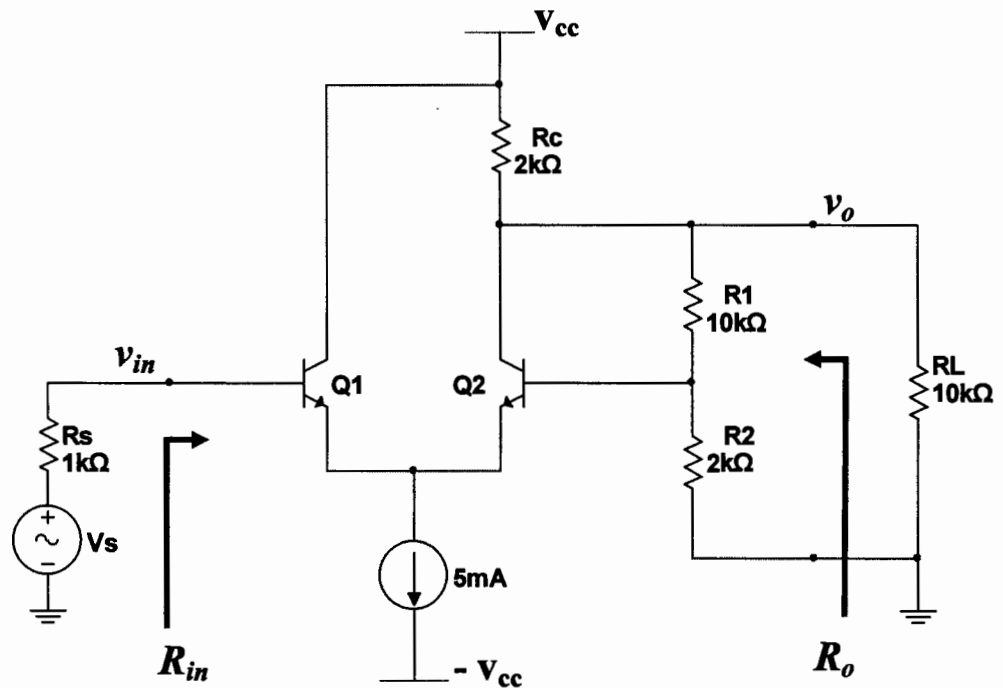- (a) A 741 opamp is specified as follows:  $A_v = 200,000$  V/V,  $r_{in} = 2$  M $\Omega$ ,  $r_{out} = 75$   $\Omega$ . It is desired to use the 741 in a feedback configuration to obtain an amplifier with input resistance of **at least** 1000 M $\Omega$  and an output resistance of **less than** 0.1  $\Omega$ .
- Which feedback configuration should be used in the required amplifier? Explain your answer. (3 marks)
  - What is the largest gain achievable in the amplifier which meets the specifications? (5 marks)
  - Design the amplifier giving components value for the feedback network. (4 marks)
- (b) For the amplifier shown in Fig. Q.3b, assume that the transistors Q1 and Q2 are matched with  $\beta = 100$ . Use feedback principles to obtain the voltage amplification factor  $\frac{v_o}{v_{in}}$  input impedance  $R_{in}$  and output impedance  $R_o$ . (13 marks)




**QUESTION FOUR (25 Marks)**

- (a) Manufacturer's noise data for the 2N5210 npn BJT are shown in Figs. Q4a.1 and Q4a.2. on the next page. The device is to be used at 200 Hz with a source resistance of  $500\Omega$  and a collector bias current of 3 mA. Assume room temperature operation at  $T = 293\text{ K}$ .
- (i) Calculate its total equivalent input noise per  $\sqrt{\text{Hz}}$ . *(10 marks)*
  - (ii) Calculate the narrow bandwidth Noise Figure. *(4 marks)*
- (b) A dc blocking L-section matches a  $300\Omega$  load to a  $50\Omega$  transmission line, the operating frequency being 500 MHz. Using the Q-method, determine the component values of the matching network. *(11 marks)*

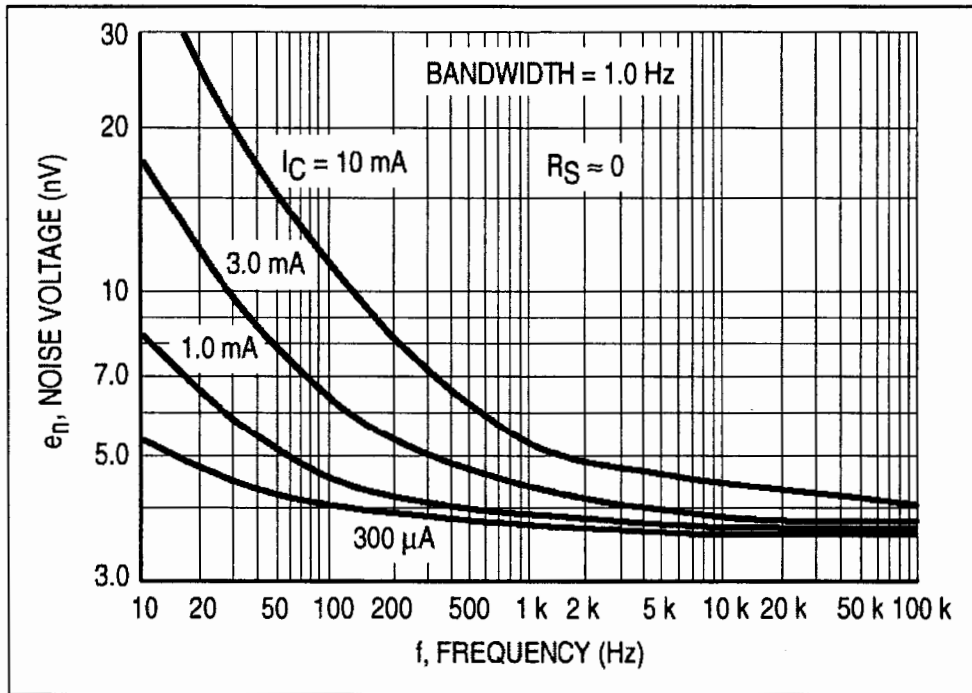

**Fig. Q4a.1** Motorola 2N5210 npn BJT: Noise voltage vs. frequency, for various quiescent collector currents, with  $R_S=0$  and  $BW = 1$  Hz.

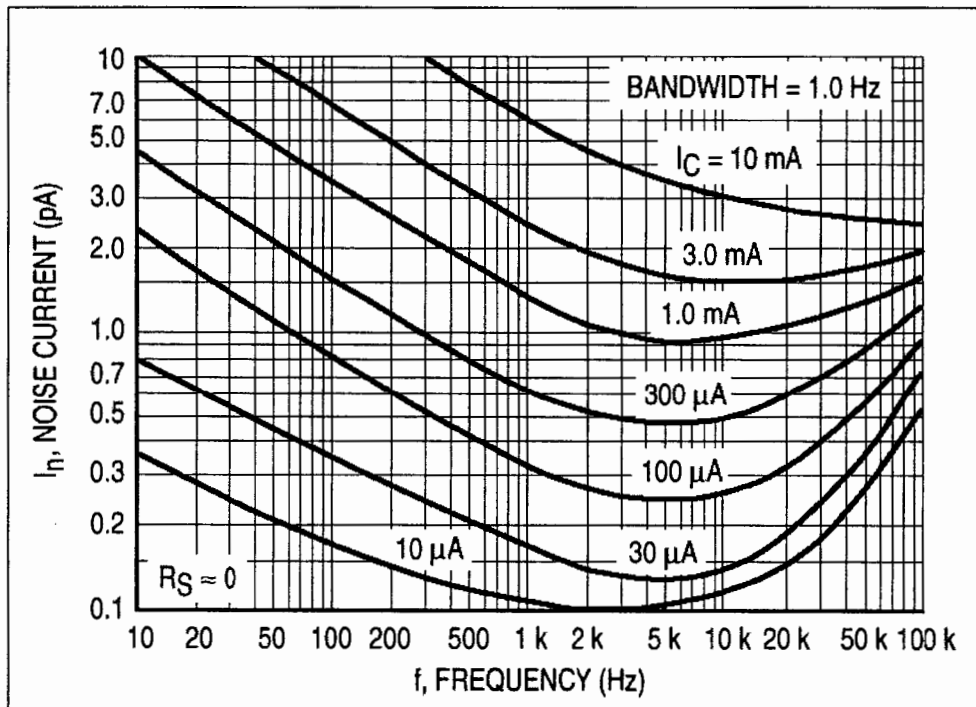

**Fig. Q4a.2** Motorola 2N5210 noise current vs. frequency, for various quiescent collector currents.

**QUESTION FIVE (25 Marks)**

An RF transistor biased at  $V_{CE} = 10$  V and  $I_C = 5$  mA has the following S-Parameters at 1 GHz. The parameters are based on 50- $\Omega$  terminations.

$$\begin{aligned} S_{11} &= 0.68 \angle 178^\circ & S_{21} &= 6.6 \angle 77^\circ \\ S_{12} &= 0.03 \angle 53^\circ & S_{22} &= 0.46 \angle -32^\circ \end{aligned}$$

- (a) Is this transistor stable with a source impedance of 300  $\Omega$  and a load of 30  $\Omega$  at this frequency? Justify your answer. (8 marks)
- (b) What is the Maximum Available Gain of this transistor? Under what condition is this obtained? (8 marks)
- (c) If the source impedance is 300  $\Omega$  and the load impedance is 30  $\Omega$  and  $S_{12}$  is assumed to be negligibly small, show with a circuit sketch how maximum gain can be obtained. Components values are not required, but you should indicate whether the components in your circuit are inductors or capacitors. (9 marks)

**QUESTION SIX (25 Marks)**

- (a) A source of 1.2 GHz is matched to a load by a matching network consisting of a transmission line and a shunt capacitor  $C$  as shown in Fig. Q6a. If the characteristic impedance of the transmission line is  $50 \Omega$ , find the required length of the line and the required value of the capacitance  $C$  using the Z-Y Smith Chart. Assume that the velocity of propagation in the transmission line is  $2.2 \times 10^8$  m/s. (19 marks)

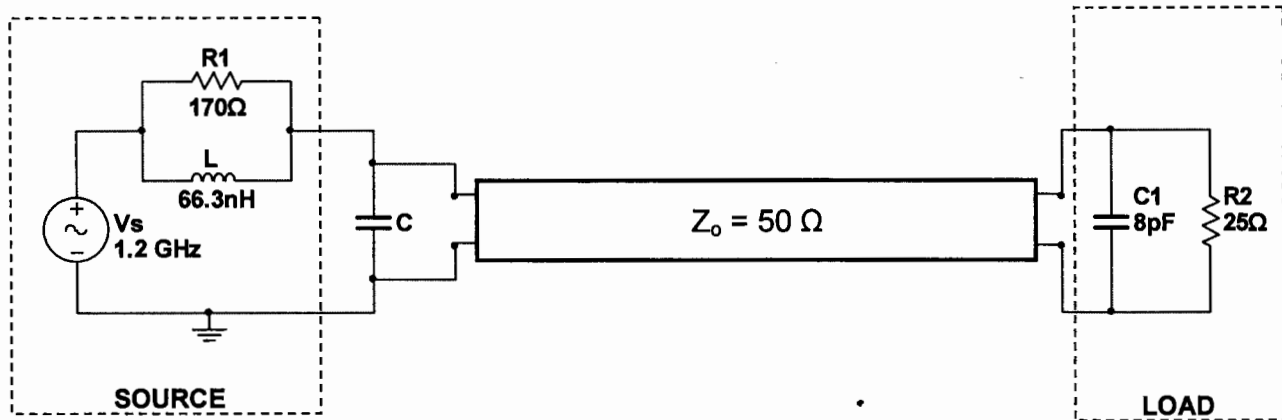


Fig Q6a

- (b) Design a dc passing L network to match a  $100\text{-}\Omega$  source to a  $10\text{-}\Omega$  load at a frequency of 1 GHz. (6 marks)



**SOME SELECTED USEFUL RF DESIGN FORMULAE**

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|^2}$$

$$\text{where } |\Delta| = |S_{11}S_{22} - S_{12}S_{21}|$$

$$\text{MAG} = 10 \log \left| \frac{S_{21}}{S_{12}} \right| + 10 \log \left| K - \text{sgn}(B_1) \sqrt{K^2 - 1} \right| \text{ dB}$$

$$\text{where } B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2$$