

UNIVERSITY OF SWAZILAND
SUPPLEMENTARY EXAMINATION, JULY 2011

FACULTY OF SCIENCE

**DEPARTMENT OF ELECTRICAL AND ELECTRONIC
ENGINEERING**

TITLE OF PAPER: ANALOGUE ELECTRONICS IV

COURSE CODE: E512

TIME ALLOWED: THREE HOURS

INSTRUCTIONS:

- 1. There are five questions in this paper. Answer any FOUR questions.
Each question carries 25 marks.**
- 2. If you think not enough data has been given in any question you may
assume any reasonable values.**
- 3. A sheet with useful RF design formulae is attached at the end of the
paper.**
- 4. Impedance-Admittance (Z-Y) Smith Charts are provided.**

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION
HAS BEEN GIVEN BY THE INVIGILATOR**

THIS PAPER CONTAINS SEVEN (7) PAGES INCLUDING THIS PAGE

QUESTION ONE (25 marks)

(a) An output stage of an amplifier is shown in Figure-Q1.

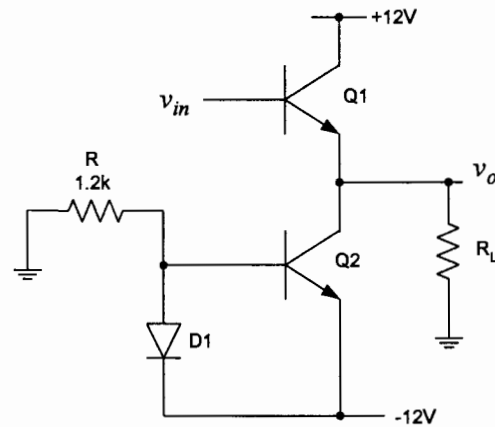


Figure-Q1

- (i) Identify the type of the amplifier stage shown and sketch the transfer characteristic (v_o vs v_{in}). **(3 marks)**
- (ii) If the ratio of emitter junction area of Q_2 to the junction area of D_1 is 50
(i.e. $\frac{A_{jQ2}}{A_{jD1}} = 50$), find the value of R_L for which the output signal is maximum.
 You may neglect the base currents and the saturation voltages. **(5 marks)**
- (iii) Calculate the maximum output power and the power conversion efficiency. **(5 marks)**
- (b) (i) Draw the safe operating area (SOA) of a BJT and identify the limits of operation. **(3 marks)**
- (ii) Some values referred from a BJT data sheet are given below.
 $T_{j\max} = 150^\circ\text{C}$ $P_{D\max} = 2.5\text{W}$ (at $T_A = 25^\circ\text{C}$)
 $P_{D\max} = 50\text{W}$ (at $T_C = 25^\circ\text{C}$)
- Find the maximum power dissipation this device can handle in free air when it is used in an ambient temperature of 40°C . If this device is required to dissipate 30W at the ambient temperature of 40°C , find the specification of the required heat sink. Also calculate the temperature of the heat sink at the steady state.
 Assume $\theta_{CS} = 0.5^\circ\text{C/W}$. **(9 marks)**

QUESTION TWO (25 marks)

Consider the class AB amplifier output stage in Figure-Q2. The transistors are of silicon and Q_2, Q_3 are matched.

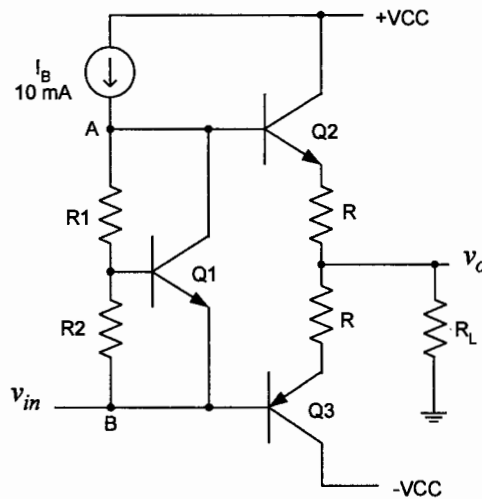


Figure-Q2

- (a) Explain the function of Q1. **(4 marks)**

- (b) If $R = 0$ and under quiescent conditions (*i.e.* $v_{in} = 0$), show that

$$I_{C2} = I_{S2} \left(\frac{I_B}{I_{S1}} \right)^{\frac{1+K}{2}} \quad \text{where} \quad K = \frac{R_1}{R_2}.$$

You may use the large signal equation $I_C = I_S e^{\frac{V_{BE}}{V_T}}$. Neglect the base currents and the currents in R_1 and R_2 . **(8 marks)**

- (c) When $R = 2.2k$, $I_{S1} = 0.4 pA$ and $I_{S2} = 6 pA$, find the value of K to have a quiescent current of $10mA$ in the output transistors. **(6 marks)**
- (d) Find V_{AB} when the current in Q_2 is $300mA$ and compare it with its value under the quiescent conditions. Assume for Q_2 and Q_3 , the current gain $\beta = 100$ and for Q_1 the gain is high. The value of K is same as in (c). **(7 marks)**

QUESTION THREE (25 marks)

A load of 120Ω is matched to a 50Ω source using a transmission line and an inductor as shown in Figure-1.

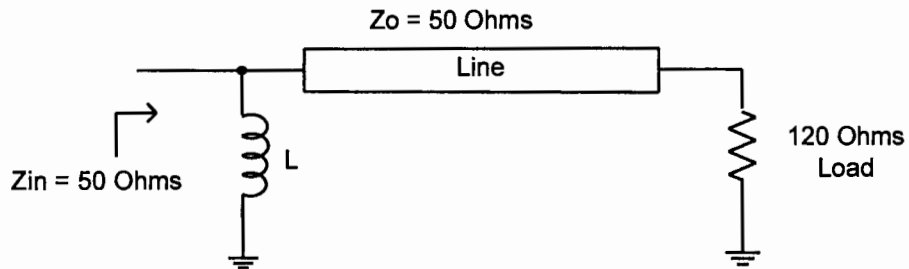


Figure -1

Using the ZY Smith Chart find the length of the transmission line and the value of inductance L at $10\ \text{MHz}$. Assume that the speed of propagation in the transmission line is $2.2 \times 10^8\ \text{m/s}$.

(25 marks)

QUESTION FOUR (25 marks)

- (a) If the parallel combination of resistor R_p and reactance jX_p is transformed to the series combination of resistance R_s and reactance jX_s , show that the Q of the combinations is given by

$$Q = \sqrt{\left(\frac{R_p}{R_s} - 1\right)}$$

(5 marks)

- (b) Design a dc passing L network to match a load of 600Ω to a source of 50Ω at 200MHz.
(10 marks)
- (c) If the noise generated in an amplifier is represented by the two input noise generators of instantaneous noise voltage e_n and instantaneous noise current i_n , show that the optimum source resistance for minimum noise factor is given by

$$R_{S(opt)} = \left(\frac{\overline{e_n^2}}{\overline{i_n^2}}\right)^{\frac{1}{2}}$$

(10 marks)

QUESTION FIVE (25 marks)

The s-parameters of a transistor used in a common emitter amplifier at 1 GHz and operating with $V_{CE} = 15V$, $I_C = 5mA$ are given below.

$$S_{11} = 0.68 \angle 178^\circ \quad S_{21} = 6.6 \angle 77^\circ \quad S_{12} = 0.03 \angle 53^\circ \quad S_{22} = 0.46 \angle -32^\circ$$

- (a) Investigate the stability of the amplifier using this transistor at 1 GHz with source and load impedance of 50Ω . **(10 marks)**
- (b) Evaluate the maximum available gain. **(7 marks)**
- (c) Assuming $S_{12} = 0$, give the schematic diagram of a maximum gain amplifier indicating the type of the components. You need not to give the values of the components. **(8 marks)**

SOME SELECTED USEFUL RF DESIGN FORMULAE

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|^2}$$

$$\text{where } |\Delta| = |S_{11}S_{22} - S_{12}S_{21}|$$

$$\text{MAG} = 10 \log \left| \frac{S_{21}}{S_{12}} \right| + 10 \log \left| K - \text{sgn}(B_1) \sqrt{K^2 - 1} \right| \text{ dB}$$

$$\text{where } B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2$$