

UNIVERSITY OF SWAZILAND
MAIN EXAMINATION, FIRST SEMESTER DECEMBER 2011

FACULTY OF SCIENCE

**DEPARTMENT OF ELECTRICAL AND ELECTRONIC
ENGINEERING**

TITLE OF PAPER: ELECTRONICS III
COURSE CODE: E511

TIME ALLOWED: THREE HOURS

INSTRUCTIONS:

- 1. There are five questions in this paper. Answer any FOUR questions.
Each question carries 25 marks.**
- 2. If you think not enough data has been given in any question you may
assume any reasonable values.**

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION
HAS BEEN GIVEN BY THE INVIGILATOR**

THIS PAPER CONTAINS SEVEN (7) PAGES INCLUDING THIS PAGE

QUESTION ONE (25 marks)

(a) A two stage IC amplifier is shown in Figure-Q1.

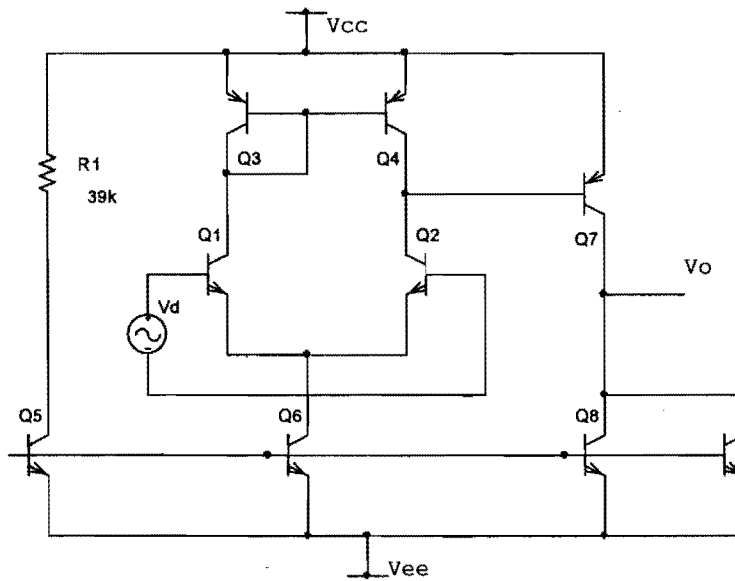


Figure-Q1

Assume that the input bias currents are drawn from the signal source. The two parallel transistors are represented by Q8 as a single equivalent. You may assume the following data.

For pnp: $V_A = 50V$ $\beta = 75$

For npn: $V_A = 120V$ $\beta = 100$

$V_{CC} = 10V$ $V_{EE} = -10V$

Find the following.

- (a) Collector Currents of all transistors at no signal. (3 marks)
- (b) Differential input impedance. (4 marks)
- (c) Voltage gain $\frac{v_o}{v_d}$. (15 marks)
- (d) Output impedance. (3 marks)

QUESTION TWO (25 marks)

A circuit of the Widlar current source is shown in Figure-Q2. Assume that the transistors are matched and the β is large unless otherwise stated.

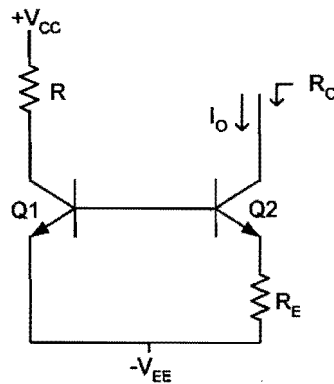


Figure-Q2

- (a) Show that the current I_O is given by

$$I_O = \frac{V_T}{R_E} \ln \left[\frac{V_{CC} - V_{BE} + V_{EE}}{R I_O} \right].$$

(5 marks)

- (b) Derive an expression for the output resistance R_O .

(10 marks)

- (c) Design the current source for $I_O = 500 \mu A$ with $\pm 10V$ supplies.

(5 marks)

- (d) Assuming $\beta = 100$ and $V_A = 100V$,

- (i) Find the minimum possible voltage at the output while maintaining proper operation of the current source.
- (ii) Also calculate the output resistance.

(5 marks)

QUESTION THREE (25 marks)

A block diagram of an IC op-amp is shown in Figure-Q3.

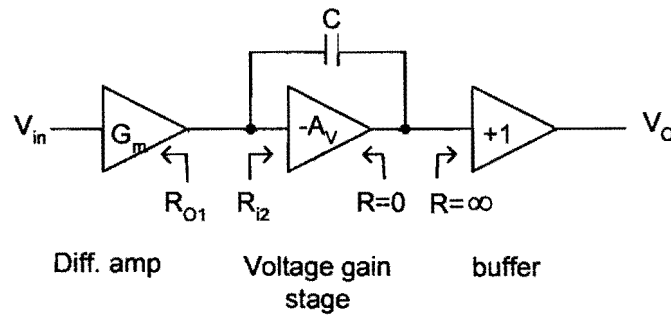


Figure-Q3

- (a) It is required to introduce a dominant pole at 10Hz for frequency compensation. The impedances R_{O1} and R_{i2} are 2M and 1.5M respectively. If $A_v = 500$, find the value of the compensation capacitor C .

Note that the value of G_m is not given intentionally.

(7 marks)

- (b) Assuming the DC gain of the op-amp is 100dB ,
- (i) Find the unity gain bandwidth using the data given in (a).
 - (ii) If the amplifier is used with negative feedback and the feedback factor is 0.01 , find the resulting bandwidth.

(10 marks)

- (c) If the total bias current available in the differential amplifier stage is $20\mu\text{A}$, find the slew rate and the full power bandwidth. Assume that the maximum available output is 10V .

(8 marks)

QUESTION FOUR (25 marks)

An integrated circuit CMOS amplifier is shown in Figure-Q4.

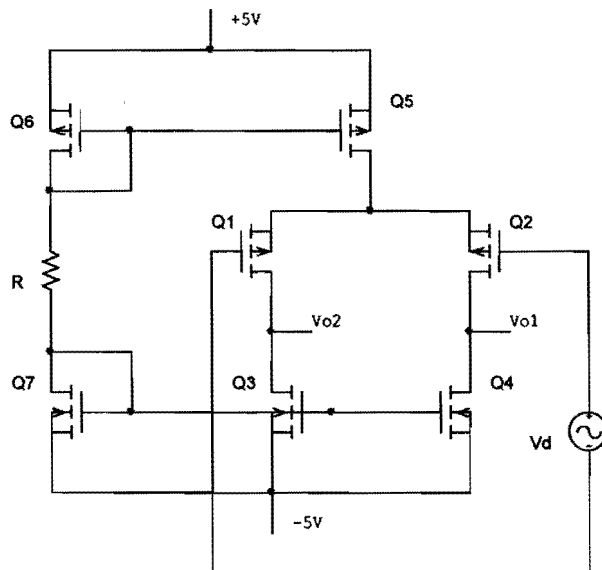


Figure-Q4

The voltage V_d is the input and the voltages V_{o1} and V_{o2} are the outputs. The sets of matching transistors are $[Q_6, Q_5]$, $[Q_1, Q_2]$, $[Q_3, Q_4]$. Some of the design data of the amplifier are given below.

$$\text{Differential gain } \frac{V_{o1} - V_{o2}}{V_d} = -50$$

$$\text{Reference current} = 200 \mu\text{A}$$

$$\text{Voltage at the gate of } Q_6 = 1.5\text{V}$$

$$\text{Voltage at the gate of } Q_7 = -1.5\text{V}$$

Process parameters:

$$V_A = 20\text{V} \quad (\text{for all transistors})$$

$$K'_P = 50 \frac{\mu\text{A}}{\text{V}^2}$$

$$K'_n = 100 \frac{\mu\text{A}}{\text{V}^2}$$

$$|V_t| = 2.5\text{V}$$

- (a) Find the bias currents of all transistors and the value of R .

(5 marks)

- (b) Show that the differential gain $\left(\frac{V_{o1} - V_{o2}}{V_d} \right) = -V_A \sqrt{\frac{K_P}{I_{D2}}}$

(8 marks)

- (c) Find the $\left(\frac{W}{L} \right)$ values of each transistor.

(12 marks)

1. SOME USEFUL MOSFET EQUATIONS

$$i_D = k_n \frac{W}{L} \left[(v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right] \text{ in triode region}$$

$$i_D = \frac{1}{2} k_n \frac{W}{L} (v_{GS} - V_t)^2 \text{ in saturation region}$$

$$i_D = \frac{1}{2} k_n \frac{W}{L} (v_{GS} - V_t)^2 (1 + \lambda v_{DS}) \text{ in saturation region with Channel Modulation effect}$$

$$V_A = 1/\lambda$$

2. BJT EBERS-MOLL EQUATIONS

$$i_E = \frac{I_s}{\alpha_F} (e^{v_{BE}/V_T} - 1) - I_s (e^{v_{BC}/V_T} - 1)$$

$$i_C = I_s (e^{v_{BE}/V_T} - 1) - \frac{I_s}{\alpha_R} (e^{v_{BC}/V_T} - 1)$$

$$i_B = \frac{I_s}{\beta_F} (e^{v_{BE}/V_T} - 1) + \frac{I_s}{\beta_R} (e^{v_{BC}/V_T} - 1)$$

3. Unless otherwise stated, $V_{BE(ON)} = 0.7 \text{ V}$ and $V_T = 0.025 \text{ V}$.
