

UNIVERSITY OF SWAZILAND
MAIN EXAMINATION, SECOND SEMESTER MAY 2012

FACULTY OF SCIENCE

**DEPARTMENT OF ELECTRICAL AND ELECTRONIC
ENGINEERING**

TITLE OF PAPER: ANALOGUE ELECTRONICS IV
COURSE CODE: E512

TIME ALLOWED: THREE HOURS

INSTRUCTIONS:

- 1. There are five questions in this paper. Answer any FOUR questions.
Each question carries 25 marks.**
- 2. If you think not enough data has been given in any question you may
assume any reasonable values.**

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION
HAS BEEN GIVEN BY THE INVIGILATOR**

THIS PAPER CONTAINS SEVEN (7) PAGES INCLUDING THIS PAGE

QUESTION ONE (25 marks)

- (a) A power output stage is shown in Figure-Q1. Assume $I_R = 100\text{mA}$, $V_{CE(sat)} = 0.2\text{V}$ and $V_{CC} = 12\text{V}$.

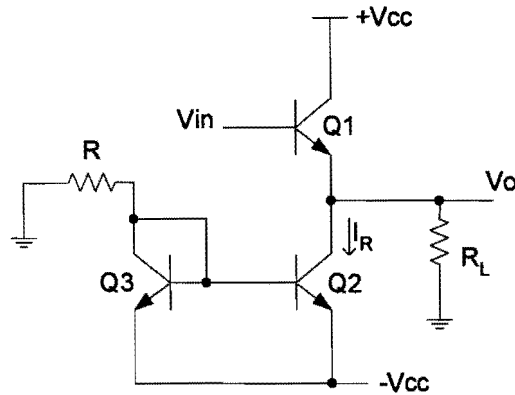


Figure-Q1

- (i) If $R_L = 100\Omega$, find the maximum input signal that can be applied while having an undistorted output signal. Calculate the power conversion efficiency under this condition. Do not neglect the dissipation in R and Q_3 . (8 marks)
- (ii) Find the value of R_L for maximum efficiency and evaluate the value of efficiency. (5 marks)
- (b) The following data is found for a BJT from a datasheet.
- $$T_{j\max} = 150^\circ\text{C} \qquad P_{D\max} = 2\text{W} \quad (\text{at } T_A = 25^\circ\text{C})$$
- $$P_{D\max} = 50\text{W} \quad (\text{at } T_C = 25^\circ\text{C})$$
- If the device is to dissipate 25W when operating in an ambient temperature of 50°C , find the specifications of the required heatsink. Assume $\theta_{CS} = 0.5 \frac{^\circ\text{C}}{\text{W}}$. Also find the temperature of the heatsink. (12 marks)

QUESTION TWO (25 marks)

A class-AB amplifier is shown in Figure-Q2. The transistors Q_1 and Q_2 have $I_S = 3 \times 10^{-13} A$. For the diodes D_1 and D_2 , $I_S = 10^{-13} A$. The amplifier is supposed to deliver $2W$ of power to the load under the maximum signal swing.

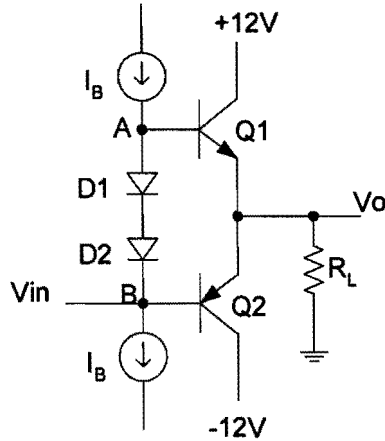


Figure-Q2

- (a) Find a value for I_B and determine the quiescent collector currents in the transistors. You may assume $\beta = 50$ and $V_{CE(sat)} = 0.3V$. (8 marks)
- (b) Find the quiescent power dissipation in the transistors and calculate the power conversion efficiency. (5 marks)
- (c) Design a V_{BE} multiplier for this circuit using a high gain transistor having $I_S = 10^{-14} A$. State clearly your assumptions. (12 marks)

QUESTION THREE (25 marks)

- (a) The op-amp used in the circuit shown in Figure-Q3(A) has an open loop gain-bandwidth product of 10^6 Hz with a single dominant pole at 10 Hz . Determine the overall bandwidth of the circuit assuming, $R_{id} = \infty$, and $R_o = 0$ for the op-amp.

(7 marks)

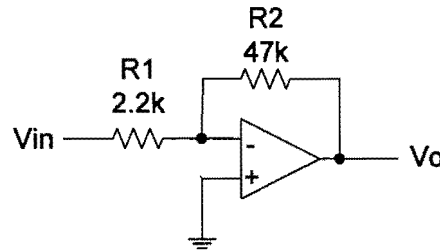


Figure-Q3(A)

- (b) Analyze the amplifier shown in Figure-Q3(B), using the method of feedback to determine the closed loop voltage gain $\frac{V_o}{V_s}$, the input impedance R_{in} and the output impedance R_o . Assume that the $\beta = 100$ for all transistors and the biasing arrangements are not shown for simplicity.

(18 marks)

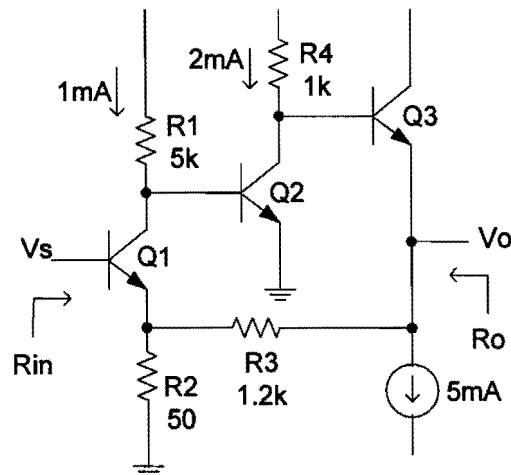


Figure-Q3(B)

QUESTION FOUR (25 marks)

A 300MHz source having an impedance of 600Ω is to be matched to a 50Ω load using a lossless network.

- (i) Using the Q method, design a dc blocking L -section matching network.

(10 marks)

- (ii) Design a suitable dc passing π -network for this matching requirement. You may assume a virtual center impedance of 10Ω .

(15 marks)

QUESTION FIVE (25 marks)

The s-parameters of a RF transistor in a common emitter amplifier at 1GHz with a bias point $V_{CE} = 12V$ and $I_C = 5mA$ are given below.

$$s_{11} = 0.7 \angle 60^\circ$$

$$s_{21} = 5.2 \angle 70^\circ$$

$$s_{12} = 0.08 \angle 70^\circ$$

$$s_{22} = 0.09 \angle -150^\circ$$

- (a) Investigate the stability of the device at the given operating conditions. (10 marks)
- (b) Find the maximum available gain when conjugate matching is employed. (7 marks)
- (c) Assume that the load and the source impedances are each of 50Ω and the reverse transmission can be neglected. Give the schematic diagram of a maximum gain amplifier indicating the component types. You need not to give the component values. (8 marks)

SOME SELECTED USEFUL RF DESIGN FORMULAE

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|^2}$$

$$\text{where } |\Delta| = |S_{11}S_{22} - S_{12}S_{21}|$$

$$\text{MAG} = 10 \log \left| \frac{S_{21}}{S_{12}} \right| + 10 \log \left| K - \text{sgn}(B_1) \sqrt{K^2 - 1} \right| \text{ dB}$$

$$\text{where } B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2$$