

UNIVERSITY OF SWAZILAND
MAIN EXAMINATION, FIRST SEMESTER DECEMBER 2011

FACULTY OF SCIENCE

**DEPARTMENT OF ELECTRICAL AND ELECTRONIC
ENGINEERING**

TITLE OF PAPER: ANALOGUE DESIGN III
COURSE CODE: EE421

TIME ALLOWED: THREE HOURS

INSTRUCTIONS:

- 1. There are five questions in this paper. Answer any FOUR questions.
Each question carries 25 marks.**
- 2. If you think not enough data has been given in any question you may
assume any reasonable values.**

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION
HAS BEEN GIVEN BY THE INVIGILATOR**

THIS PAPER CONTAINS SIX (6) PAGES INCLUDING THIS PAGE

QUESTION ONE (25 marks)

Consider the differential amplifier shown in Figure-Q1.

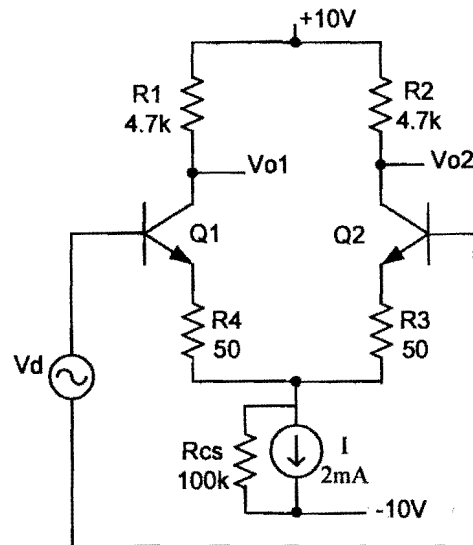


Figure-Q1

- (a) Find the differential input resistance. Assume $\beta = 100$. (3 marks)

- (b) Draw the differential half circuit. Hence calculate the voltage gains $\frac{V_{o2}}{V_d}$ and

$$\frac{V_{o2} - V_{o1}}{V_d}. \quad (7 \text{ marks})$$

- (c) Draw the common mode half circuit. Then calculate the common mode gain at the output V_{o2} and CMRR in dB. (7 marks)

- (d) Estimate the high frequency 3dB bandwidth if $R_4 = R_3 = 0$.

$$C_\pi = 13 \text{ pF} \quad C_\mu = 2 \text{ pF} \quad r_o = \infty \quad (8 \text{ marks})$$

QUESTION TWO (25 marks)

- (a) For the circuit shown in Figure-Q2(a), the two transistors Q1 and Q2 are matched.

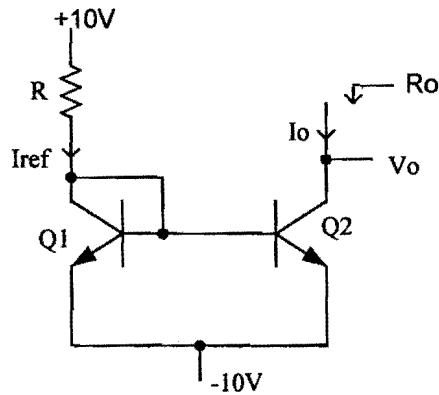


Figure-Q2(a)

- (i) If the current gain of the transistors are β ,
- 1.1 Find an expression for I_o with I_{ref} .
 - 1.2 Calculate the value of R to have an $I_o = 1mA$. Assume $\beta = 75$.
- (5 marks)
- (ii) What is the output resistance R_o ? Find the value of the output current I_o , if the output voltage V_o is 5V. Assume $V_A = 100V$.
- (9 marks)
- (b) Consider the current source shown in Figure-Q2(b). You may assume that the transistors are matched.

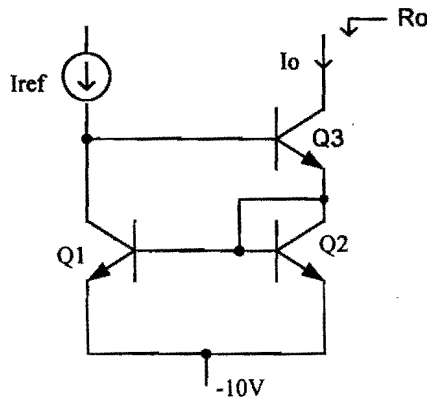


Figure-Q2(b)

- (i) Derive the percentage change of I_o with respect to I_{ref} .
- (6 marks)
- (ii) Calculate the value of R_o . You may use any formula known to you.
- $I_{ref} = 100\mu A$ $V_A = 120V$ $\beta = 100$
- (3 marks)
- (iii) State two advantages of this circuit.
- (2 marks)

QUESTION THREE (25 marks)

- (a) A circuit of an enhancement type NMOS amplifier is shown in Figure-Q3(a).

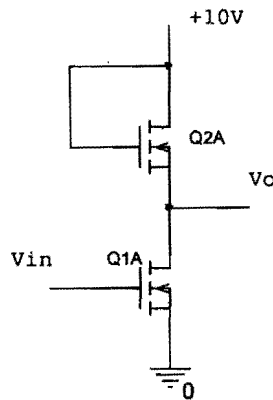


Figure-Q3(a)

For this amplifier, following process parameters are given.

$$W_1 = 100\mu\text{m} \quad L_1 = 6\mu\text{m} \quad W_2 = 1\mu\text{m} \quad L_2 = 6\mu\text{m} \quad V_t = 1\text{V}$$

- (i) Obtain a relationship between
- V_o
- and
- V_{in}
- for dc voltages. Calculate
- V_o
- if

$$V_{in} = 1.5\text{V}.$$

(10 marks)

- (ii) Draw the small signal equivalent circuit. Hence derive an expression for the voltage gain and calculate its value.

(8 marks)

- (b) For the CMOS amplifier shown in Figure-Q3(b),

$$K_n = K_p = 100\mu\text{A}/\text{V}^2 \quad V_{in} = |V_{tp}| = 1\text{V} \quad V_{An} = V_{Ap} = 100\text{V} \quad I_{ref} = 100\mu\text{A}.$$

Find the small signal voltage gain.

(7 marks)

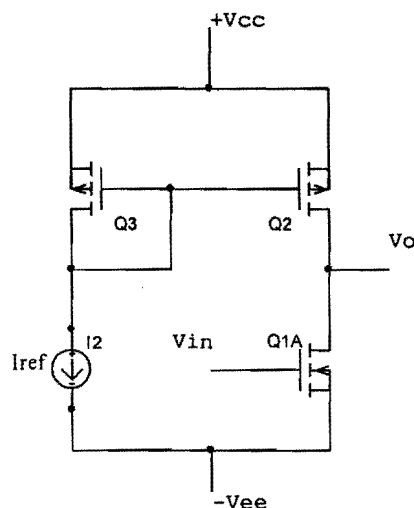


Figure-Q3(b)

QUESTION FOUR (25 marks)

Consider the cascode amplifier shown in Figure-Q4.

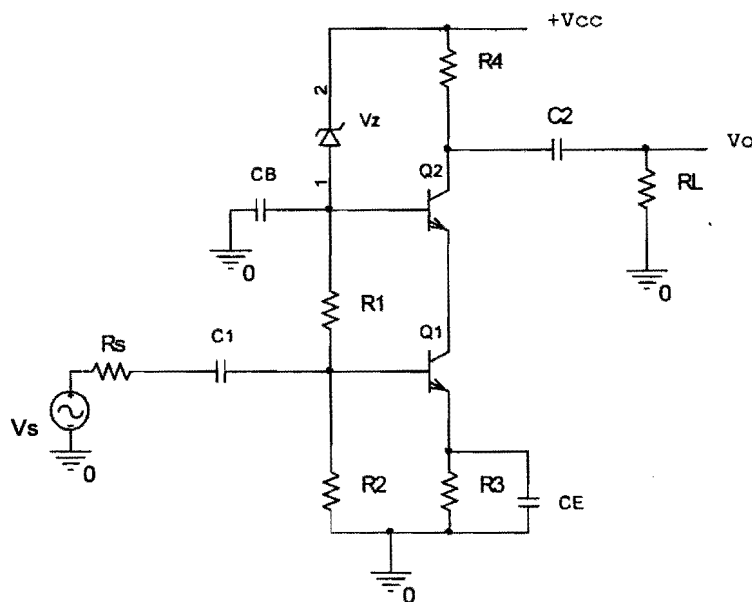


Figure-Q4

- (a) Assuming that the transistors are identical,
- (i) Find an expression for the mid band voltage gain.
 - (ii) Calculate the mid band gain for the data given below.

$$R_S = 2k \quad R_1 = 5k \quad R_2 = 8k \quad R_3 = 1k \quad R_4 = 5k \quad R_L = 3k \quad V_Z = 5V$$

$$\beta = 100 \quad I_{C2} = 1mA \quad (13 \text{ marks})$$

- (b) Find the values of the pole frequencies and hence determine the high frequency 3dB bandwidth. (12 marks)

QUESTION FIVE (25 marks)

A dc regulator circuit is shown in Figure-Q5.

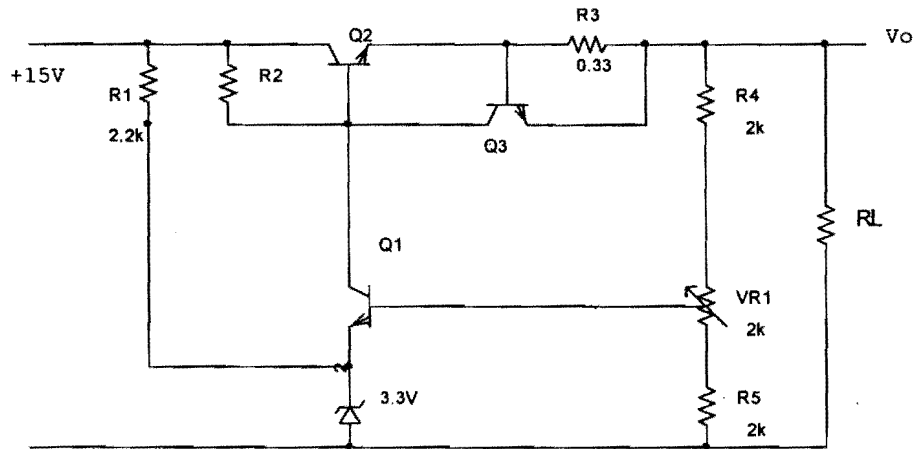


Figure-Q5

- (a) Find the range of the output voltage V_o . (6 marks)
- (b) Find an expression for the power dissipation in Q_2 in terms of the load current at a short circuit of the output. (4 marks)
- (c) Derive a relationship of the load current and the minimum load resistance that can be applied while maintaining the regulation. (3 marks)
- (d) If the minimum collector current of Q_1 is I_{CIL} , find an expression for R_2 . (6 marks)
- (e) Calculate the maximum load current value. Then find out,
- The maximum power dissipation in Q_2 .
 - The minimum load resistance.
 - The value of R_2 . Assume that the $\beta = 20$ for Q_2 and $I_{CIL} = 5mA$.
- (6 marks)

1. SOME USEFUL MOSFET EQUATIONS

$$i_D = k_n' \frac{W}{L} \left[(v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right] \text{ in triode region}$$

$$i_D = \frac{1}{2} k_n' \frac{W}{L} (v_{GS} - V_t)^2 \text{ in saturation region}$$

$$i_D = \frac{1}{2} k_n' \frac{W}{L} (v_{GS} - V_t)^2 (1 + \lambda v_{DS}) \text{ in saturation region with Channel Modulation effect}$$

$$V_A = \frac{1}{\lambda}$$

2. Unless otherwise stated, $V_{BE(ON)} = 0.7V$ and $V_T = 0.025V$.