

UNIVERSITY OF SWAZILAND
FACULTY OF SCIENCE
DEPARTMENT OF ELECTRICAL AND ELECTRONIC
ENGINEERING

MAIN EXAMINATION DECEMBER 2011

TITLE OF PAPER: ELECTRICAL MACHINES
COURSE CODE: EE 451
TIME ALLOWED: THREE HOURS

Student Name:	
Student Number:	

INSTRUCTIONS:

1. Answer all questions.
2. Give your answers on the question paper, and if more space is required, complete your answer on the back of the paper or in your answer book and mention about the place of your answer completion.
3. Put the question sheet inside the answer book upon submission of your exam paper.
(DON'T FORGET TO SUBMIT BOTH OF THE ANSWER BOOK AND QUESTION PAPER)
4. Marks for different questions are indicated on the beginning of the question.
5. Rough work maybe done in the examination answer book and crossed through.

DO NOT OPEN THIS PAPER UNTIL PERMISSION HAS BEEN GRANTED BY THE INVIGILATOR

This paper starts at page 1 and ends at page 16.

Question 1: Solve the following questions (19 marks)


- a) The equivalent circuit impedances of a 20 kVA, 2200 V / 220 V, 50 Hz transformer to be determined. The open circuit test and short circuit test were performed and the following data were found. Calculate the impedances of approximate equivalent circuit referred to primary.

(Calculate $R_C, X_M, R_{eqp}, X_{eqp}$)

Open circuit results	Short circuit results
$V_{oc} = 2200V$	$V_{sc} = 50V$
$I_{oc} = 0.2A$	$I_{sc} = 8A$
$P_{oc} = 40W$	$P_{sc} = 170W$

- b) 60 KVA, 13800 V / 478 V (line to line) Δ -Y distribution transformers has equivalent impedance referred to the primary side $Z_{eqp} = 100 + j600 \Omega$. Find the primary phase voltage at the source $V_{\phi p}$ and voltage regulation V_R assuming the transformer supplies rated load at 0.8 pf lagging.

- c) 300 VA, 200 V / 20 V transformer to be connected to form a step up autotransformer. Calculate the voltage at the high voltage side of the transformer V_H , maximum current at the high voltage side I_H , the current in low voltage side I_L and the output volt-ampere S_{out} .
 (Calculate V_H, I_H, I_L, S_{out})

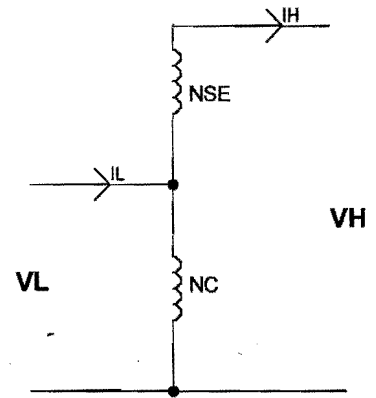

Question 2: Solve the following questions (28 marks)


a) A 460 V (line to line) 50 Hz Y connected two pole synchronous generator. The generator has a synchronous reactance of 0.15Ω and armature resistance of 0.02Ω . At full load the machine supplies 800 A at $\text{pf}=0.85$ lagging. Calculate the internal voltage E_A and the output power from generator P_{out} .

b) A 400 V 50 KVA 0.8 pf Δ connected 60 Hz synchronous motor has synchronous reactance 3Ω and negligible armature resistance. The friction and windage losses are 1.5 KW and core losses = 2 KW. Initially the shaft supplies 20 hp and pf of the machine is 0.8 leading. Find the armature current I_A and induced voltage E_A (Calculate I_A, E_A)

c) Assume in b, the load shaft increased to 40 hp, find the armature current I_A .
What is the main effect of increasing motor load torque on motor current?

- d) A 40 hp, 200V, 1000 rev/min DC shunt motor has armature resistance $R_A = 0.3 \Omega$. The field winding has a total resistance $R_F + R_{adj}$ of 50Ω which produces no load speed at 1000 rev/min. Calculate the speed of the motor expressed in rev/min n_m , the motor input power P_{in} and the motor induced torque T_{ind} when the input current I_L is 100 A.



(Calculate: n_m, P_{in}, T_{ind})

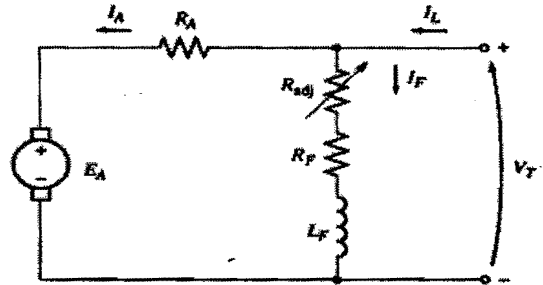

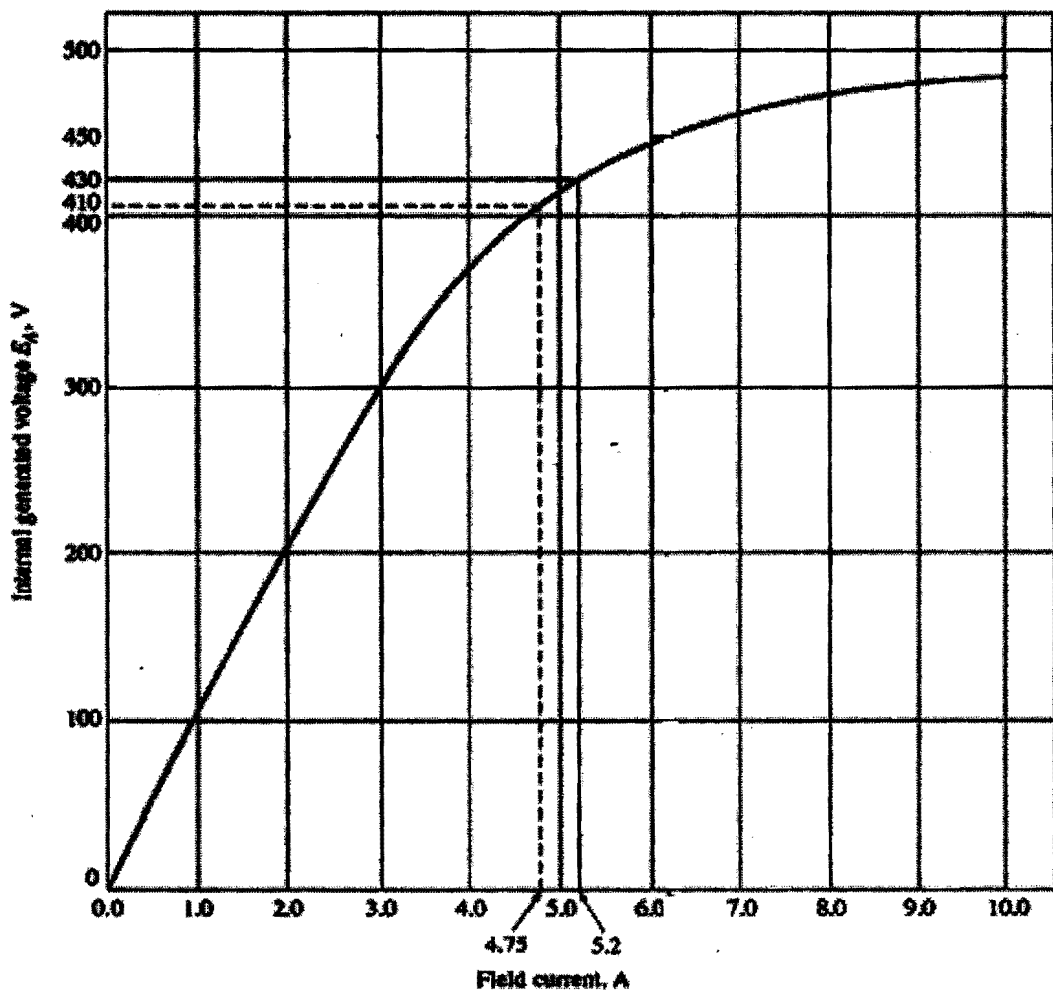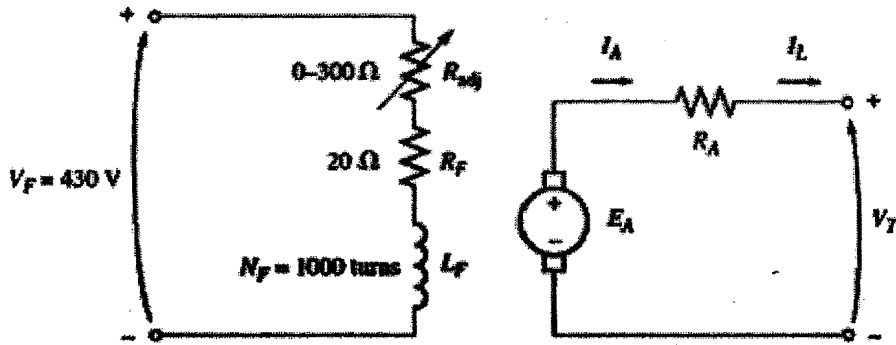Question 3: Solve the following questions (13 marks)

A separately excited dc generator, 172 KW, 430V, 400 A and 1800 rpm. The DC generator equivalent circuit and its magnetization curve are shown in the following figures. The machine has the following characteristics:

$R_A = 0.1 \Omega$, $V_F = 430 \text{ V}$, $R_F = 20 \Omega$, $R_{adj} = 0 \text{ to } 300 \Omega$.



If $R_{adj} = 63 \ \Omega$ and the prime mover speed = 1200 rev/min,

a) Calculate the no load generator voltage.

b) What is the terminal voltage V_T when $2 \ \Omega$ load connected?

(Calculate V_T)


c) Calculate the induced voltage E_A to restore V_T at no load value.

(Calculate E_A)

- d) How much the field current and the field adjustable resistance needed to restore V_T at no load value? .
(Calculate I_F , R_F)

Question 4: Solve the following questions (8 marks)

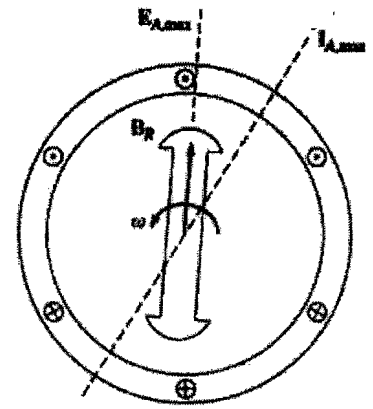
a) Explain briefly the principle of operation of the synchronous generator.



b) Indicate, for a given phase voltage and load current, will a more internal voltage E_A is needed for leading power factor load or lagging power factor load?

Question 5: Answer the following questions (21 marks)

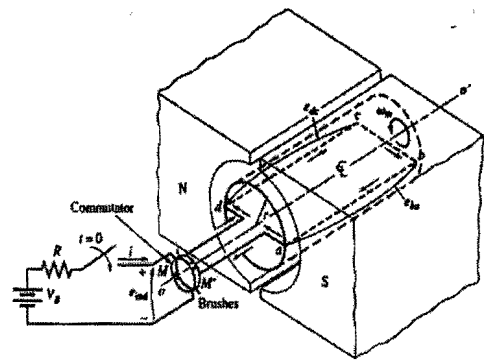a) Explain briefly the principle of operation of the DC motor.



b) What is the effect of increasing the mechanical load torque on DC motor?

c) How is possible to control the DC motor speed? Mention about two methods used. Indicate which method is used to control DC motor speed above base speed and which method used to control DC motor speed below base speed.

d) Draw the equivalent circuit of the cumulatively compounded motor. Mention the main advantages of the cumulatively compounded motor and the main disadvantage of the differentially compounded DC motor.

e) What is the effect of increasing the electrical load on the DC generator terminal voltage?

f) How it is possible to increase the DC generator terminal voltage?

g) How the terminal voltage in shunt DC generator will build up:

- a) By the voltage source connected to the field winding
- b) By the residual flux in the generator

h) When the number of series winding turns N_{SE} of the cumulatively compounded DC generator is very large, the DC generator is

- a) Flat compounded.
- b) Under compounded.
- c) Over compounded.

i) The under compounded DC generator will have


- a) No load voltage > full load voltage.
- b) No load voltage < full load voltage.
- c) No load voltage = full load voltage.

j) The differentially compounded DC generator will have

- a) Small drop in terminal voltage as load increased on the generator.
- b) Large drop in terminal voltage as load increased on the generator.
- c) No change in terminal voltage as load increased on the generator

Question 6: Answer the following questions (11 marks)

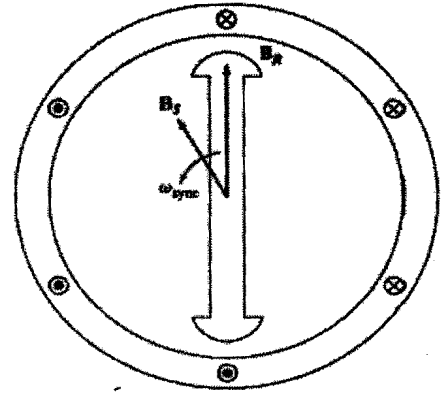a) Explain briefly the principle of operation of the synchronous motor.



b) What is the effect of increasing mechanical load torque on the synchronous motor?

c) What is the effect of increasing the field current on synchronous motor?

d) How is possible to control the synchronous motor speed? Mention about two methods used.