

UNIVERSITY OF SWAZILAND
SUPPLEMENTARY EXAMINATIONS, JULY 2013
FACULTY OF SCIENCE AND ENGINEERING
DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

TITLE OF PAPER: BASIC ELECTRONICS

COURSE NUMBER: EE221

TIME ALLOWED: THREE HOURS

INSTRUCTIONS:


1. There are five questions in this paper. **Answer any FOUR questions.**
 2. Each question carries 25 marks.
 3. Marks for different sections are shown on the right hand margin.
 4. Clearly state **the units** of any values you calculate.
 5. If you think not enough data has been given in any question you may assume any reasonable values.
 6. A sheet containing useful formulae and other information is attached at the end.
-

THIS PAPER IS NOT TO BE OPENED UNTIL PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR

THIS PAPER HAS SEVEN (7) PAGES INCLUDING THIS PAGE

QUESTION 1 (25 marks)

- (a) The forward current in a diode is $32 \mu\text{A}$ when the diode forward voltage drop is 0.5 V , and 4.5 mA when the diode forward drop is 0.72 V . Using the approximate diode equation for a diode in forward bias, find
- (i) The value of the parameter n for the diode. (5 marks)
 - (i) The value of the parameter I_s . (5 marks)
- (b) The forward voltage in a diode which has $n=1$ is increased by 0.06V . By what factor does its forward current change? (5 marks)
- (c) In Fig.Q1c, a source of 100 V r.m.s. supplies a sinusoidal a.c. voltage to a circuit made up of diodes and resistors. Assume that the diodes are ideal.
- (i) Determine the behaviour of the diodes during each half-cycle. (2 marks)
 - (ii) Find the peak current in each of the resistors. (4marks)
 - (iii) Sketch and clearly label the current waveforms in each resistor. (4 marks)

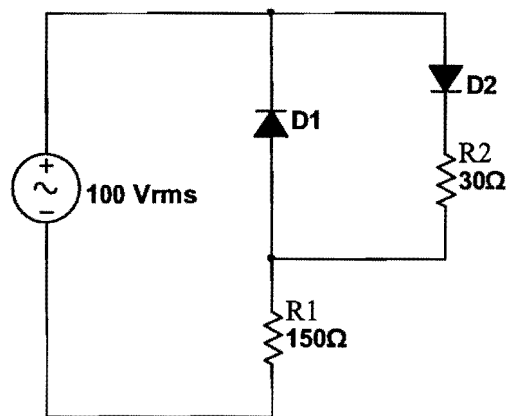**Fig. Q1c**

QUESTION 2 (25 marks)

- (a) (I) Draw the circuit of a mains-operated full-wave diode bridge rectifier with capacitor smoothing. (3 marks)
- (II) A full-wave bridge rectifier is supplied with a voltage $20 \sin 100\pi t$ volts and feeds a load of 100Ω with $C = 2000 \mu\text{F}$. Assuming that the diode voltage drop is 0.7 V and may not be neglected, determine
- (i) The load voltage. (3 marks)
 - (ii) The peak-to-peak ripple voltage. (3 marks)
 - (iii) The peak inverse voltage across each diode. (3 marks)
 - (iv) The peak current in the diodes. (3 marks)
- (b) Figure Q.2b shows a simple application of a zener diode.
- (i) Explain the operation of the circuit. (2 marks)
 - (ii) If R_L is removed from the circuit, find the power dissipated in the diode. (3 marks)
 - (iii) Find the range of R_L during which the zener diode is not conducting. (3 marks)
 - (iv) If a minimum current of 5 mA must be maintained in the zener diode for proper operation of the circuit, find the minimum value of R_L which may be used. (2 marks)

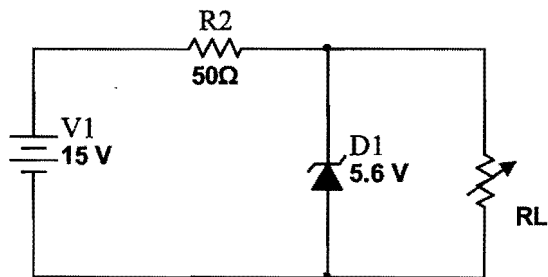


Fig.Q2b

QUESTION 3 (25 marks)

(a) Consider the circuit shown in Fig.Q3a. Determine the quiescent values of base current, collector current and collector-emitter voltage when

- (i) The current gain $\beta = 50$ (6 marks)
 (ii) The current gain $\beta = 300$ (7 marks)
 (iii) Comment on the two results above. (2 marks)

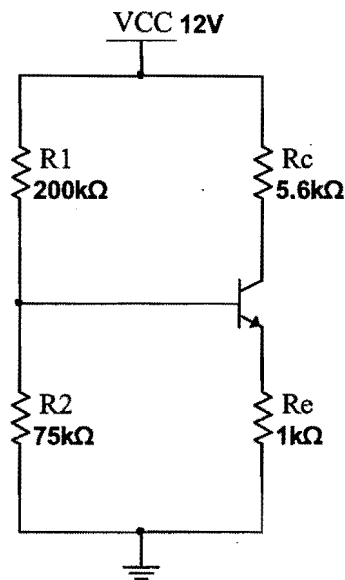


Fig. Q3a

(b) A transistor is biased as shown in Fig.Q3b. Determine the quiescent operating point of the transistor, assuming that $\beta = 100$. (10 marks)

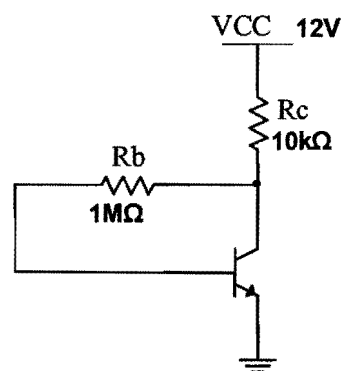


Fig.Q3b

QUESTION 4 (25 marks)

(a) (i) List 3 important characteristics of an ideal opamp. (3 marks)

(ii) Show that the voltage gain of the opamp-based circuit in Fig.Q4a is given by

$$\frac{v_o}{v_{in}} = -\left(\frac{R_4}{R_3}\right)\left(\frac{R_2R_3}{R_1R_2 + R_2R_3 + R_3R_1}\right) \quad (12 \text{ marks})$$

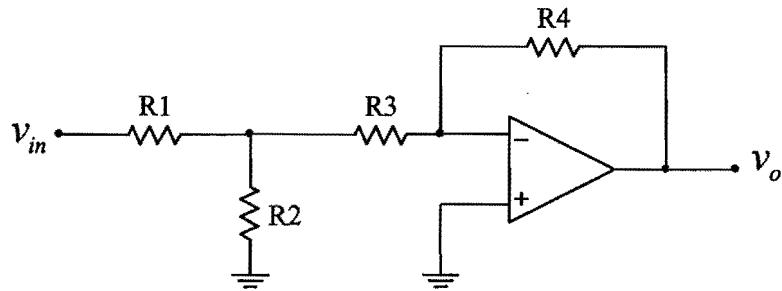


Fig.Q4a

(b) Consider the opamp-based circuit shown in Fig.Q4b.

(i) Show that the output voltage and input voltages are related by

$$v_o = -\frac{1}{RC} \int_0^t (v_1 + v_2) dt \quad (5 \text{ marks})$$

(ii) Hence find the output voltage when $R = 100 \text{ k}\Omega$, $C = 1 \mu\text{F}$, $v_1 = 3 \cos 10t$, $v_2 = 5 \sin 20t$

(5 marks)

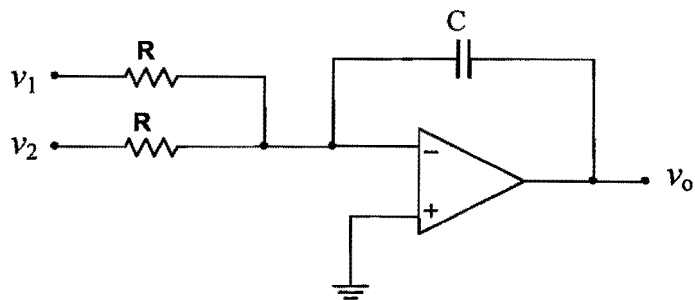


Fig.Q4b

QUESTION 5 (25 marks)

- (a) A transistor with $V_A=75$ V is operated with a collector current of 2 mA and collector-emitter voltage of 10 V. The current gain is 150.
- (i) Find the parameters g_m , r_π , and r_o at this operating point. (5 marks)
 - (ii) Draw the small signal ac equivalent circuit of the transistor. (2 marks)
 - (iii) If the transistor is supplied from a source of internal resistance 400Ω and the effective collector load is $2.7 \text{ k}\Omega$, find the voltage gain of the amplifier. Assume that the base bias resistors are very large compared with other resistors in the circuit. (5 marks)
- (b) A circuit is to be designed which takes an input triangular wave of frequency 500 Hz with its amplitude changing between -5 V to $+5$ V and outputs a bipolar (+ and -) square-wave of same frequency but with amplitude oscillating between -10 V to $+10$ V. The phase relationship is that the square wave is positive whenever the triangular wave is decreasing in amplitude.
- (i) Draw a sketch of the two waveforms and mark the amplitude and time axes. (3 marks)
 - (ii) Draw a suitable opamp-based circuit that can be used to effect the waveform change. (2 marks)
 - (iii) Derive a formula that can help you in your design. (3 marks)
 - (iv) Specify the components of your circuit, assuming all the components used are available in the E12 range. (5 marks)

USEFUL INFORMATION AND FORMULAE

1. E12 Range: 10 12 15 18 22 27 33 39 47 56 68 82
2. Diode:
$$i_D = I_S \left(e^{\frac{v_D}{nV_T}} - 1 \right) \approx I_S e^{\frac{v_D}{nV_T}}$$
3. BJT:
$$i_C = \alpha I_S \left(e^{\frac{v_{BE}}{V_T}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$
4. Half wave rectifier:
$$V_r = \frac{V_m T}{CR_L}, \quad \theta_C = \omega \Delta t = \sqrt{\frac{2V_r}{V_m}}, \quad i_{D\text{ave}} = I_L \left(1 + \pi \sqrt{\frac{2V_m}{V_r}} \right)$$

$$i_{D\text{max}} = I_L \left(1 + 2\pi \sqrt{\frac{2V_m}{V_r}} \right)$$
5. Unless otherwise stated, assume that $V_{BE\text{on}} = 0.7 \text{ V}$, $V_{CE\text{sat}} = 0.2 \text{ V}$ and $V_T = 25 \text{ mV}$.
6. Unless otherwise stated assume that opamps are ideal.