

UNIVERSITY OF SWAZILAND

FACULTY OF SCIENCE

DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING

DIGITAL SYSTEMS I

COURSE CODE – EE322

MAIN EXAMINATION DECEMBER 2012

DURATION OF THE EXAMINATION - 3 HOURS

INSTRUCTIONS TO CANDIDATES

- i. There are FIVE questions in this paper. Answer any FOUR questions only.
- ii. Each question carries equal marks.
- iii. Show all your steps clearly in any calculations.
- iv. State clearly any assumptions made.
- v. Start each new question on a fresh page.

DO NOT OPEN THIS PAPER UNTIL PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR.

Question 1

(a) Using the tabular method, minimize the following Boolean function:

$$F(A, B, C, D) = \sum(1, 3, 4, 5, 10, 11, 12, 13, 14, 15) \quad [12]$$

(b) Simplify the following using a k-map:

(i) $F = abc + cd + a'd + a'b$ [5]

(ii) $F(A,B,C,D) = \sum(1, 3, 5, 7, 9, 15)$ [4]
 $d(A, B, C, D) = \sum(4, 6, 12, 13)$

(c) Using Boolean algebra simplify the following Boolean expression to a minimum number of literals:

$$F = (x'y' + z)' + z + xy + wz \quad [4]$$

Question 2

Analyse the combinational circuit shown in Figure Q2 and determine the following:

(a) Truth table. [12]

(b) Boolean function of the output F. [5]

(c) Timing Diagram showing how change in input relates to change in output with time. [8]

Show all working.

 


Figure Q2: Diagram for question 2

Question 3

- (a) Derive the Boolean expressions for the output sum and output carry in a full adder circuit with inputs x_i , y_i , and c_i . [6]

- (b) Assuming that the *carry propagate* and *carry generate* are defined as

$$P_i = x_i + y_i$$

$$G_i = x_i y_i$$

respectively, show that the output carry and output sum of a full adder becomes

$$C_{i+1} = (C_i G'_i + P'_i)' \quad [8]$$

$$S_i = (P_i G'_i) \oplus C_i \quad [7]$$

- (c) Design a half-subtractor circuit with inputs x and y and outputs D and B . The circuit subtracts the bits $x - y$ and places the difference in D and the borrow in B . [4]

Question 4

Figure 4 shows two devices A and B , which communicate through *Interface I*. Device B takes as input a 3-bit binary number in the range 0_{10} - 5_{10} and outputs a binary number equivalent to the input binary number multiplied by 3. Device B sends its output to Device A . However, Device A only understands information presented in the hexadecimal numbering system. On the one hand, Device B only outputs information presented in the binary numbering system.

 


Figure 4: Diagram for question 4

Design two combinational circuits:

- (a) A circuit for Device B , which ensures that the binary input $I_2 I_1 I_0$ is multiplied by 3.
- (b) A circuit for Interface I , which ensures that data flowing from B to A is interpreted correctly at A . Use only one hexadecimal digit in Device A .

[25]

Question 5

- (a) Using a minimum number of logic gates, design a combinational logic circuit which implements the following mathematical function:

$$f(x, y) = 3x + y$$

WHERE

x and y are 2-bit binary numbers.

[16]

- (b) Implement the following Boolean function with a 4 x 1 multiplexer and external gates. [5]

$$F(A, B, C, D) = \sum(0, 1, 3, 4, 8, 9, 15)$$

- (c) An 8 x 1 multiplexer has inputs A, B, and C connected to the selection inputs S_2 , S_1 , and S_0 , respectively. The data inputs I_0 through I_7 are as follows: $I_1 = I_2 = I_7 = 0$; $I_3 = I_5 = 1$; $I_0 = I_4 = D$; and $I_6 = D'$. Determine the Boolean function that the multiplexer implements. Express this Boolean function in sum-of-products form.

[4]

END OF PAPER