

UNIVERSITY OF SWAZILAND
MAIN EXAMINATION, SECOND SEMESTER MAY 2013

FACULTY OF SCIENCE AND ENGINEERING

**DEPARTMENT OF ELECTRICAL AND ELECTRONIC
ENGINEERING**

TITLE OF PAPER: MICROELECTRONIC CIRCUITS

COURSE CODE: EE523

TIME ALLOWED: THREE HOURS

INSTRUCTIONS:

- 1. There are five questions in this paper. Answer any FOUR questions.
Each question carries 25 marks.**
- 2. If you think not enough data has been given in any question you may
assume any reasonable values.**
- 3. A sheet containing some selected useful formulae is attached at the end.**

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION
HAS BEEN GIVEN BY THE INVIGILATOR**

THIS PAPER CONTAINS SEVEN (7) PAGES INCLUDING THIS PAGE

QUESTION ONE (25 marks)

Consider the IC amplifier shown in Figure-Q1.

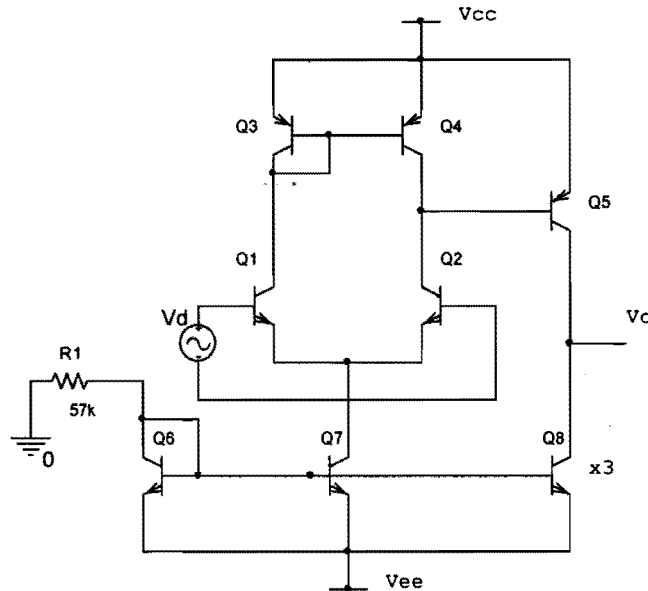


Figure-Q1

You may assume the following data.

$V_{A,PNP} = 70V$	$\beta_{PNP} = 75$	$V_{A,NPN} = 125V$	$\beta_{NPN} = 100$
$V_{CC} = 12V$	$V_{ee} = -12V$	$V_{BE} = 0.6V$	

Calculate the following for this amplifier.

- (a) Quiescent collector currents of the transistors. (3 marks)
- (b) Power dissipation of the amplifier at no signal. (2 marks)
- (c) Signal voltage gain $\frac{V_o}{V_d}$. (10 marks)
- (d) Input impedance and the output impedance. (4 marks)
- (e) Input common mode voltage range. (6 marks)

QUESTION TWO (25 marks)

The block diagram of an uncompensated IC op-amp is shown in Figure-Q(2).

 


Figure-Q2

- (a) Show to which points a capacitor is usually added to have dominant pole compensation. (2 marks)

- (b) If the compensation capacitor is 35pF, find the bandwidth of the op-amp after compensation.

$$R_{do} = 1.5M \quad R_{i2} = 2M \quad A_v = -600$$

Value of G_m is not given intentionally.

(7 marks)

- (c) The DC gain of the op-amp is 100dB and is compensated as in (b).
- (i) What is the bandwidth of the op-amp at unity gain?
- (ii) The compensated op-amp is used with negative feedback to obtain a minimum bandwidth of 15 kHz. Find the limit of the maximum gain available and the feedback factor.

(8 marks)

- (d) The current source in the differential amplifier stage supplies a current of $25\mu A$. If the maximum available output is 12V, calculate the slew rate and the full power bandwidth of the compensated amplifier.

(8 marks)

QUESTION THREE (25 marks)

- (a) Consider the emitter coupled differential pair shown in Figure-Q3.

 


Figure-Q3

The input signal v_1 and v_2 are any voltage signals. Assuming that the transistors $Q1$ and $Q2$ are matched, show the circuit can be used as a multiplier giving

$v_o = kv_x(v_1 - v_2)$, where k is a constant. In how many quadrant/s this multiplier is operational?

(10 marks)

- (b) A multiplier can be assumed to have the input-output relationship $M = kXY$ where X and Y are the inputs and M is the output. The multiplier constant is k . Using this multiplier, show the implementation of the following with justification.

- (i) A frequency doubler.
- (ii) Square root function.
- (ii) A divider.

(15 marks)

QUESTION FOUR (25 marks)

(a) The inverter shown in Figure-Q4 is fabricated in a $1.2\mu m$ CMOS technology.

 


Figure - Q4

You may use the following process parameters and assume usual notation throughout.

$$L_N = L_P = 1.2\mu m \quad W_N = 1.8\mu m \quad k'_n = 70 \frac{\mu A}{V^2}$$

$$k'_p = 25 \frac{\mu A}{V^2} \quad |V_{tp}| = V_{tn} = 0.8V$$

(i) Show that the input threshold voltage V_{th} is given by

$$V_{th} = \frac{a(V_{DD} - |V_{tp}|) + V_{th}}{1+a} \quad \text{where} \quad a = \sqrt{\frac{k'_p \left(\frac{W}{L}\right)_p}{k'_n \left(\frac{W}{L}\right)_n}} \quad (3 \text{ marks})$$

(ii) Calculate V_{th} and W_p if the devices are matched. (2 marks)

(iii) Find the values of V_{IH} , V_{IL} and the noise margins. (4 marks)

(iv) Assuming $W_p = 5.5\mu m$, calculate the output resistance of the inverter when $V_o = V_{OH}$. (3 marks)

(v) If the total effective load capacitance is $25fF$, estimate the propagation delay t_p assuming $W_p = 5.5\mu m$. (3 marks)

(vi) What is the power dissipation of the inverter if the load capacitance is $25fF$ and operated at a frequency of $100MHz$. (2 marks)

(b) Show the implementation of a 3-input NOR gate in CMOS technology. Provide

transistor $\left(\frac{W}{L}\right)$ ratios in a $0.25\mu m$ process if $n = 2$ and $p = 5$.

(8 marks)

QUESTION FIVE (25 marks)

- (a) A switched capacitor circuit is shown in Figure-Q5(a), which is driven by the two phase clock ϕ_1 and ϕ_2 with a cycle time of T_C .

 


Figure - Q5(a)

- (i) Derive expressions for $\frac{v_o}{v_{in}}$ and R_{eq} . (7 marks)
- (ii) Show how you can get an inverted output v_o using the same circuit. (3 marks)
- (b) A circuit of an active low pass filter is shown in Figure-Q5(b).

 


Figure-Q5(b)

The transfer function of the circuit is given by
$$-\frac{1}{R_3 R_1 C_5 C_6 \left(s^2 + \frac{s}{C_5 R_2} + \frac{1}{C_5 C_6 R_3 R_4} \right)}$$

- (i) Find the switched capacitor equivalent for this circuit using only two op-amps. Mark the clocks ϕ_1 and ϕ_2 clearly on the diagram. (5 marks)
- (ii) Calculate the capacitor values of your implementation to have a 3dB cutoff frequency of 10KHz when operating with a 100KHz clock. You may assume, $R_3 = R_4$ and, $C_5 = C_6 = 10pF$ $Q = \frac{1}{\sqrt{2}}$ $K = 1$ $\omega_{3dB} = \omega_0$ (10 marks)

SOME SELECTED USEFUL FORMULAE

MOSFET Equations:

$$i_D = k'_n \frac{W}{L} \left[(v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right] \quad \text{in triode region}$$

$$i_D = \frac{1}{2} k'_n \frac{W}{L} (v_{GS} - V_t)^2 \quad \text{in saturation region}$$

Ebers-Moll Equation for i_C :

$$i_C = I_S (e^{v_{BE}/V_T} - 1) - \frac{I_S}{\alpha_R} (e^{v_{BC}/V_T} - 1)$$

Basic Inverter:

$$t_{PHL} = \frac{2C}{k'_n \left(\frac{W}{L}\right)_n (V_{DD} - V_{t,n})} \left[\frac{V_{t,n}}{(V_{DD} - V_{t,n})} + \frac{1}{2} \ln \left(\frac{3V_{DD} - 4V_{t,n}}{V_{DD}} \right) \right]$$

Low Pass Filter:

$$\text{Transfer Function} = \frac{K \omega_0^2}{s^2 + \left(\frac{\omega_0}{Q}\right)s + \omega_0^2}$$