

UNIVERSITY OF SWAZILAND
Faculty of Science and Engineering
Department of Electrical and Electronic Engineering
Supplementary Examination 2015

Title of Paper : **Analogue Design II**
Course Code : **EE323**
Time Allowed : **3 hrs**

Instructions:

1. Answer **all** four (4) questions
2. Each question carries 25 marks

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION HAS BEEN
GIVEN BY THE INVIGILATOR**

The paper consists of five (5) pages including the cover page

Question 1 [25]

- a) Fill in the blank(s) with appropriate word(s) [10]
- i) A MOSFET is a _____ controlled _____ carrier device.
 - ii) Enhancement type MOSFETs are normally _____ devices while depletion type MOSFETs are normally _____ devices.
 - iii) The Gate terminal of a MOSFET is isolated from the semiconductor by a thin layer of _____.
 - iv) The MOSFET cell embeds a parasitic _____ in its structure.
 - v) The gate-source voltage at which the _____ layer in a MOSFET is formed is called the _____ voltage.
 - vi) The thickness of the _____ layer remains constant as gate source voltage is increased beyond the _____ voltage.
- b) Determine the voltage gain, input and output impedance with feedback for voltage series feedback having $A = -100$, $R_i = 10k\Omega$, $R_o = 20k\Omega$ for feedback of $\beta = -0.1$. [9]
- c) List out two characteristics of feedback amplifier. [2]
- d) How does an oscillator differs from an amplifier [2]
- e) Name two low frequency oscillators [2]

Question 2 [25]

- a) The feedback amplifier shown in figure 2.1 makes use of an op – amp with an open – loop gain $A = 10^5$.

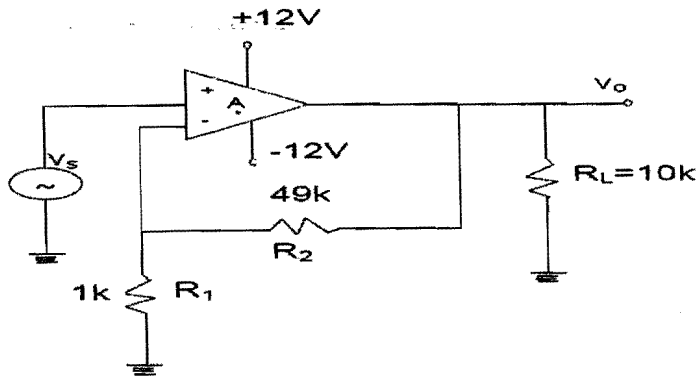


Figure 2.1

- i) How much is the output voltage (v_o) for input signal $v_s = 2\text{ mV}$ in the circuit shown [6]
- b) Figure 2.2 shows an op – amp circuit with voltage series through R_1 and R_2 . The open – loop gain of the op – amp is $A = 10^4$ and input impedance is $100\text{K}\Omega$.

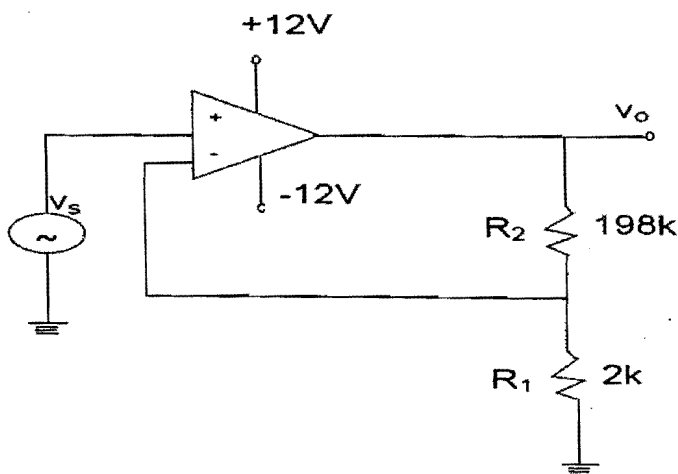


Figure 2.2

- i) Find the gain and input impedance of the amplifier with feedback. [8]

- c) An amplifier has a bandwidth of **500 KHz** and an open voltage gain of **100**.
- i) What should be the amount of negative feedback (β) if the bandwidth is extended to **5 MHz**? [5]
 - ii) What will be the new gain after negative feedback is introduced? [1]
- d) Design a **Wien-bridge oscillator** using op-amp to generate a sinusoidal waveform of frequency **1 KHz**. [5]

Question 3 [25]

a) For the circuit of figure 3.1.

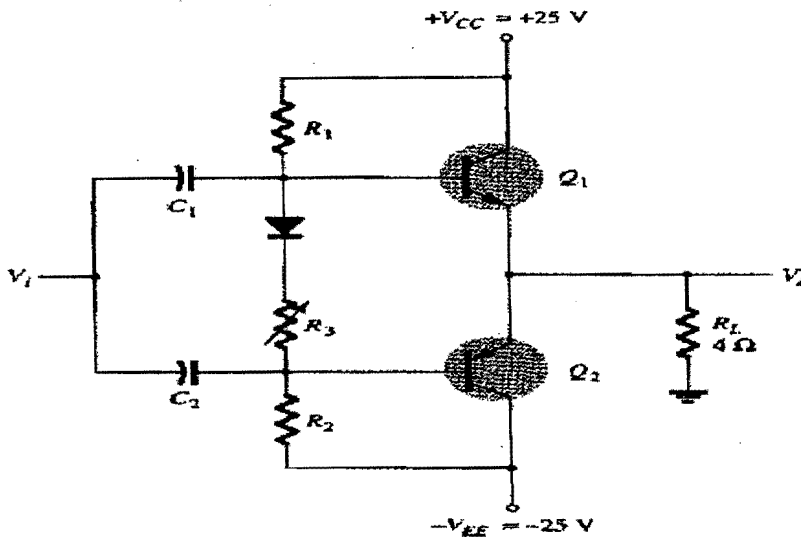


Figure 3.1

- i) Calculate the:
 - Output power [2]
 - Input power [2]
 - Power handled by each output transistor [2]
 - Circuit efficiency for an input of $12 V_{rms}$ [1]
 - ii) Calculate the:
 - Maximum input power [2]
 - Maximum output power [2]
 - Input voltage for maximum power operation [2]
 - Power dissipated by the output transistors at this [2]
 - iii) Calculate the maximum power dissipated by the output transistors and the voltage at which this occurs [4]
- b) For the Harmonic Distortion reading: $D_2 = 0.1, D_3 = 0.02,$ and $D_4 = 0.01,$ with $I_1 = 4 A$ and $R_c = 8\Omega$. Calculate the:
- i) Total Harmonic Distortion [2]
 - ii) Fundamental power component [2]
 - iii) Total power [2]

Question 4 [25]

- a) Determine the following parameters: I_{DQ} , V_{DSQ} , $V_{DS(sat)}$, g_m , r_o and A_v of a MOSFET circuit. The circuit in figure 4.1 assumes the following parameters: $V_{GSQ} = 2.12V$, $V_{DD} = 5V$, $V_{GS} = 1.82V$ and $R_D = 2.5K\Omega$. The transistor parameters are $V_{TN} = 1V$, $k_n = 0.80mA/V^2$ and $\lambda = 0.02V^{-2}$. Assume the transistor is biased in the saturation region. [14]

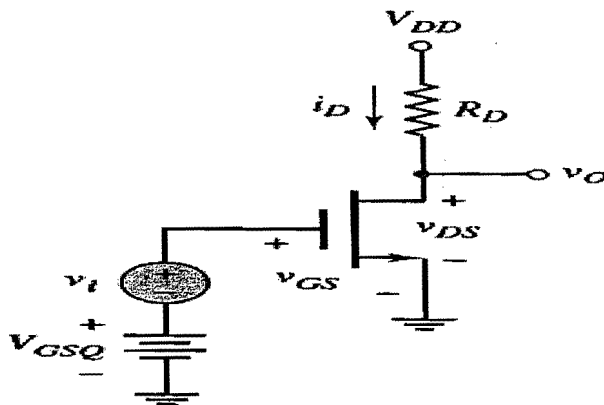


figure 4.1

- b) For the circuit below (figure 4.2) determine: R_{Thi} , C_i and f_{Hi} . Where $A_v = -3$, $C_G = 0.01\mu F$, $C_c = 0.5\mu F$, $C_s = 2\mu F$, $C_{gd} = 2pF$, $C_{gs} = 4pF$. [11]

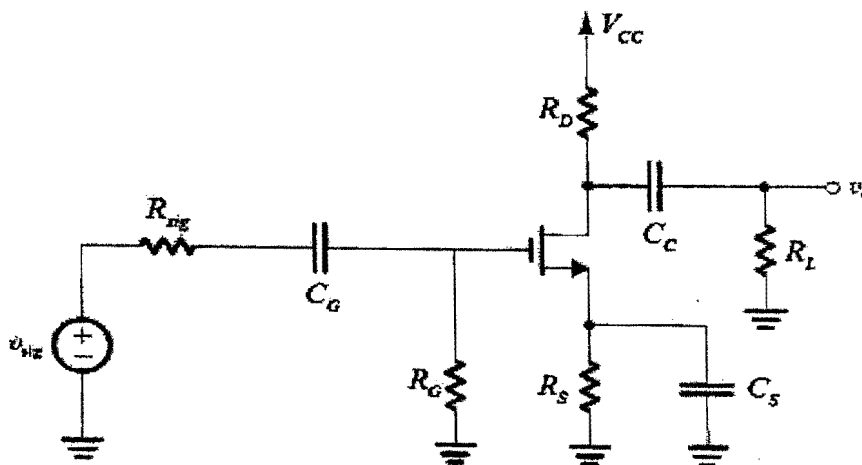


figure 4.2