

Faculty of Science
Department of Electrical and Electronic Engineering
Supplementary Examination 2016

Title of Paper : **Digital Systems I**

Course Number : **EE322**
University of Swaziland

Time Allowed : **3 hrs**

Instructions :

- 1. Answer all four (4) questions**
- 2. Each question carries 25 marks**

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION HAS
BEEN GIVEN BY THE INVIGILATOR**

The paper consists of six (6) pages including the cover page

Question 1 [25]

a) Convert the following decimal numbers to the base indicated

- i. 7562 to octal [2]
- ii. 1938 to hexadecimal [2]
- iii. 175 to binary [1]

b) Show the following operations using 2's complement:

- i. $1011001 - 1000011$ [2]
- ii. $0.1001 - 0.0101$ [3]

c) Using postulates and theorems of Boolean algebra, reduce the combinational circuit in figure 1.1 to a minimum number of literals. Draw the circuit using one gate. [15]

 


figure 1.1

Question 2 [25]

a) What do you understand about the following terms as used in digital design:

- i) Encoder [1]
- ii) Decoder [1]
- iii) Multiplexer [1]
- iv) Demultiplexer [1]
- v) Combinational circuit [2]
- vi) Sequential circuit [2]
- vii) Magnitude comparator [2]

b) A BCD-to-seven-segment decoder is a combinational circuit that converts a decimal digit in BCD to an appropriate code for the selection of segments in a display indicator used for displaying the decimal digit in a familiar form. The seven outputs of the decoder (*a, b, c, d, e, f, g*) select the corresponding segments in the display, as shown in Figure 2.1. The numeric display chosen to represent the decimal digit is shown Figure 2.2. Design this decoder using a minimum number of gates. The six invalid combinations should result in a blank display. [15]

 


figure 2.1

 


figure 2.2

Question 3 [25]

a) Implement the following Boolean function with a multiplexer:
 $F(A, B, C, D) = (0, 1, 3, 4, 8, 9, 15)$ [10]

b) From the following state diagram, create the next state table, output, and flip flop excitation equations for a J/K flip-flop implementation using a 1-hot encoding. [15]


 
 


figure 3.1

Question 4 [25]

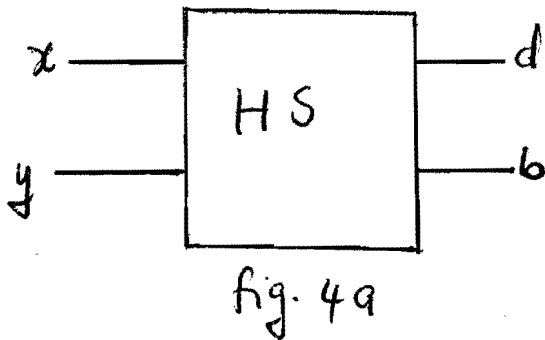- a) The graphical symbols of a half-subtractor (HS) and a full-subtractor (FS) for computing $b, d = x - y$, where b stands for borrow and d stands for difference are shown below:



- i) Derive the truth table and minimal cost Sum of Product (SOP) implementation for the HS. [4]
- ii) Derive the truth table and a minimal cost SOP implementation for the FS [7]
- iii) Show how to build a FS from two HS blocks and an additional gate. [5]

b) Draw a circuit using *AND*, *OR*, and *NOT* gates to implement the function f specified by the truth table shown below. Try to minimize the number gates used.

[9]

<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i>
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0