

University of Swaziland
Faculty of Science
Department of Electrical and Electronic Engineering
Supplementary Examination 2016

Title of Paper : **Analogue Design II**
Course Number : **EE323**

Time Allowed : **3 hrs**

Instructions :

- 1. This paper contains five (5) questions**
- 2. Answer all questions**
- 3. Each question carries 20 marks**

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION HAS
BEEN GIVEN BY THE INVIGILATOR**

The paper consists of six (6) pages

Question 1 [20]

- a) Define the following terms: [5]
- i) Feedback
 - ii) Sensitivity
 - iii) Barkhausen Criterion
 - iv) Oscillator
 - v) Power Amplifier Efficiency

- b) Give the effect of negative feedback on amplifier characteristics [8]
NB: Use *increase* and *decrease* to complete the table below

Characteristics	type of feedback			
	Current-series	voltage-series	voltage-shunt	current-shunt
Gain				
Bandwidth				
Input resistance				
Output resistance				

- c) Design a *Wien-bridge oscillator* using op-amp to generate a sinusoidal waveform of frequency *1 KHz*. [7]

Question 2 [20]

For a series-series feedback BJT amplifier shown in *Figure 2.1*. The input variable is the voltage v_1 and the output variable is the voltage v_2 . Assume $\beta = 100$, $r_\pi = 2.5K\Omega$, $\alpha = \frac{\beta}{1+\beta}$, $r_e = \frac{\alpha}{g_m}$, $r_0 = \infty$, $r_x = 0$, $V_T = 25mV$, $R_1 = 100\Omega$, $R_2 = 1K\Omega$, $R_3 = 20K\Omega$ and $R_4 = 10K\Omega$

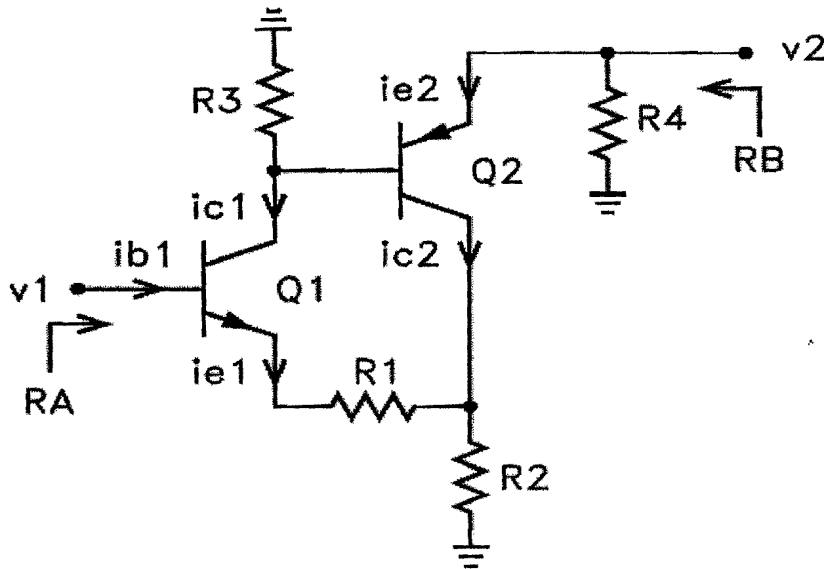


Figure 2.1

- a. Redraw the circuit on *Figure 2.1* with the feedback path removed. [2]
NB: your diagram should be clearly labelled.

- b. Calculate the:
 - i. Transconductance $\frac{ie2}{v1}$ [6]
 - ii. Voltage gain $v2/v1$ [4]
 - iii. Input resistance R_A [4]
 - iv. Output resistance R_b [4]

Question 3 [20]

a) For the circuit of *Figure 3.1*.

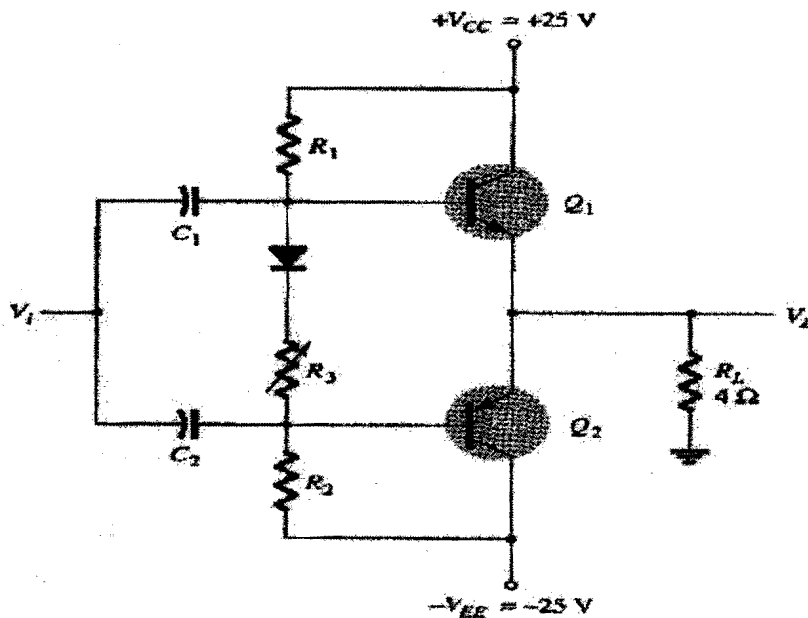


Figure 3.1

- i) Calculate the:
 - Output power [2]
 - Input power [2]
 - Power handled by each output transistor [2]
 - Circuit efficiency for an input of $12 V_{rms}$ [1]
 - ii) Calculate the:
 - Maximum input power [1]
 - Maximum output power [1]
 - Input voltage for maximum power operation [1]
 - Power dissipated by the output transistors at this [1]
 - iii) Calculate the maximum power dissipated by the output transistors and the voltage at which this occurs [4]
- b) For the Harmonic Distortion reading: $D_2 = 0.1, D_3 = 0.02, \text{ and } D_4 = 0.01, \text{ with } I_1 = 4 A \text{ and } R_c = 8\Omega$. Calculate the:
- i) Total Harmonic Distortion [2]
 - ii) Fundamental power component [2]
 - iii) Total power [1]

Question 4 [20]

Figure 4.1 shows a series-shunt amplifier in which the three MOSFETs are sized to operate at $|V_{ov}| = 0.2\text{ V}$. Let $|V_t| = 0.5\text{ V}$ and $|V_A| = 10\text{ V}$. The current source utilizes single transistors and thus have output resistances equal to r_0 .

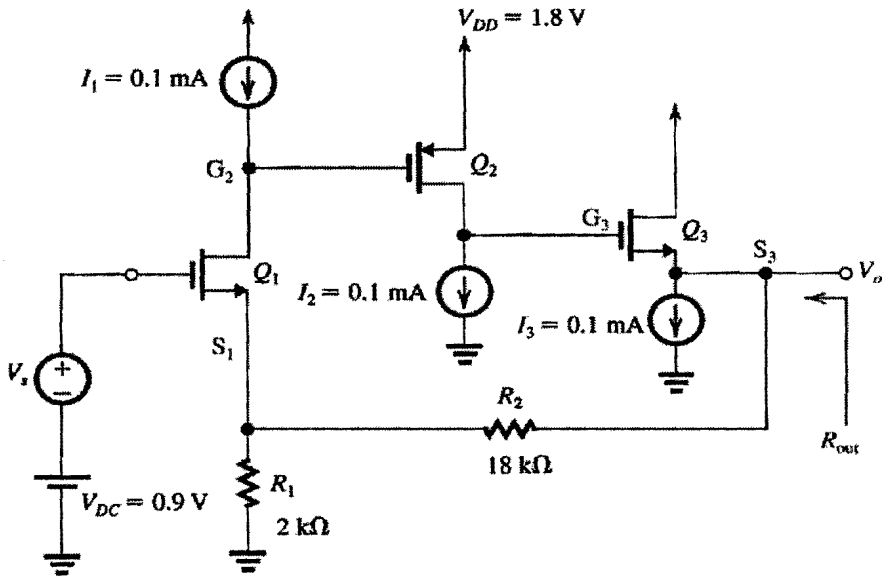


Figure 4.1

- Assume the loop gain to be large, what do you expect the closed loop voltage $\frac{v_o}{v_s}$ to be approximately? [1]
- If V_s has a zero dc component, find the dc voltages at nodes S_1 , G_2 , S_3 , and G_3 [4]
- Find the open – loop gain circuit. Calculate the gain of each of the three (3) stages and the overall voltage gain, A [15]

Question 5 [20]

- a) Fill in the blank(s) with appropriate word(s) [10]
- A MOSFET is a _____ controlled _____ carrier device.
 - Enhancement type MOSFETs are normally _____ devices while depletion type MOSFETs are normally _____ devices.
 - The Gate terminal of a MOSFET is isolated from the semiconductor by a thin layer of _____.
 - The MOSFET cell embeds a parasitic _____ in its structure.
 - The gate-source voltage at which the _____ layer in a MOSFET is formed is called the _____ voltage.
 - The thickness of the _____ layer remains constant as gate source voltage is increased beyond the _____ voltage.

- b) Determine the small-signal voltage gain, input and output resistances of a common-source amplifier. For the circuit shown in *Figure 5.1*, the parameters are: $V_{DD} = 10V$, $R_1 = 70.9K\Omega$, $R_2 = 29.1K\Omega$ and $R_D = 5K\Omega$. The transistor parameters are: $V_{TN} = 1.5V$, $K_n = 0.5mA/V^2$, and $\lambda = 0.01V^{-1}$. Assume $R_{Si} = 4K\Omega$ and $g_m = 2k_n(V_{GSQ} - V_{TN})$

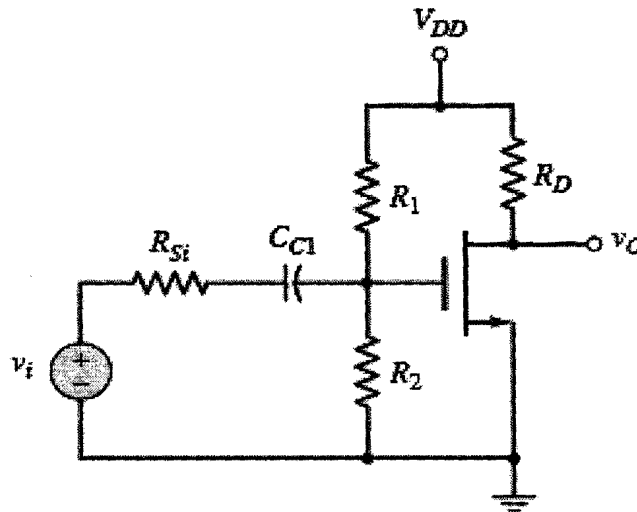


Figure 5.1