

**UNIVERSITY OF SWAZILAND
SUPPLIMENTERY EXAMINATION**

JULY 2016

FACULTY OF SCIENCE AND ENGINEERING

**DEPARTMENT OF ELECTRICAL AND ELECTRONIC
ENGINEERING**

TITLE OF PAPER: ANALOGUE DESIGN III

COURSE CODE: EE421

TIME ALLOWED: THREE HOURS

INSTRUCTIONS:

- 1. There are five questions in this paper. Answer any FOUR questions.
Each question carries 25 marks.**
- 2. If you think not enough data has been given in any question you may
assume any reasonable values.**
- 3. Some useful formulas are given in the last page.**

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION
HAS BEEN GIVEN BY THE INVIGILATOR**

THIS PAPER CONTAINS SEVEN (7) PAGES INCLUDING THIS PAGE

QUESTION ONE (25 marks)

A differential amplifier using BJTs, is shown in Figure-Q1.

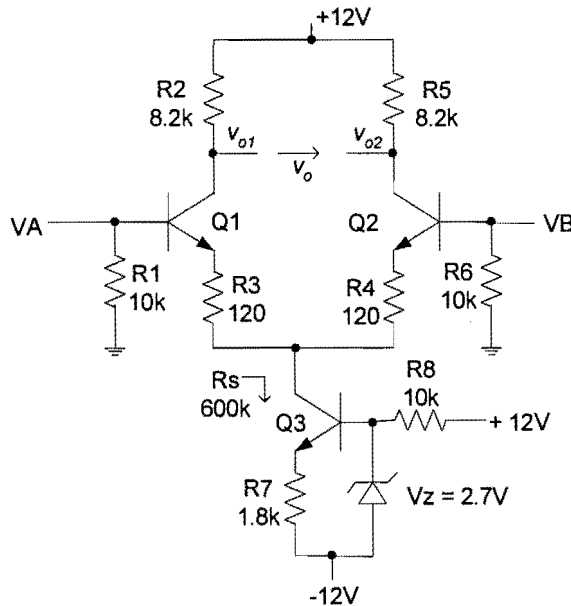


Figure-Q1

- (a) Calculate the collector current and collector voltage of each transistor at no signal. Assume that the transistors are of high gain type and matched.

(6 marks)

- (b) A signal source v_d is differentially connected to the inputs, such that $v_d = v_A - v_B$. Draw the differential half circuits for the mid-band signals and find the voltage gains $\frac{v_{o1}}{v_d}$, $\frac{v_{o2}}{v_d}$ and $\frac{v_o}{v_d}$, deriving any formula you use.

(8 marks)

- (c) Calculate the differential input resistance of the amplifier, assuming $\beta_{Q1} = \beta_{Q2} = 100$.

(5 marks)

- (d) If $V_A = V_B = 0$, find the value of $|V_o|$, assuming the following data.

Tolerance of R_2 and $R_5 = \pm 5\%$

Tolerance of scale current = $\pm 10\%$

You may neglect the tolerances related to other components.

(6 marks)

QUESTION TWO (25 marks)

Consider the NMOS amplifier shown in Figure-Q2. The devices Q_1 and Q_2 are matched.

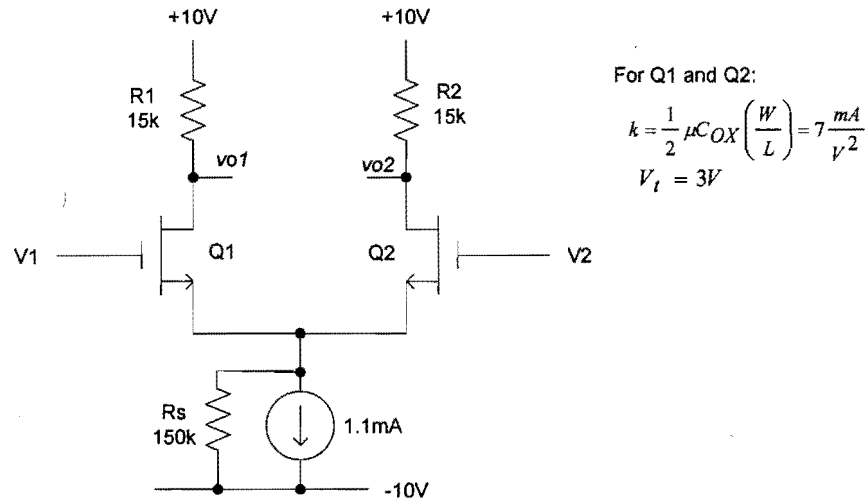


Figure - Q2

- (a) When a differential voltage V_D is applied to the input, the value of $I_{D2} = 1.1mA$. Find the value of V_D , if $V_D = V_1 - V_2$. You may assume standard notation. (5 marks)
- (b) Draw the common mode half circuit for a single ended output. Assuming $V_1 = V_2$, calculate the common mode gain for a single ended output proving any formula you used. (8 marks)
- (c) Calculate the CMRR in dB for the part (b) above. (7 marks)
- (d) Find the numerical value of the common mode gain when the outputs are taken differentially, with the tolerances of resistors being $\pm 5\%$. (5 marks)

QUESTION THREE (25 marks)

- (a) A circuit of a current source implemented with BJTs is shown in Figure-Q3(a), where the devices are matched and of high gain type.

(i) Show that $I_o = I_{ref} e^{-\frac{I_o R}{V_T}}$, assuming standard notation

(6 marks)

- (ii) Find the component values if the output current is $200\mu A$. You may use the following data.

$V_{CC} = 12V$

$V_{BE1} = 0.6V$

$I_{ref} = 1.2mA$

(6 marks)

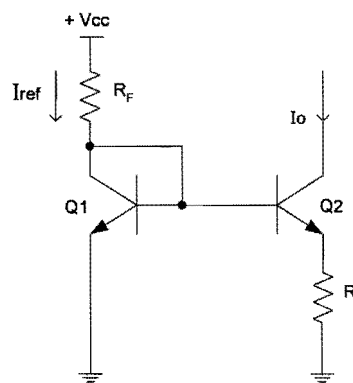


Figure - Q3(a)

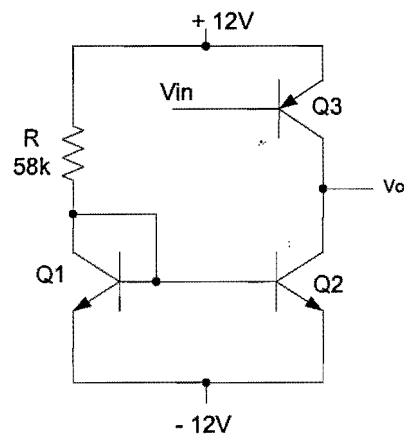


Figure-Q3 (b)

- (b) An IC amplifier is shown in Figure-Q3(b). The transistors are of high gain type while Q_1 and Q_2 are matched.

(i) Find the emitter current of Q_3 .

(4 marks)

(ii) Derive an expression for the voltage gain $\frac{v_o}{v_{in}}$ and calculate its value. Assume that the

$V_A = 75V$.

(5 marks)

- (iii) What is the voltage gain if this amplifier drives an external load of $25k$ connected to the output through a large capacitor?

(4 marks)

QUESTION FOUR (25 marks)

- (a) An amplifier implemented in CMOS technology is shown in Figure-Q4(a), having the following data.

$$K_1 = 8 \frac{mA}{V^2} \quad K_2 = 4 \frac{mA}{V^2} \quad K_3 = 6 \frac{mA}{V^2}$$

$$|V_t| = 2V \quad |V_A| = 60V$$

- (i) Calculate the bias voltage V_i required at the input. (4 marks)

- (ii) Derive an expression for the voltage gain $\frac{v_o}{v_i}$ and calculate its value. (5 marks)

- (iii) Determine the maximum and minimum signal limits of v_o . (4 marks)

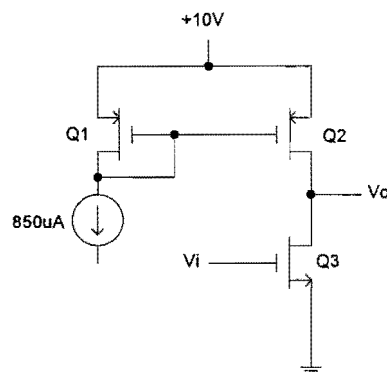


Figure-Q4(a)

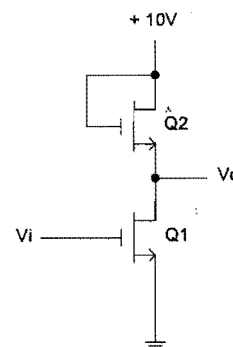


Figure-Q4(b)

- (b) An enhancement type NMOS amplifier is shown in Figure-Q4(b). You may assume the following data with respect to this circuit.

$$L_1 = 10\mu m \quad L_2 = 20\mu m \quad W_1 = 800\mu m \quad W_2 = 10\mu m$$

$$V_t = 2V \quad \mu C_{OX} = 200 \frac{\mu A}{V^2} \quad V_A = 80V$$

- (i) Find the dc voltage to be applied at the input, such that the value of $V_o = 6V$. What is the current flowing in Q_2 ? (6 marks)

- (ii) Draw the ac equivalent circuit for mid-band signals and hence calculate the mid band voltage gain. (6 marks)

QUESTION FIVE (25 marks)

A cascode amplifier is shown in Figure-Q5.

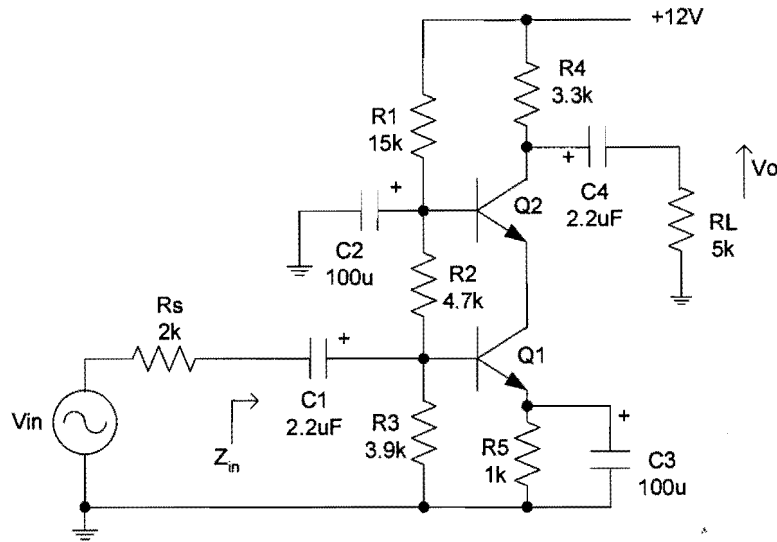


Figure-Q5

- (i) Find the voltages at the terminals of two transistors under no signal. You may assume that the transistors are identical and of high gain type.
- (8 marks)
- (ii) Derive an expression for the mid-band gain $\frac{v_o}{v_{in}}$, and find its value. Assume that the $\beta = 100$ and the Early effect is negligible.
- (11 marks)
- (iii) Find an expression with numerical values, for the input impedance $Z_{in}(\omega)$ at high frequency signals.

(6 marks)

1. SOME USEFUL MOSFET EQUATIONS

$$i_D = \mu_n C_{ox} \frac{W}{L} \left[(v_{GS} - v_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right] \text{ in triode region}$$

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - v_t)^2 \text{ in saturation region}$$

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - v_t)^2 (1 + \lambda v_{DS}) \text{ in saturation region with Channel Modulation effect}$$

$$V_A = \frac{1}{\lambda}$$

2. Unless otherwise stated $V_{BE(ON)} = 0.6V$ and $V_T = 0.025V$.