

UNIVERSITY OF SWAZILAND
MAIN EXAMINATION, SECOND SEMESTER MAY 2016
FACULTY OF SCIENCE AND ENGINEERING
DEPARTMENT OF ELECTRICAL AND ELECTRONIC
ENGINEERING

TITLE OF PAPER: POWER ELECTRONICS

COURSE CODE: EE422

TIME ALLOWED: THREE HOURS

INSTRUCTIONS:

- 1. There are five questions in this paper. Answer any FOUR questions. Each question carries 25 marks.**
- 2. If you think not enough data has been given in any question you may assume any reasonable values.**

THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR

THIS PAPER CONTAINS SIX (6) PAGES INCLUDING THIS PAGE

QUESTION ONE (25 marks)

A power transistor used in a convertor switches a load current of 45A with a supply voltage of 250Vdc. The load can be assumed as inductive with a clamping diode. The transistor is driven by a 25kHz square wave signal having a duty cycle of 50%. Assume the following device parameters which are given using usual notation.

$$t_{d(on)} = t_{d(off)} = 120ns \quad t_{ri} = t_{fi} = 200ns \quad t_{rv} = t_{fv} = 150ns$$

$$V_{CE(sat)} = 1.2V \quad \theta_{jc} = 0.5^{\circ} \frac{C}{W} \quad T_{j(max)} = 150^{\circ}C$$

- (i) Draw the collector emitter-voltage and collector current wave forms for one switching cycle marked with relevant parameters.

(5 marks)

- (ii) Calculate the energy dissipated in the transistor during one switching cycle and hence the device power loss.

(10 marks)

- (iii) If the transistor is mounted on a heat sink, find its required thermal specifications.

Assume that the maximum ambient temperature is 40°C and the thermal resistance of the mounting accessories is 0.2°C/W.

(6 marks)

- (iv) Calculate the temperature of the transistor case and the heat sink under steady state of operation for the conditions stated in (iii) above.

(4 marks)

QUESTION TWO (25 marks)

- (a) An IGBT is used to switch an inductive load as shown in Figure-Q2. You may assume that the load current is fairly constant.

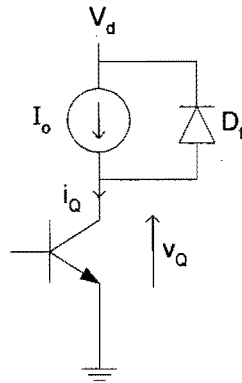


Figure - Q2

- (a) Show the circuit of a turn off snubber which can be used with this IGBT switch. Draw the voltage and current waveforms modified by the snubber if optimum conditions are applied. (4 marks)
- (b) With respect to the circuit in (a) above, derive expressions for the turn-off power loss in the IGBT and in any other components. (8 marks)
- (c) Design the snubber circuit assuming optimum conditions, for the following data. (7 marks)
- $$t_{d(on)} = t_{d(off)} = \text{negligible} \quad t_{fi} = 500\text{ns}$$
- $$V_d = 150\text{V} \quad I_o = 15\text{A} \quad \text{Duty ratio} = 50\%$$
- $$\text{Switching frequency} = 100\text{kHz}$$
- (d) Using the data given in (c) above, calculate the turn-off power loss in the IGBT and in the snubber circuit. What is the turn-off $\frac{dv}{dt}$ value? (6 marks)

QUESTION THREE (25 marks)

A fully controlled single phase bridge circuit is connected to a separately excited dc motor as shown in Figure-Q3. Assume that the motor is operating in the inverting mode for regeneration.

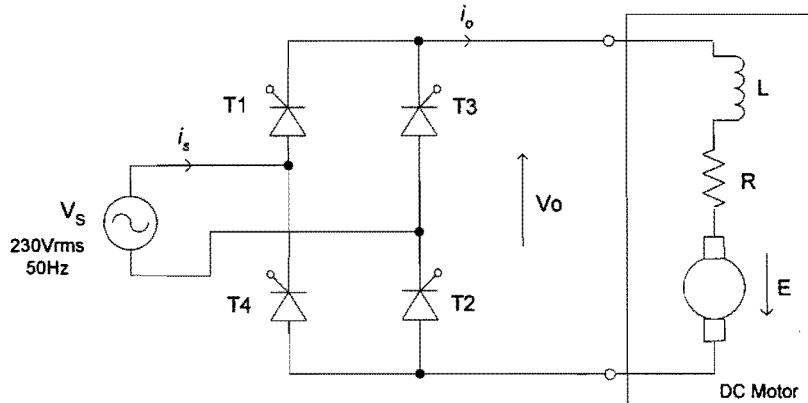


Figure-Q3

The speed of the motor is $150 \frac{\text{rad}}{\text{s}}$ and the torque applied is 12 Nm . Some parameters related to the armature are,

$$L = 0.05 \text{ H} \quad R = 2 \Omega \quad \text{torque constant} = 1 \frac{\text{Nm}}{\text{A}} \quad \text{voltage constant} = 1 \frac{\text{V}}{\text{rad/s}}$$

While operating in the inverter mode and assuming that the armature current is continuous,

- (a) Draw the following waveforms with reference to V_s .
 - (i) Motor terminal voltage v_o .
 - (ii) Armature current i_o . (4 marks)
- (b) Derive an expression for i_o . (5 marks)
- (c) Derive an expression for the average value of v_o . Hence find the required delay angle for the given operating point. (8 marks)
- (d) Justify the initial assumption of 'continuous current'. (4 marks)
- (e) Find the power transferred to the ac supply and the power losses in the system if the thyristors are ideal. (4 marks)

Note:
$$i = \frac{V_m}{Z} [\sin(\omega t - \theta)] + \frac{E}{R} + A e^{-\frac{t}{\tau}} \quad \text{where,}$$

$$Z = \sqrt{R^2 + (\omega L)^2} \quad \theta = \tan^{-1} \left(\frac{\omega L}{R} \right) \quad \tau = \frac{L}{R} \quad A = \text{constant}$$

QUESTION FOUR (25 marks)

A three phase fully controlled full wave rectifier connected to an R-L load is shown in FigureQ4.

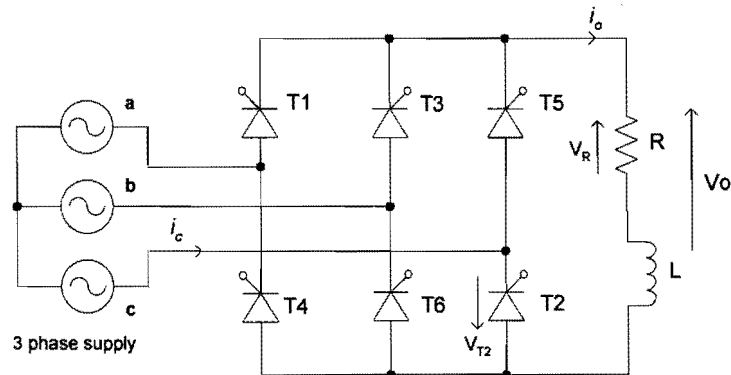


Figure-Q4

The three phase supply is $410V_{rms,L-L}$, $50Hz$ and the load is $R = 8\Omega$ in series with $L = 75mH$. Assume that the phase sequence is $a b c$ and the output current is ripple free.

- (a) Derive an expression for the average load voltage if the delay angle is ' α '. (3 marks)
- (b) What is the positive peak value of the output voltage? Calculate the delay angle for an average output voltage of $350V$. (3 marks)
- (c) Draw the following waveforms on the sheets provided at the end of the paper. You may assume that the operating conditions are, as in (b) above.
 - (i) Output voltage v_o and the voltage v_R . (3 marks)
 - (ii) Currents in the thyristors T_2 and T_5 . (4 marks)
 - (iii) Phase current and the phase voltage of 'phase c'. (3 mark)
 - (iv) Voltage v_{T2} , across the thyristor T_2 . (4 marks)
- (d) Find the values of the following with respect to this convertor assuming the conditions given in (b).
 - (i) Value of the rms current in the thyristor T_5 and in 'phase c'. (3 marks)
 - (ii) Power dissipated in the load. (2 marks)

QUESTION FIVE (25 marks)

A dc to dc buck converter is shown in Figure-Q5. It is operating at a switching frequency of f_s with a duty ratio of D .

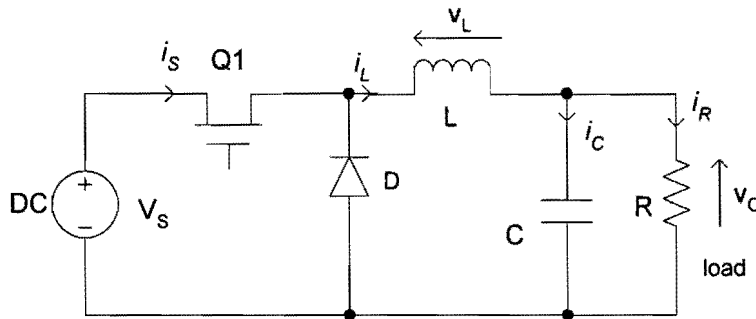


Figure-Q5

- (a) Assuming that C is large, draw the waveforms of v_L and i_L . (2 marks)
- (b) If V_o can be assumed as constant show that the duty factor D is given by $\left[1 - \frac{|\Delta i_L| L f_s}{V_o}\right]$, where Δi_L is the peak to peak variation of the inductor current. (5 marks)
- (c) Derive an expression for the amplitude of the ripple voltage at the output. (5 marks)
- (d) Some of the data related to this converter are given below.
 $V_s = 60V$ $V_o = 48V$ $f_s = 50KHz$ $R = 15\Omega$
 Using these values, calculate the following.
- (i) The Duty factor. (2 marks)
- (ii) Value of L , to have a peak to peak variation of i_L a 10% of the average load current. What is the maximum value of the current in the inductor? (4 marks)
- (iii) Value of C , to have a peak to peak variation of v_o a 5% of the average load voltage. (2 marks)
- (e) Calculate the value of the average source current. (5 marks)

Question Four

Reg No:

