

UNIVERSITY OF SWAZILAND
FACULTY OF SCIENCE
Department of Electrical and Electronic Engineering

July 2016
SUPPLEMENTARY EXAMINATION

Title of the Paper:
Electrical Machines

Course Number: EE451
Time Allowed: Three Hours.

Instructions:

1. Answer all questions, no choice.
2. The answer must be written in the space provided in the question book. Use the answer book as a scratch pad. Both the question and answer book must be marked with ID and name and handed in as well.
3. This paper has 6 pages, including this page.

**DO NOT OPEN THE PAPER UNTIL
PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR.**

Q1, (20pts): A 75-KVA 24000:400-V 3- ϕ transformer, Δ -Y connected is under a performance test. A short-circuit test gives the instrument readings: 480V, 1.804A, and 620W. An open-circuit test gives instrument readings: 400V, 5.4A, and 580W. Find:

- (i). the copper loss and the iron loss.
- (ii). the series parameters of the transformer
- (iii). the parallel parameters of the transformer
- (iv). draw the equivalent circuit in pu of this transformer.

Q2, (20 pts): Given a 3- ϕ , Y connected induction motor is rated at 380 V, 15 KW, 50Hz, and 4-pole. The friction windage and core loss is assumed to be a constant independent of load at 400 W. The motor is operated under rated terminal voltage and frequency. The motor constants are:

$$R_1=0.6, R_2=0.3, X_1=2.7, X_2=0.5, \text{ and } X_M=27 \Omega$$

Evaluate the performance at a rated slip of 5%:

- (i). motor speed,
- (ii). stator current,
- (iii). out put shaft torque and power,
- (iv). motor power factor and efficiency.

Q3, (20 pts): A synchronous generator is rated: 100 MVA, 11.5 KV, 50 Hz, 2-pole, and Y connected. It has a synchronous reactance of 0.8 pu and armature resistance of 0.01.

- (i). When field over-excited, operating at a leading power factor, sketch the phasor diagram, relating V_a , I_a and E_a . Mark explicitly the angle ϕ and δ .
- (ii). When feed to a load at rated conditions and a power factor 0.8 lagging, find the generated internal voltage E_a ,
- (iii). torque angle δ , and
- (iv). prime mover torque required.

- Q4, (20 pts):** A 220 V shunt DC motor runs on no-load at 1600 rpm. The no-load current is 8 A. The armature circuit resistance is 0.25Ω and shunt field resistance is 220Ω . Calculate:
- (i). the armature no load current,
 - (ii). the counter emf under no load,
 - (iii). the speed when the load current is 41A,
 - (iv). the speed regulation.

Q5, (20 pts): Fig. Q5-1 shows a cross-sectional sketch of a machine having a rotor winding f and two identical stator windings “a” and “b” with turns N whose axes are in quadrature. The uniform air gap between rotor and stator is “ g ”, its equivalent cross-sectional area “ A_g ”, and the material of the core $\mu \rightarrow \infty$. The stator windings are energized by a balanced two-phase currents:

$$i_a = I_0 \cdot \sin \omega t \quad i_b = I_0 \cdot \cos \omega t$$

- (i). Derive the resultant flux density, B_{tt} , in the air gap.
- (ii). Show the B_{tt} is rotating and its rotating direction CCW or CW.

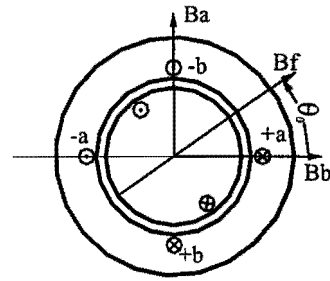


Fig. Q5-1