

UNIVERSITY OF SWAZILAND
FACULTY OF SCIENCE AND ENGINEERING
DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

MAIN EXAMINATION DECEMBER 2015

TITLE OF PAPER:	POWER SYSTEM ANALYSIS AND OPERATIONS
COURSE CODE:	EE552
TIME ALLOWED:	THREE HOURS

INSTRUCTIONS:

1. Answer any five (5) questions
2. Each question carries 20 marks
3. Marks for different sections are shown in then right hand margin

This paper has 4 pages including this page

DO NOT OPEN THE PAPER UNTIL PERMISSION HAS BEEN GRANTED BY THE INVIGILATOR

QUESTION 1 [20]

- (a) State 4 conditions for successful operation of a power system under normal balanced three-phase steady-state conditions [4]
- (a) For the two bus power system shown in Fig. Q. 1(b), use the Newton-Raphson power flow to determine the voltage magnitude and angle at bus two. Assume that bus one is the slack and $S_{Base} = 100$ MVA [16]

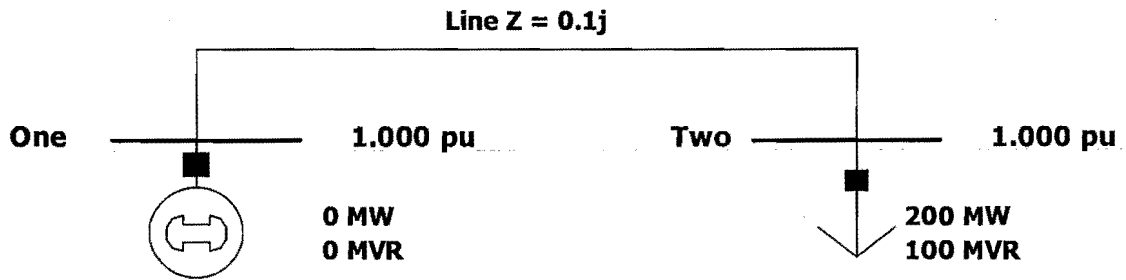


Fig. Q. 1(b).

QUESTION 2 [20]

- (a) The single-line diagram for a simple three-phase power system is shown in Fig. Q. 2 (a). A bolted fault occurs at bus 3 (B3), with a pre fault voltage of 272 kV

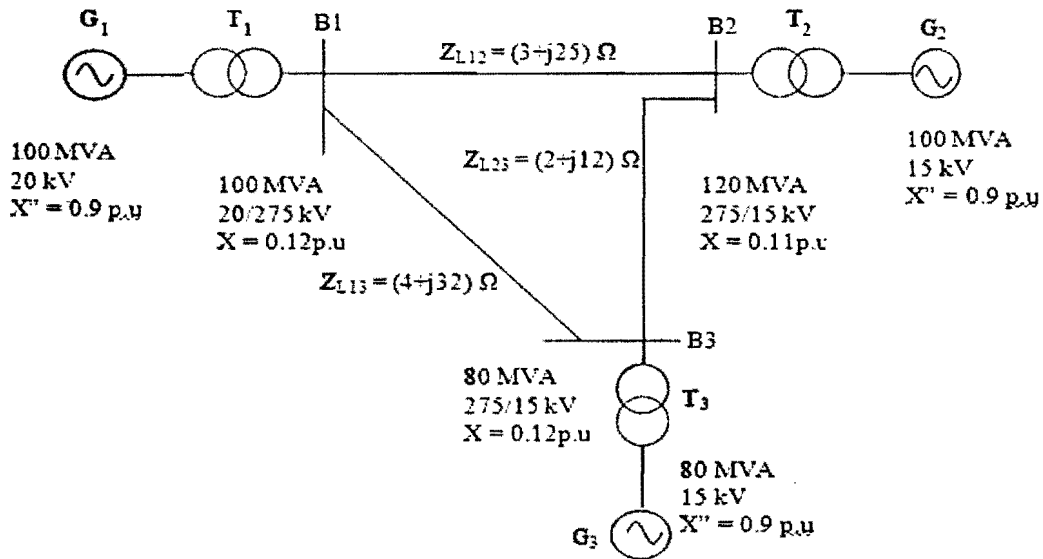


Fig. Q. 2(a).

- (i) Calculate the Thevenin impedance at the fault point. Use a base of 120 MVA [17]
- (ii) Determine the sub-transient *L-L-L* fault current in p.u and in kA [3]

QUESTION 3 [20]

- (a) State and explain any 3 main parameters of a transmission line [6]
- (b) A transmission line delivers a load of 50 MVA at 110 kV and p.f. 0.8 lagging. If the ABCD constants of the line are: $A = D = 0.98 \angle 3^\circ$; $B = 110 \angle 75^\circ \Omega$; $C = 0.0005 \angle 80^\circ \text{ S}$. Determine:
 - (i) Sending end voltage [6]
 - (ii) Sending end current [4]
 - (iii) Sending end power [2]
 - (iv) Efficiency of transmission. [2]

QUESTION 4 [20]

- (a) Define fault and state at least two common causes of fault [3]
- (b) State 2 methods of computing fault current [2]
- (c) Differentiate between balanced and unbalanced faults [2]
- (d) Define symmetrical components and briefly explain how symmetrical components is used to analyze unbalanced systems [4]
- (e) Compute the sequence components of the following balanced line – to- neutral currents with *abc* sequence [9]

$$\begin{bmatrix} I_{AN} \\ I_{BN} \\ I_{CN} \end{bmatrix} = \begin{bmatrix} 150 \angle 45^\circ \\ 250 \angle 150^\circ \\ 100 \angle 300^\circ \end{bmatrix} \text{ Amps}$$

QUESTION 5 [20]

- (a) Using two port network approach, derive the expressions for ABCD constants of a medium transmission line modeled using nominal π representation [7]
- (b) Which of the following will increase the resistance of a transmission line? Briefly explain
 - (i) Increasing line temperature [2]
 - (ii) Moving from a 60Hz ac system to a 50Hz ac system [2]
- (c) From hydroelectric power plant, 900 MW are to be transmitted to a load center located 500 km from the plant. Based on practical line loadability criteria, determine the number

of 3 – phase 60 Hz lines required to transmit this power with one line out of service for the following cases

- (i) 345 kV lines with $Z_C = 295 \Omega$ [3]
- (ii) 500 kV lines with $Z_C = 277 \Omega$ [3]
- (iii) 765 kV lines with $Z_C = 266 \Omega$ [3]

Assume $V_S = 1.0$ per unit $V_R = 0.95$ per unit and $\delta = 35^\circ$. Also assume that the lines are uncompensated.

QUESTION 6 [20]

- (a) Discuss a basic procedure used in solving a power flow problem using Gauss-Siedel iterative method [7]
- (b) In a 2-bus power system shown in Fig Q. 6(b), a generator attached to bus 1 and loads attached to bus 2. The series impedance of a single transmission line connecting them is $(0.1+j0.5)$ per unit. The shunt admittance of the line may be neglected. Assume that bus 1 is the slack bus and that it has a voltage $V_1 = 1.0\angle 0^\circ$ per unit. Real and reactive powers supplied to the loads from the system at bus 2 are $P_2 = 0.3$ per unit, $Q_2 = 0.2$ per unit (powers supplied to the system at each busses is negative of the above values). Determine voltages at each bus for the specified load conditions. *Use the Gauss-Siedel iterative method* [13]

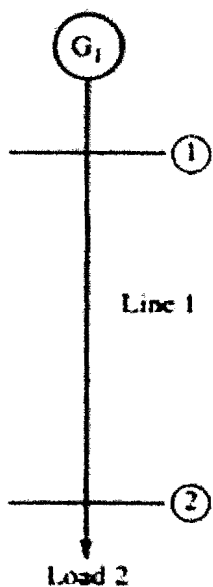


Table of Busses:

Bus 1	Slack bus
Bus 2	Load bus

Fig. Q. 6(b)