

**UNIVERSITY OF SWAZILAND  
SUPPLEMENTARY EXAMINATION, JULY 2017**

**FACULTY OF SCIENCE AND ENGINEERING**

**DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING**

**TITLE OF PAPER: INSTRUMENTATION SYSTEMS**

**COURSE NUMBER: EE521**

**TIME ALLOWED: THREE HOURS**

---

**INSTRUCTIONS:**

1. There are four questions in this paper. **Answer all four questions.**
2. Each question carries 25 marks.
3. Marks for different sections are shown on the right hand margin.
4. Show the steps clearly in all your calculations including any assumptions made.

---

**THIS PAPER IS NOT TO BE OPENED UNTIL PERMISSION HAS BEEN GIVEN BY  
THE INVIGILATOR**

**THIS PAPER HAS FIVE (5) PAGES INCLUDING THIS PAGE**

**QUESTION 1 (25 marks)**

- (a) A temperature measurement system consists of an RTD (Resistance Temperature Detector) sensor excited by a constant current source. Explain how the following can cause errors in the temperature measurement:
- (i) Self-heating of the sensor (2 marks)
  - (ii) Lead wire resistance. (2 marks)
- (b) An RTD with a nominal resistance of  $250\ \Omega$  is excited with a 10 mA current source. The RTD is packaged in a material which has a thermal resistance of  $40^\circ\text{C}/\text{W}$ .
- (i) Determine the temperature measurement error due to self-heating? (5 marks)
  - (ii) The two wire lead to the RTD sensor is 30 m long with a wire resistance of  $1.028 \times 10^{-3}\ \Omega/\text{m}$ . The sensor has a temperature coefficient of resistance (thermal response) of  $0.00385\ \Omega/\Omega/^\circ\text{C}$ . Determine temperature measurement error caused by the resistance of the two lead wires. (6 marks)
- (c) Explain, giving illustrative examples where applicable, how the RTD measurement system described in (b) may be improved so as to reduce:
- (i) the measurement error due to self-heating. (4 marks)
  - (ii) the measurement error due to the lead wires. (6 marks)

**QUESTION 2 (25 marks)**

- (a) List any five distinct electronic functions (or operations) which are normally carried out during sensor 'conditioning'. (5 marks)
- (b) Why are 'bridge' circuits used in sensor circuits? (2 marks)
- (c) Define the terms 'strain' and 'gauge factor' as used in strain gauge sensors. (5 marks)
- (d) A measurement system consists of a strain gauge connected to one arm of a quarter bridge circuit. The bridge output is connected to the input of an instrumentation amplifier.
- (i) Draw the circuit diagram (not a block diagram) of the measurement system showing the bridge, sensor and a three-opamp version of the instrumentation amplifier. (4 marks)
- (ii) The strain gauge has a gauge factor of 2, nominal resistance of  $120\ \Omega$  and, in the measurement, the strain gauge experiences a strain ranging from  $-10^{-4}$  to  $+10^{-4}$ . It is desired that the resulting output voltage from the instrumentation amplifier be in the range  $-5\ \text{V}$  to  $+5\ \text{V}$ .

Determine the gain required in the instrumentation amplifier, assuming that the bridge excitation voltage is  $+15\ \text{V}$ . **Do not design the instrumentation amplifier itself.**

(9 marks)

**QUESTION 3 (25 marks)**

- (a) What are the differences between each of the following sets of terms:
- (i) 'Sensitivity' and 'Cross sensitivity' as used in description of sensors. (2 marks)
  - (ii) 'Accuracy' and 'Precision' as used in measurement. (2 marks)
  - (iii) 'The piezo-resistive effect' and 'the piezo-electric effect' as used in sensors. (2 marks)
  - (iv) 'Static' and 'Dynamic' properties as used in description of instruments. (2 marks)
  - (v) 'Contact' and 'Non-contact' measurement methods. (2 marks)
- (b) In this question you are expected to design a **four-pole Butterworth lowpass filter** with a lower cut-off frequency  $f_c$  of 5 kHz. You are given that for the equal-component value, Sallen-Key, 4-pole, lowpass filter shown in Fig. Q3a, the components may be found using the following normalized data:

Poles	$k_3 = RC\omega_c$	G
4	1.000	1.152
	1.000	2.235

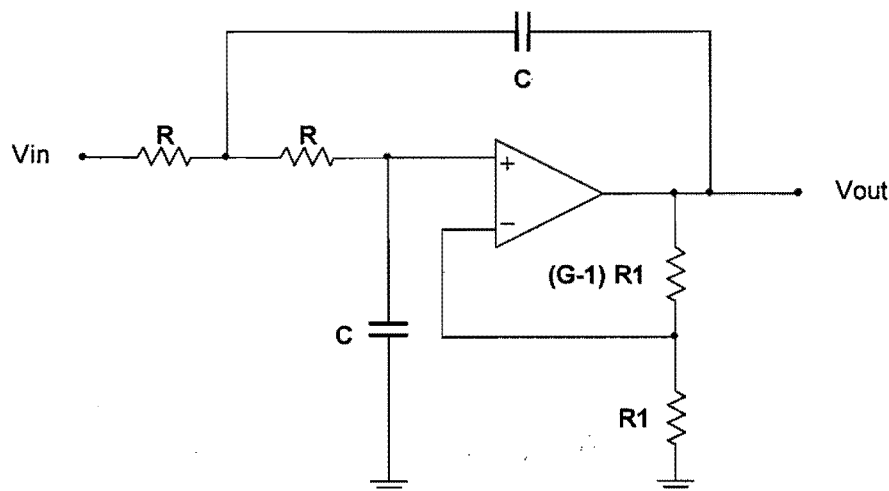


Fig. Q3a

- (i) Determine the values of all the components in your circuit. (12 marks)
- (ii) Draw a circuit schematic diagram showing all components values of your diagram. (3 marks)

**QUESTION 4 (25 marks)**

- (a) (i) What is an 'isothermal block'? (2 marks)
- (ii) Explain why and how an isothermal block is used in electronic measurements using thermocouples. (5 marks)
- (b) A sensor used in a measurement system produces a signal with a minimum value of 1.8 V and a maximum value of 2.6 V. A circuit is required which changes this sensor signal to the range 0 V to 5 V for feeding into an ADC input of a microcontroller with maximum possible resolution, so that the sensor signal fills the entire input range of the ADC.
- (i) By means of a diagram, suggest a circuit which can be used to realize the required change in signal levels. (4 marks)
- (ii) Design the circuit, calculating the values of all the required components. (14 marks)

===== END OF QUESTION PAPER =====