

**UNIVERSITY OF SWAZILAND**  
**SUPPLEMENTARY EXAMINATION, SECOND SEMESTER**  
**MAY 2017**

**FACULTY OF SCIENCE AND ENGINEERING**

**DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING**

**TITLE OF PAPER: Switchgear and Protection**

**COURSE CODE : EE551**

**TIME ALLOWED: THREE HOURS**

**INSTRUCTIONS:**


- 1. There are five questions in this paper. Answer any four questions. Each question carries 25 marks.**
- 2. If you think not enough data has been given in any question you may assume any reasonable values.**

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION  
HAS BEEN GIVEN BY THE INVIGILATOR**

**THIS PAPER CONTAINS EIGHT (8) PAGES INCLUDING THIS PAGE**

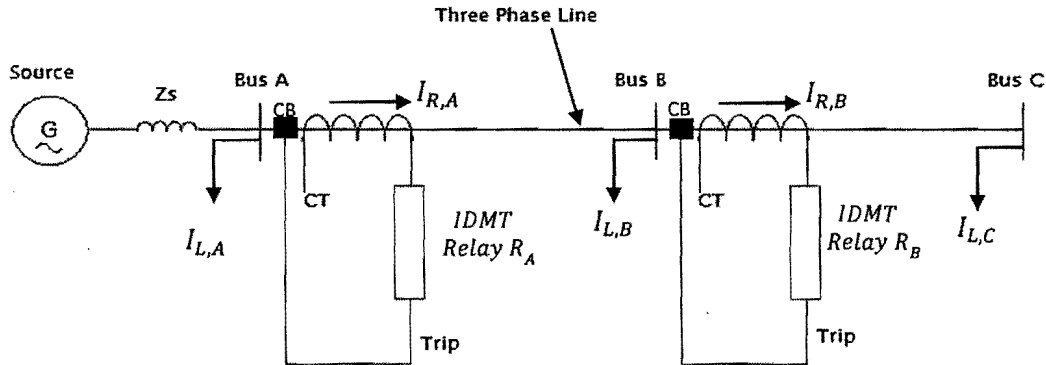**QUESTION ONE (25 marks)** Solve the following questions

Consider a radial feeder with three buses A, B and C where IDMT OC relays used. The load current at each bus and fault currents when having a fault at each bus are given below




Bus A	Bus B	Bus C
$I_{L,A} = 200 \text{ A}$	$I_{L,B} = 115 \text{ A}$	$I_{L,C} = 125 \text{ A}$
$I_{FA, \max} = 2500 \text{ A}$	$I_{FB, \max} = 2000 \text{ A}$	$I_{FC, \max} = 1500 \text{ A}$

- a) Determine the CT ratios and the plug settings for the relays at bus A and bus B. Assume 20% overload when calculating the maximum load, 5 A relay rating is used and the plug settings to be done at 130%. [4]

Note: Assume the available CT ratings are: 100 A, 200 A, 300 A, 400 A, 500 A, 600 A ..., etc.

- b) Determine the time dial setting for the relay at bus A. Assume the time dial setting for the relay at bus B is 0.1 sec ( $T_{DS,B} = 0.1 \text{ sec}$ ), each circuit breaker operating time is 0.3 sec ( $T_{CB} = 0.3 \text{ sec}$ ) and each relay overshoot time is calculated to be 15% of the summation of relay operating time and circuit breaker operating time of the previous coordinated relay  $T_{OS} = 0.15(T_{CB} + T_R)$  [7]

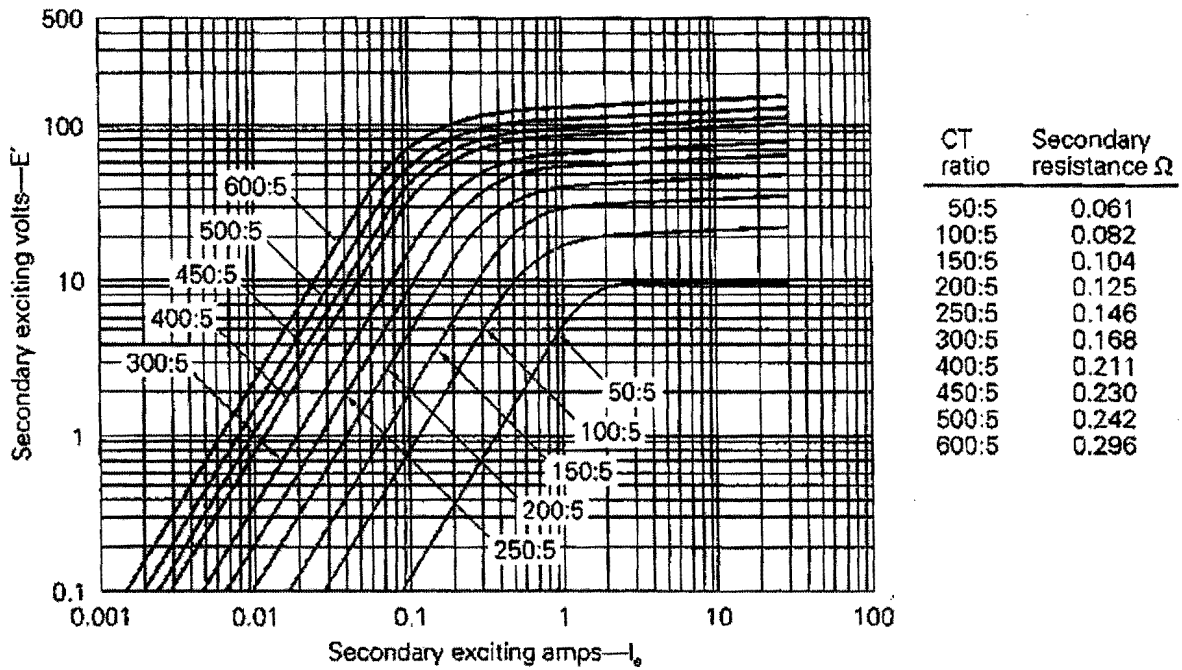c) The figure below shows excitation curves for a multi-ratio bushing CT with a C100 ANSI accuracy classification.




- (i) Evaluate the performance of the multi-ratio Current Transformer with a 200 : 5 CT ratio, for the following secondary output currents  $I' = 5A$  and burden  $Z_B = 0.5 \Omega$  [5]
- (ii) Explain why it is not advisable to open circuit current transformers. [4]
- (iii) Describe the knee point voltage of Current Transformer [5]

**Question 2: Solve the following questions (25 marks):**

- (a) Give the classification of circuit breakers based on the medium used for arc extinction? [6]
- (b) Give the three advantages of SF6 Circuit Breaker. [3]
- (c) Discuss the theories which explain the phenomenon of arc extinction. [4]
- (d) Define the term *pilot* with reference to power line protection. [2]
- (e) A current transformer has turns ratio 1:188 and is rated 1000/5A. The core loss component is 2.5A and the magnetizing component is 8 A under full load conditions. Find the phase and ratio errors under full load conditions if the secondary circuit power factor is 0.75 lagging.
- i. The Ratio error [6]
  - ii. The Phase Angle error [4]

**Question 3: Solve the following questions (25 marks)**

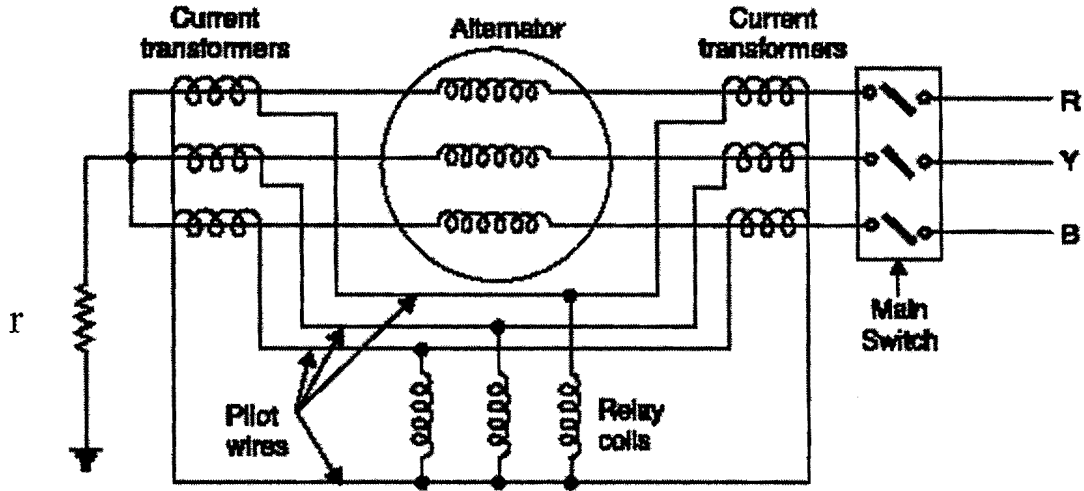
- (a) A 50MVA, 66 kV, 3-phase star connected alternator is protected by Merz-Price circulating current system. If the ratio of the current transformer is 2000/5, the minimum operating current for the relay is 0.85 A.



Calculate:

- i) The minimum resistance to provide protection for 95% of the rotor winding. [10]
- ii) Give the limitations of Merz Price protection. [3]

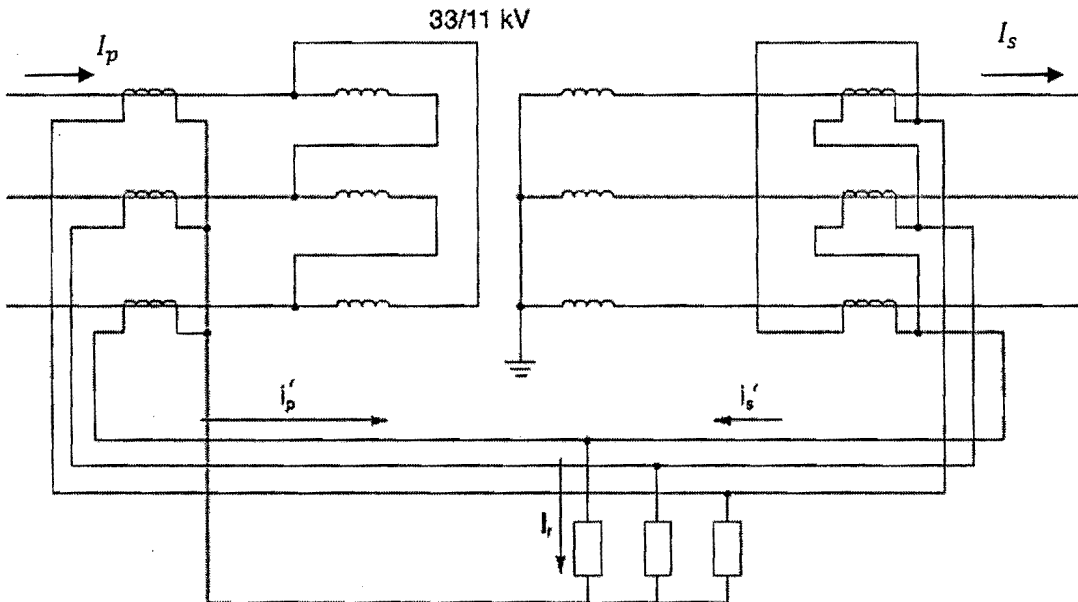
- (b) Consider the three-phase  $\Delta$ -Y connected, 30-MVA, 33:11 kV transformers with differential relay protection as shown in the figure below,



- (i) Determine the CT ratios for differential protection of the three-phase,  $\Delta$ -Y connected transformer, such that the circulating current in the transformer does not exceed 5 A. [10]
- (ii) Compute the relay current setting for faults drawing up to 150 % of rated transformer current. [2]

**Question 4:** Solve the following questions (25 marks):

- a) Derive and draw the characteristics of an impedance relay. [5]
- b) Explain with sketches the R-X diagrams for the following distance relays.
  - (i) Mho relay [3]
  - (ii) Reactance relay [3]
  - (iii) Directional Relay [3]
- c) What is the need of relay coordination? [2]
- d) Name the different kinds of over current relays. [3]
- e) Discuss Primary protection and Backup protection with reference to the Figure Q4 below [6]

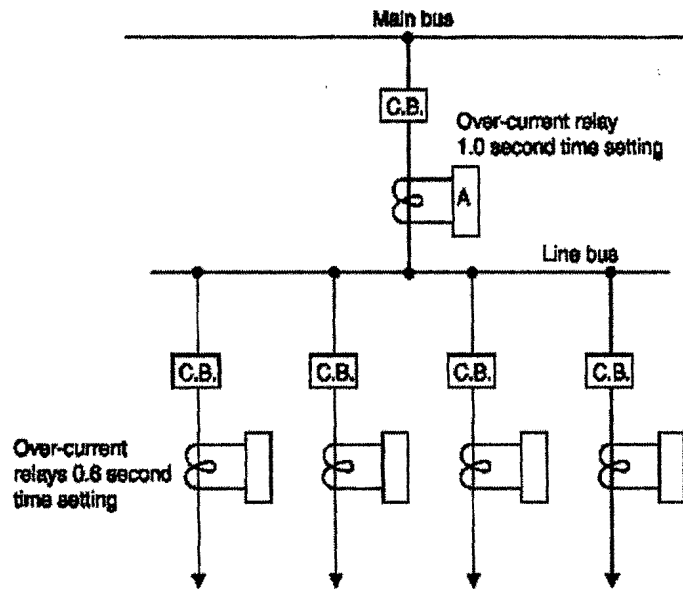

**Figure Q4**

### Question 5

(a) Explain the principle of operation of the circuit breaker.

[4]

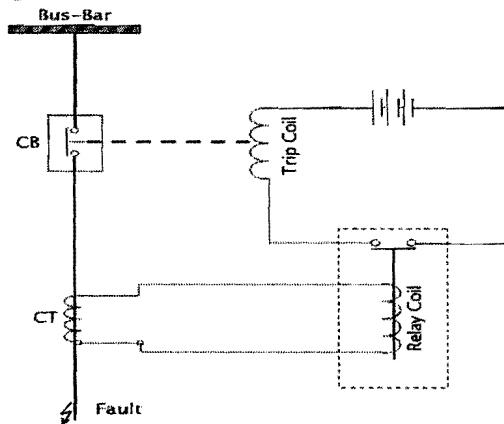


Figure Q5a

(b) The following table gives the positive sequence line impedances as well as the CT and VT ratios of the distance relay at B12 for a 132 kV (line to line) systems.

Line	Positive sequence impedance $\Omega$
1-2	$11+j60$
2-3	$9+j35$
2-4	$8+j55$
1-3	$5+j30$

Circuit Breaker	CT ratio	VT ratio
B12	2500:5	400:1


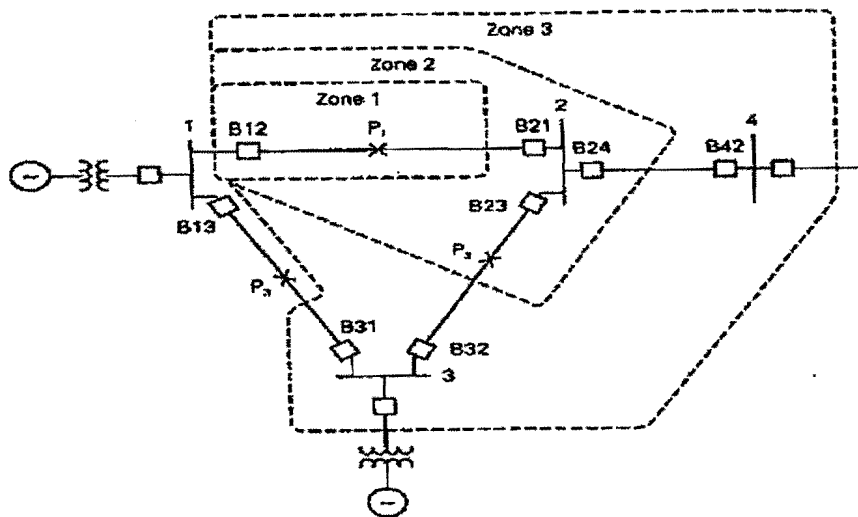


Figure Q5b

- (i) Determine the three impedance relay zones settings  $Z_{r1}$ ,  $Z_{r2}$ ,  $Z_{r3}$  for the breaker B12, [9]
- (ii) Maximum current for line 1-2 during emergency loading conditions is 180 A at a power factor 0.7 lagging. Verify that B12 does not trip during normal and emergency loadings. [8]

- (c) Coordinate the direction of supervision and the time delay between the directional OC relays in the following ring network so that a fault in any section causes only the CBs associated with that section to trip. [6]

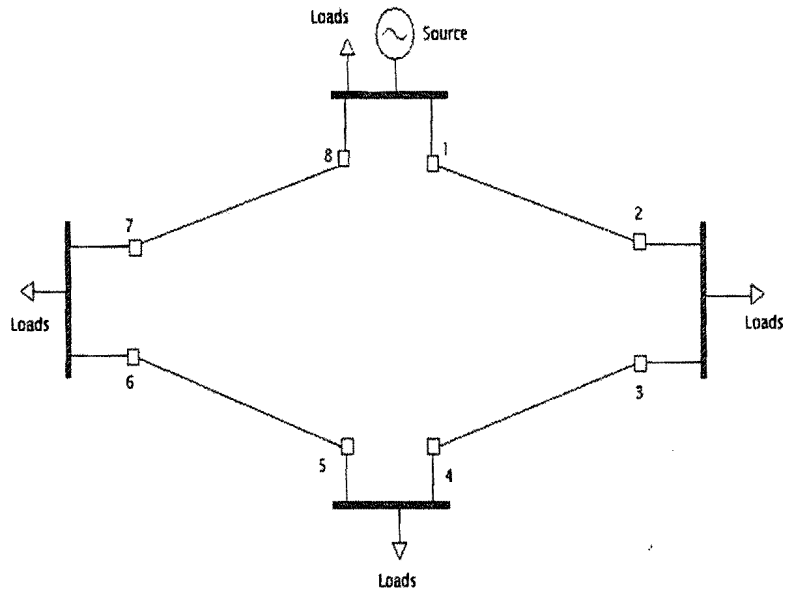

**Figure Q5c**

- (d) If there is a fault in the middle of the line 5-6, which relays are going to energize and what will be their operating time according to your coordination? [2]