

UNIVERSITY OF SWAZILAND
FACULTY OF SCIENCE & ENGINEERING
DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING
MAIN EXAMINATION
DECEMBER 2016

TITLE OF PAPER: BASIC ELECTRICAL ENGINEERING

COURSE CODE: EEE251/EE251

DURATION: 3 HOURS

INSTRUCTIONS:

1. There are five (5) questions in this paper. Answer question 1 and any other three (3) questions.
2. Each question carries equal marks.
3. Start each question in a new page.

This paper should not be opened until permission has been given by the invigilator.

This paper contains six (6) pages including this page.

Question 1 [25 Marks]

- a. Describe a rheostat and potentiometer. Give two examples where they can be used. [2 Marks]
- b. Using simple circuit diagrams illustrate how each can be connected in a circuit. [4 Marks]
- c. An experimenter building the voltage circuits shown in Figure Q.1c predicted that varying the resistance R_2 and R_3 should give the results shown on the graphs below the circuits.
- i. Make pairs of each voltage divider circuit (a) or (b) with a corresponding graph (c) or (d). Give reasons for your pairs. Further determine what the axis variables X and Y should be. [6 Marks]
- ii. Define the labeling of the graphs by working out, from the circuit variables, expressions for the voltages labelled A , B , C , D and E . [10 Marks]

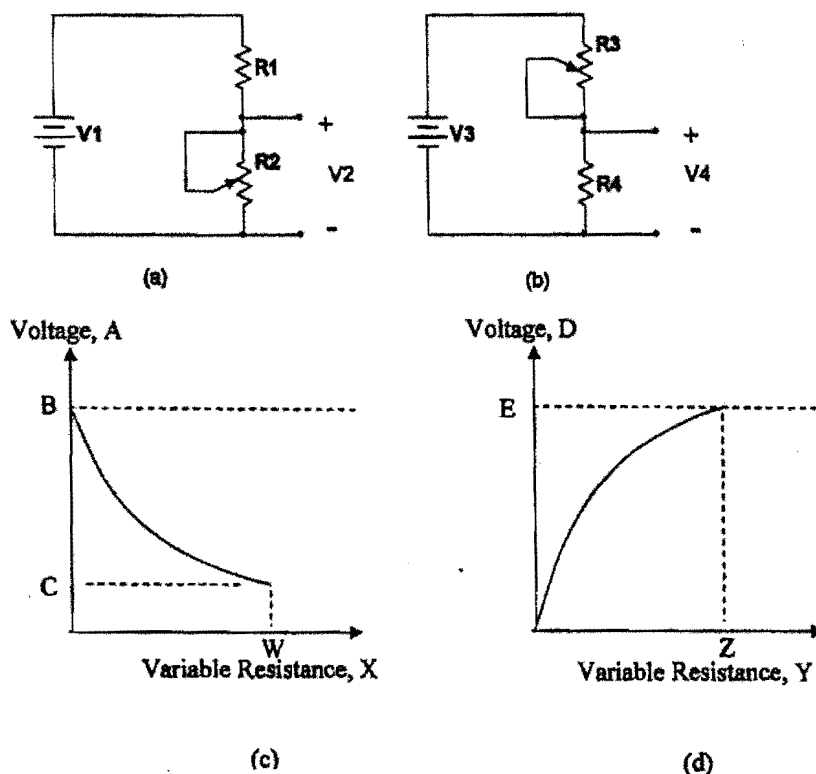


Figure Q.1c.

- d. Determine the ratio of powers dissipated in two resistors, each having the same length and each made of copper wire of circular cross section, but one having a diameter twice that of the other, and each being connected across the same voltage. [3 Marks]

Question 2 [25 Marks]

- a. In Figure Q.2a, use wye-delta or delta-wye transformation to evaluate the following;
- i. The current supplied by the source, i.e. I_s . [7 Marks]
 - ii. The Voltage across R_4 . [3 Marks]

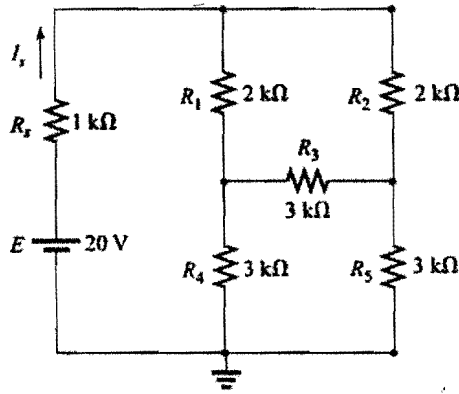


Figure Q.2a.

- b. In Figure Q.2b, use the mesh current analysis technique to find;
- i. The loop and branch currents. [10 Marks]
 - ii. The voltage across 1 Ω and 4 Ω resistor. [5 Marks]

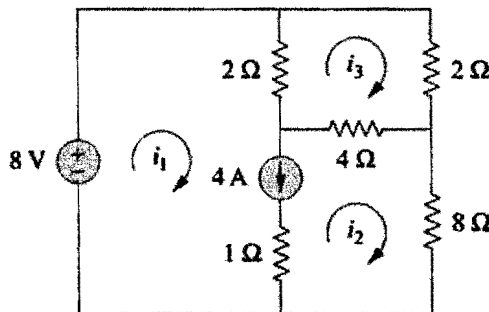


Figure Q.2b.

Question 3 [25 Marks]

- a. Consider the circuit shown in Figure Q.3a.
- Find the Thevenin equivalent of the circuit across the points a and b. [7 Marks]
 - If a variable resistor were connected between the points a and b, what will be the maximum power dissipated in the variable resistor? [2 Marks]

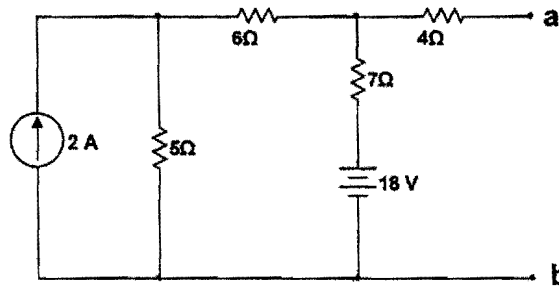


Figure Q.3a.

- b. Use nodal analysis to find the voltage through the 4 Ω resistor shown in Figure Q.3b. [7 Marks]

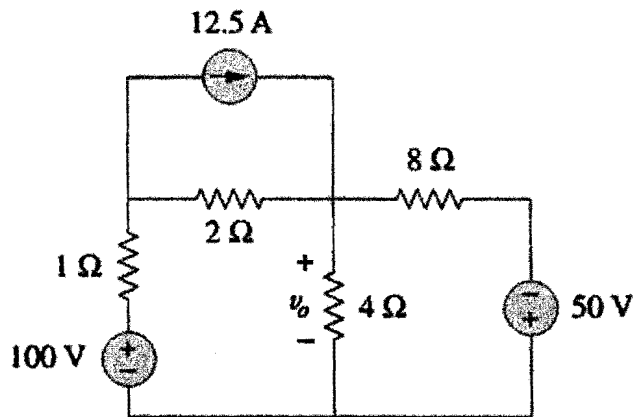


Figure Q.3b.

- c. The circuit shown in Figure Q.3c has two current sources one of which is a voltage dependent source. Find the following:
- The voltage across the independent current source. [5 Marks]
 - The power dissipated in each resistor. [2 Marks]
 - The total power supplied by the sources. [2 Marks]

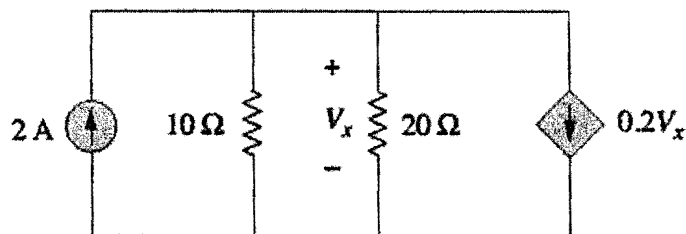


Figure Q.3c.

Question 4 [25 Marks]

- a. A $4\ \Omega$ resistor in series with a $7.96\ \text{mH}$ inductor is connected across a $230\ \text{V}$ $50\ \text{Hz}$ source. Determine:
- The total impedance. [2 Marks]
 - The input current [2 Marks]
 - The voltages across the resistor and the inductor. [3 Marks]
 - Draw a phasor diagram showing the current and the voltages. [4 Marks]
 - The power factor. [2 Marks]
 - The input power. [2 Marks]
- b. Given that an inductor draws $5\ \text{A}$ of current at $230\ \text{V}$ $50\ \text{Hz}$, find the inductive reactance and the inductance. [4 Marks]
- c. Given that a capacitor draws $2\ \text{A}$ of current at $230\ \text{V}$ $50\ \text{Hz}$. Find the capacitive reactance and the capacitance. [4 Marks]

Question 5. [25 Marks]

- a. A circuit consisting of a coil of inductance $150\ \mu\text{H}$ and resistance $5\ \Omega$, in series with a capacitance of $22\ \text{nF}$ is connected to a variable frequency supply which has a constant voltage $20\ \text{V}$. Determine:
- The resonance frequency of the circuit. [2 Marks]
 - The current in the circuit at resonance. [2 Marks]
 - The voltages across the inductance and the capacitor at resonance. [3 Marks]
 - The Q-factor of the circuit [2 Marks]
- b. A coil of inductance $0.1\ \text{H}$ is connected across a $50\ \text{V}$, $60\ \text{Hz}$ supply, in parallel with it is a $60\ \mu\text{F}$ capacitor which is also in parallel with a $30\ \Omega$ resistor as shown in Figure Q.5b. Determine:
- The total impedance of the circuit. [4 Marks]
 - The branch currents [3 Marks]
 - The total Active Power taken from the supply. [2 Marks]
 - The total reactive power supplied. [3 Marks]
 - The apparent power supplied. [2 Marks]
 - The power factor of the combined circuits stating whether it is leading or lagging. [2 Marks]

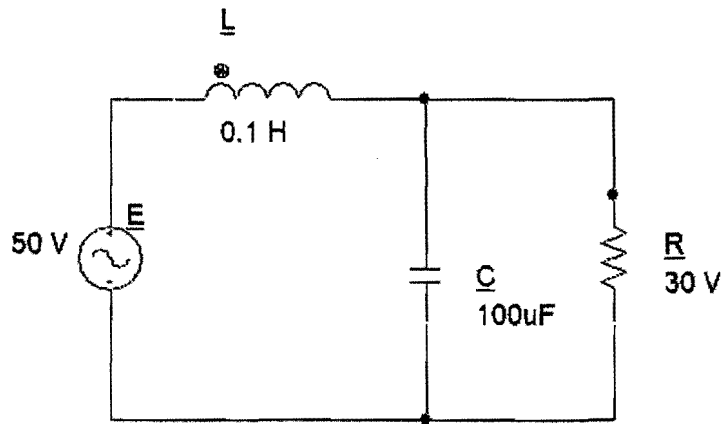


Figure Q.5b.

End of Paper