

UNIVERSITY OF SWAZILAND

FACULTY OF SCIENCE & ENGINEERING

DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING

SUPPLEMENTARY EXAMINATION

JULY 2017

TITLE OF PAPER: BASIC ELECTRICAL ENGINEERING

COURSE CODE: EEE251/EE251

DURATION: 3 HOURS

INSTRUCTIONS:

1. There are five (5) questions in this paper. Answer question 1 and any other three (3) questions.
2. Each question carries equal marks.
3. Start each question in a new page.

This paper should not be opened until permission has been given by the invigilator.

This paper contains six (6) pages including this page.

Question 1 [25 Marks]

- a. Describe a rheostat and potentiometer. Give two examples where they can be used. [2 Marks]
- b. Using simple circuit diagrams illustrate how each can be connected in a circuit. [4 Marks]
- c. An experimenter building the voltage circuits shown in Figure Q.1c predicted that varying the resistance **R2** and **R3** should give the results shown on the graphs below the circuits. Make pairs of each voltage divider circuit (a) or (b) with a corresponding graph (c) or (d). Give reasons for your pairs. Further determine what the axis variables **X** and **Y** should be. [6 Marks]

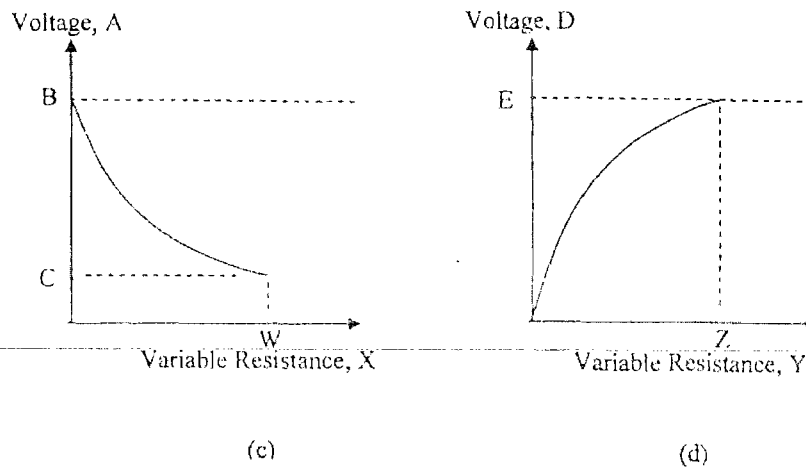
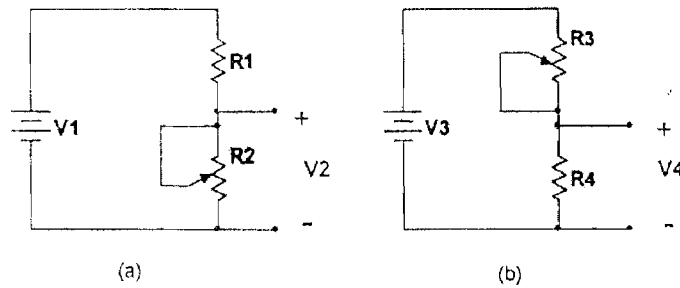


Figure Q.1c.

- d. Find the total resistance between points 1 and 2 shown in Figure Q.1d [10 Marks]

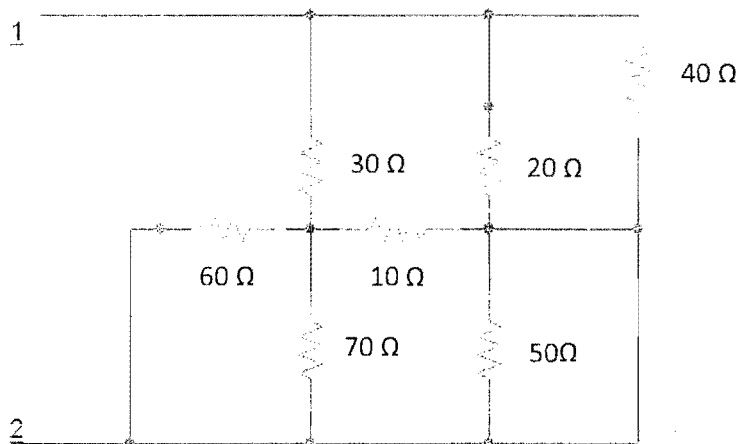


Figure Q.1d.

- e. Determine the ratio of powers dissipated in two resistors, each having the same length and each made of copper wire of circular cross section, but one having a diameter twice that of the other, and each being connected across the same voltage.

[3 Marks]

Question 2 [25 Marks]

- a. In Figure Q.2a, use wye-delta or delta-wye transformation to evaluate the following;

- i. The current supplied by the source, i.e. I_s . [7 Marks]
- ii. The Voltage across R_4 . [3 Marks]

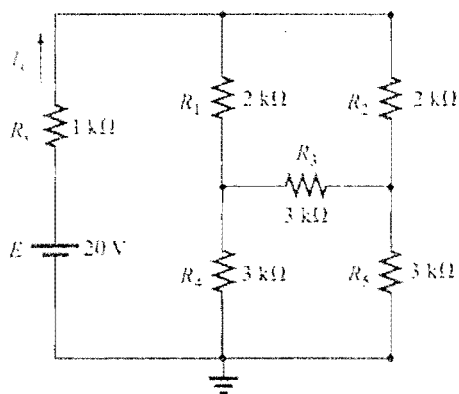


Figure Q.2a.

- b. In Figure Q.2b, use the mesh current analysis technique to find;

- i. The loop and branch currents. [10 Marks]
- ii. The voltage across 1 Ω and 4 Ω resistor. [5 Marks]

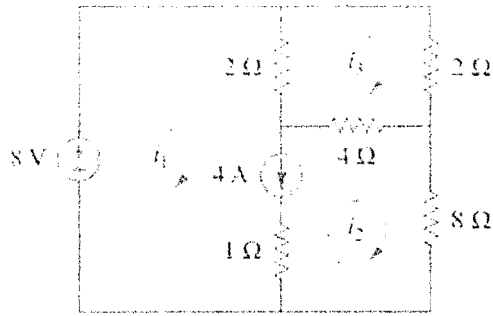


Figure Q.2b.

Question 3 [25 Marks]

a. Consider the circuit shown in Figure Q.3a.

i. Find R so that maximum power is transferred to the resistance R .

[15 Marks]

ii. Find this maximum power.

[3 Marks]

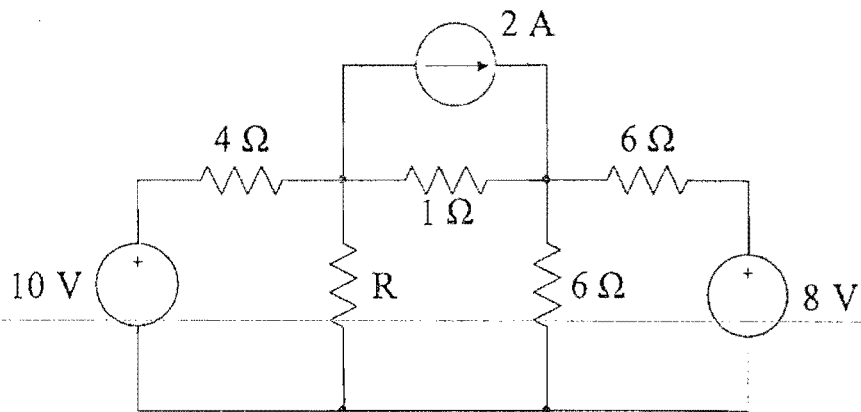


Figure Q.3a.

- b. Use nodal analysis to find the voltage through the $4\ \Omega$ resistor shown in Figure Q.3b. [7 Marks]

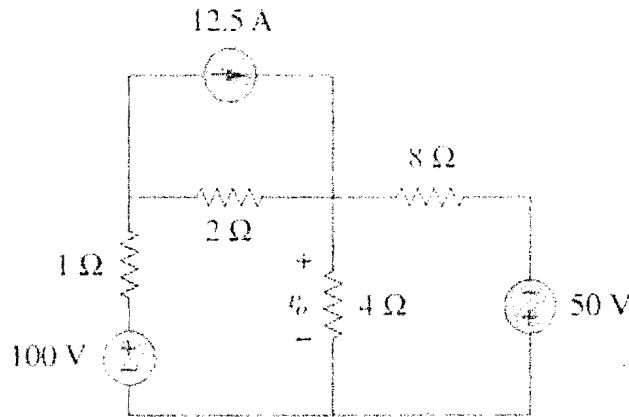


Figure Q.3b.

Question 4 [25 Marks]

- a. A $4\ \Omega$ resistor in series with a $7.96\ \text{mH}$ inductor is connected across a $230\ \text{V}$ $50\ \text{Hz}$ source. Determine:
- The total impedance. [2 Marks]
 - The input current [2 Marks]
 - The voltages across the resistor and the inductor. [3 Marks]
 - Draw a phasor diagram showing the current and the voltages. [4 Marks]
 - The power factor. [2 Marks]
 - The input power. [2 Marks]
- b. Given that an inductor draws $5\ \text{A}$ of current at $230\ \text{V}$ $50\ \text{Hz}$, find the inductive reactance and the inductance. [4 Marks]
- c. Given that a capacitor draws $2\ \text{A}$ of current at $230\ \text{V}$ $50\ \text{Hz}$. Find the capacitive reactance and the capacitance. [4 Marks]

Question 5. [25 Marks]

- a. A circuit consisting of a coil of inductance $150\ \mu\text{H}$ and resistance $5\ \Omega$, in series with a capacitance of $22\ \text{nF}$ is connected to a variable frequency supply which has a constant voltage $20\ \text{V}$. Determine:
- The resonance frequency of the circuit. [2 Marks]
 - The current in the circuit at resonance. [2 Marks]

- iii. The voltages across the inductance and the capacitor at resonance. [3 Marks]
- iv. The Q-factor of the circuit [2 Marks]

b. A coil of inductance 0.1 H is connected across a 50 V, 60 Hz supply, in parallel with it is a 60 μ F capacitor which is also in parallel with a 30 Ω resistor as shown in Figure Q.5b. Determine:

- i. The total impedance of the circuit. [4 Marks]
- ii. The branch currents [3 Marks]
- iii. The total Active Power taken from the supply. [2 Marks]
- iv. The total reactive power supplied. [3 Marks]
- v. The apparent power supplied. [2 Marks]
- vi. The power factor of the combined circuits stating whether it is leading or lagging. [2 Marks]

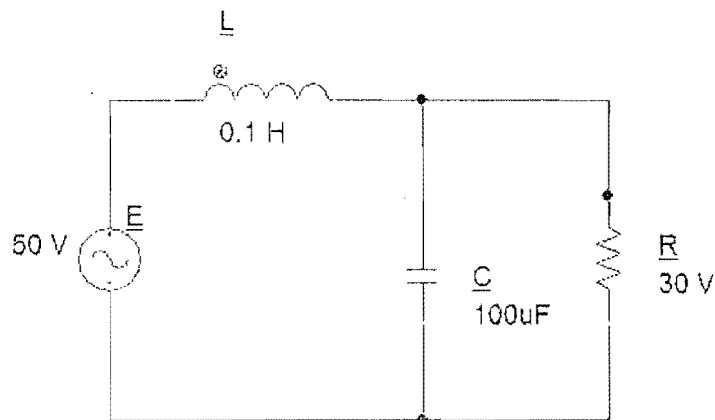


Figure Q.5b.

End of Paper