

8

UNIVERSITY OF SWAZILAND

FACULTY OF SCIENCE & ENGINEERING

DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING

RESIT EXAMINATION

JULY 2018

TITLE OF PAPER: BASIC ELECTRICAL ENGINEERING

COURSE CODE: EEE251

DURATION: 3 HOURS

INSTRUCTIONS:

1. There are five (5) questions in this paper. Answer question 1 and any other three (3) questions.
2. Each question carries equal marks.
3. Start each question in a new page.

This paper should not be opened until permission has been given by the invigilator.

This paper contains six (6) pages including this page.

Question 1 [25 Marks]

- a. A wire of uniform cross section has a resistance of 0.8Ω . If the length of the wire is doubled and its cross sectional area increased 4 times, what is the resistance? (ignore the effect of temperature). [4 Marks]
- b. Normally, heat energy is measured in joules (J). Given that you are required to design a heating element to boil a certain amount of water in 2 minutes using 200 kilojoules of energy. If the heating element is to operate at 240V, calculate its current and power rating. [4 Marks]
- c. What is the total cost of using the following appliances at 1 Lilangeni 34 cents per kilowatt-hour?
- 100W home theatre system for 2 hours. [1 Mark]
 - 150 W LCD TV for 3hrs 20 minutes [1 Mark]
 - 1500 W electric heater for 30 minutes [1 Mark]
- d. Given that two resistors are wound with round copper wire, the length and the diameter of the first wire are l and A respectively and those of the second wire are $0.25l$ and $0.5A$.
- Determine the ratio of currents and powers of the two resistors if they are connected across the same voltage source. [6 Marks]
 - If the same current flows through the two resistors, determine the ratios of voltage and power. [4 Marks]
- e. Consider the circuit shown in Figure Q1e. Given that $I_2 = 2.5A$ and $I_3 = 1.5A$, find the values of R_2 and R_3

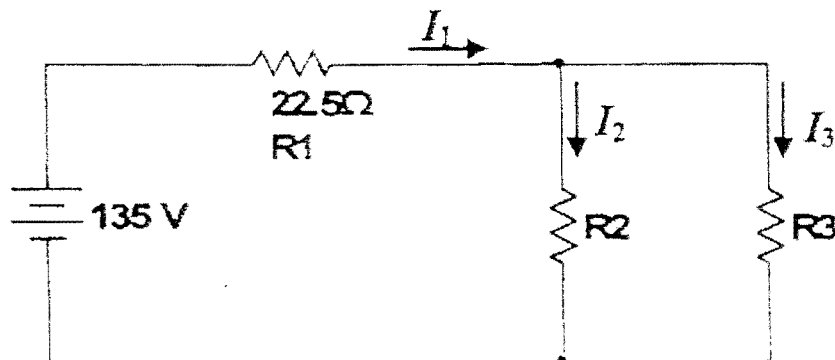


Figure Q2.e

[4 Marks]

Question 2 [25 Marks]

- a. Reduce the resistor network between terminals A and B of Figure Q.2a to a single resistor. [3 Marks]

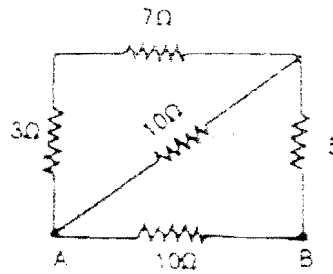


Figure Q.2a

- b. For the series-parallel network shown in Figure Q.2b, find the following.

- (i) The current I_5 .
- (ii) The currents I_2 and I_8 .
- (iii) The current I_7 .
- (iv) The voltage V_{ab} .

[12 Marks]

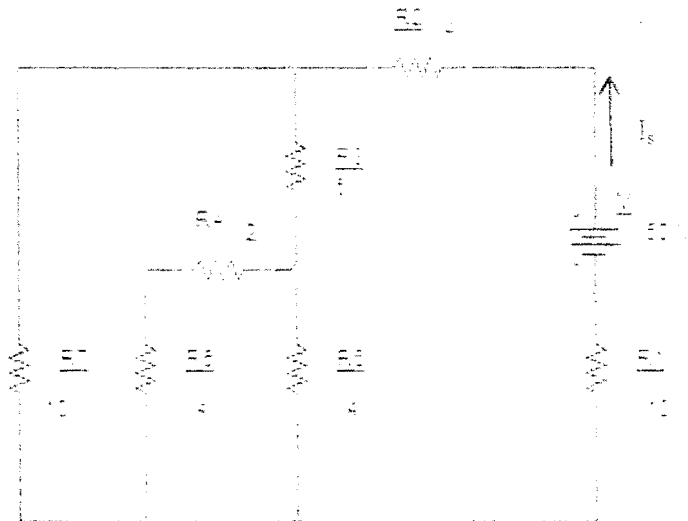


Figure Q.2b.

- c. Given that $I_5 = 4\text{A}$, use the current divider rule to evaluate the currents I , I_1 , I_2 , I_3 , I_4 , and I_6 in Figure Q.2c. [11 Marks]

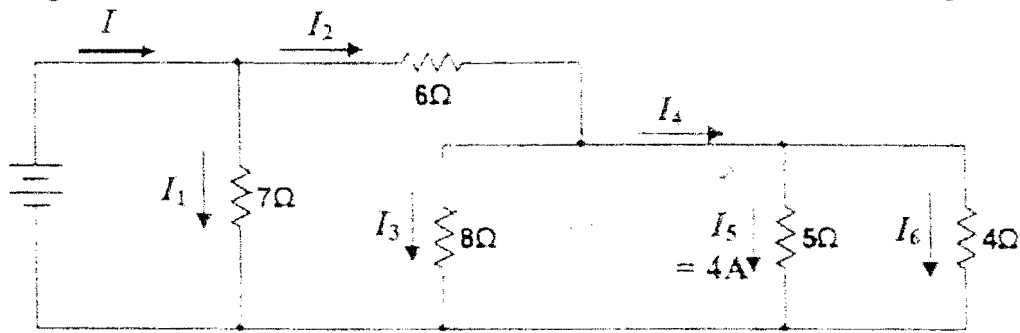


Figure Q.2c.

Question 3 [25 Marks]

- a. Find the maximum power transferred to R in the circuit of Figure Q.3a. [10 Marks]

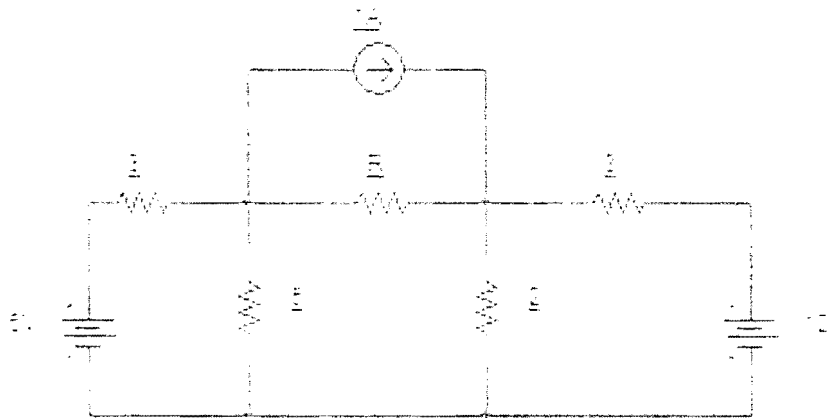


Figure Q.3a.

- b. Use nodal analysis to find current I_1 and I_2 in the circuit shown in Figure Q.3b. [10 Marks]

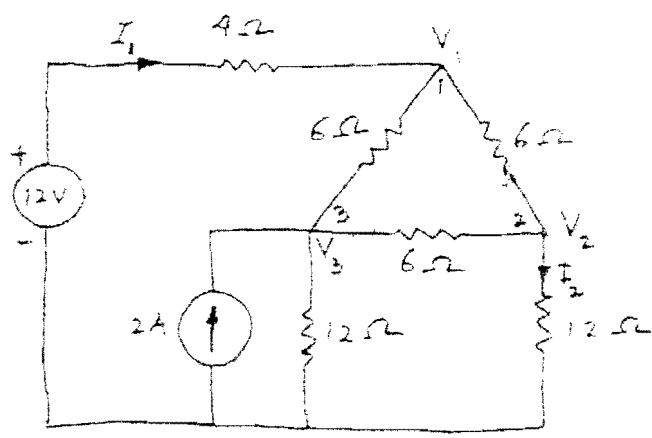


Figure Q.3b.

- c. You are told that a capacitor stores 0.3 J of energy when 400V d.c. supply is connected across the capacitor. Find the following.
- i. The capacitance. [2]
 - ii. The charge on the capacitor. [2]

Question 4 [25 Marks]

- a. Given the circuit shown in Figure Q.4a, answer the following:
- i. Use mesh analysis to determine current I_1 and I_2 [16 Marks]

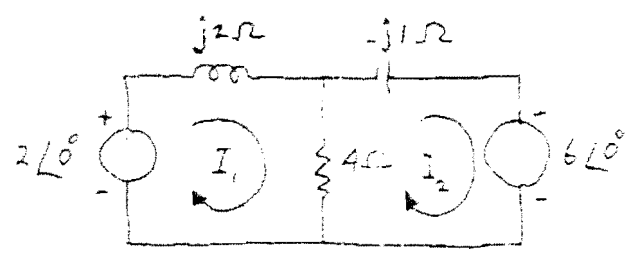


Figure Q.4a

- ii. Find the power supplied (or absorbed) by each source of the circuit. [4 Marks]

- b. An impedance $Z_1 = (4 + j4)\Omega$ is connected in parallel with an impedance $Z_2 = (12 - j6)\Omega$. If the input reactive power is 2500VAR (lagging), what is the total active power? [5 Marks]

Question 5 [25 Marks]

- a. A circuit consisting of a coil of inductance 10 mH and resistance 30 Ω , in series with a capacitance of 4 μ F is connected to a variable frequency supply which has a constant voltage 10 V. Determine:
- i. The resonance frequency of the circuit. [2 Marks]
 - ii. The current in the circuit at resonance. [2 Marks]
 - iii. The voltages across the inductance and the capacitor at resonance. [3 Marks]
 - iv. The Q-factor of the circuit [2 Marks]
- b. A coil of inductance 0.1 H is connected across a 50 V, 60 Hz supply, in parallel with it is a 100 μ F capacitor which is also in parallel with a 30 Ω resistor as shown in Figure Q.5b. Determine:
- i. The total impedance of the circuit. [4 Marks]
 - ii. The branch currents [3 Marks]
 - iii. The total Active Power taken from the supply. [2 Marks]
 - iv. The total reactive power supplied. [3 Marks]
 - v. The apparent power supplied. [2 Marks]
 - vi. The power factor of the combined circuits stating whether it is leading or lagging. [2 Marks]

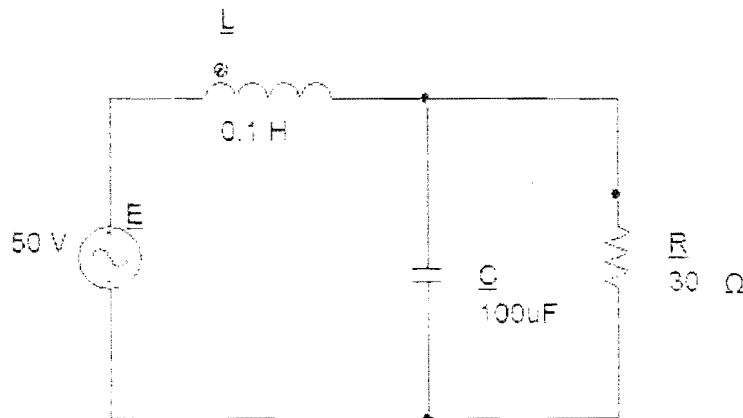


Figure Q.5b.

End of Paper