

UNIVERSITY OF SWAZILAND

FACULTY OF SCIENCE
**Department of Electrical and
Electronic engineering**

MAIN EXAMINATION 2018

Title of the paper:

Analogue Design II

Course Code: **EE323**


Time allowed: **Three Hours**

Instructions:

1. To answer, pick any 5 from the 6 questions in the following pages.
2. The answer must be written in the space provided in the question book; those in elsewhere considered invalid. Use the answer book as a scratch pad. Both question and answer book must be handed-in and marked with name and ID.
3. This paper has 7 pages, including this page.

**DO NOT OPEN THIS PAPER UNTIL
PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR**

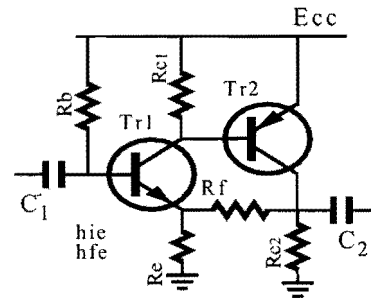Q1: (20 pts) (i) Draw the equivalent circuit of the schematic on the right. (ii) Write the matrix of the equivalent circuit. (each 10 pts) What is the configuration of this 2-stage amplifier (extra 5 pts). Assume the two Tr's are of the same spec.



Q2: (20 pts) Give 2 examples of positive feedback circuit in schematic diagram, (i)(7 pts). wideband feedback and (ii)(7 pts). narrowband feedback. (iii)(6 pts) Compare the differences of the output voltage time trace.


Q3: (20 pts) 2N3055 has a power dissipation rating 140 Watts at case temperature 25°C, a maximum junction temperature 200°C. (i) (10pts) Study the relationship between the power dissipation rating, P_D , and case temperature, T_C . Draw the curve $P_D \sim T_C$. (ii)(5 pts) Design a practical heat sink to dissipate the heat to the air at a temperature 25°C. Assume the transistor case and heat sink have a perfect thermal contact. Case temp may be around 45°C; calculate the sink θ_{ca} , where ca is between the case and the air. (iii)(5 pts) Find the new power dissipation again.

Q4: (20 pts) Given $V_s=1\text{ V}_{\text{rms}}$, the g_m of the FET, 12 mS in the circuit, and all components values marked in the circuit.

(i)(6 pts) Calculate the FET power output to the speaker under a direct-coupled speaker load $16\ \Omega$.

(ii)(7 pts) Use an emitter follower ($h_{ie}=1\text{K}$, $h_{fe}=100$) as the matching device (not an exact maximum power match) to the load $16\ \Omega$. Draw the schematic circuit.

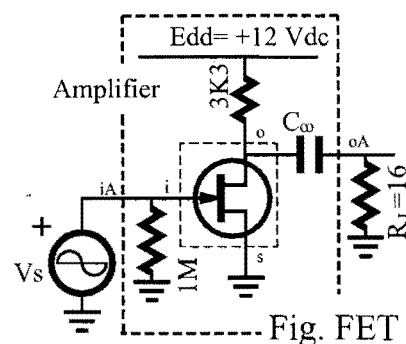(iii)(7 pts) Find the new power output to the speaker.



Q5: (20 pts) Class AB bias design:

- (i)(10 pts) Draw the V_{be} multiplier bias schematic circuit with the bias Tr. Q_1 , and the pair of the power Tr. Q_p , and Q_n .
- (ii)(5 pts) The circuit constants are: the bias constant current $I_{bias}=4$ mA, $I_Q=3$ mA (I_c of Q_p and Q_n , $I_s=10^{-13}$ A) and the small bias Tr Q_1 of $I_s=10^{-14}$ A and $V_T=25$ mV. Design V_{be1}
- (ii) (5 pts) Design R_1 , and R_2 . Neglect I_b of $Q_1, Q_{p,n}$.

Q6: (20 pts) A Darlington Tr linear feed-back amplifier is shown on the right.

(i)(5 pts) Identify whether the feedback is positive or negative. (No guess but mark as in the class lecture) (ii)(5 pts) Find A_{v_o} and (iii)(5 pts) A_{v_f} , and (iv)(5 pts) β and check if $\beta = R_1/R_f$. The circuit constants are: $h_{ie} = 3 \text{ K}$, $h_{fe} = 400$, $R_1 = 2.2 \text{ K}$, $R_f = 220 \text{ K}$, $R_c = 3.3 \text{ K}$, $R_s = 0$, and $R_L = \infty$.

(hint: set R_f symbolical and all the rest numerical, and calculate open loop gain A_{v_o} as $R_f \rightarrow \infty$ and A_{v_f} as $R_f = 220 \text{ K}$).

