

# UNIVERSITY OF SWAZILAND

FACULTY OF SCIENCE  
**Department of Electrical and  
Electronic engineering**

**July 2018**

## **SUPPLEMENTARY EXAMINATION**

Title of the paper:

**Fundamentals of Power Machines**

Course Code: **EEE352**

Time allowed: **Three Hours**


Instructions:

1. Answer all questions in the following pages.
2. The answer must be written in the space provided in the question book; those in elsewhere considered invalid. Use the answer book as a scratch pad. Both question and answer book must be handed-in and marked with name and ID.
3. This paper has 6 pages, including this page.

**DO NOT OPEN THIS PAPER UNTIL  
PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR**

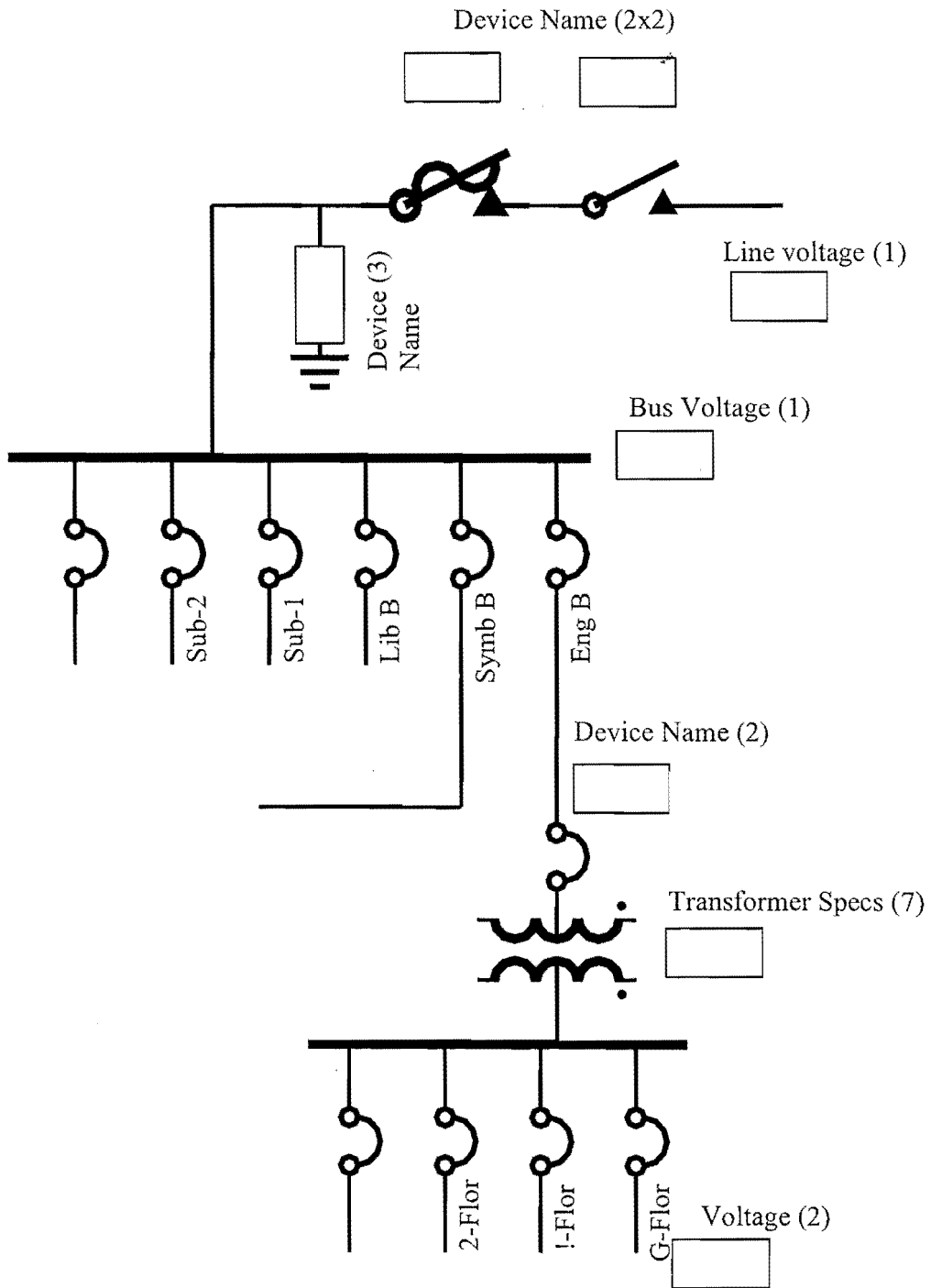**Q1: (20 pts)** The UniSwa distribution system structure is shown below.

Fill in the blank boxes the proper data indicated near the box. (pts assigned in the figure)



**Q2: (20 pts)** Draw a per-unit reactance diagram for the balanced 3- $\Phi$  system shown in Fig. Q2-1. Choose 80 MVA and 66 KV at the transmission line as the system base. (8 pts for structure; -2 pts for each component mistake until a total 12)

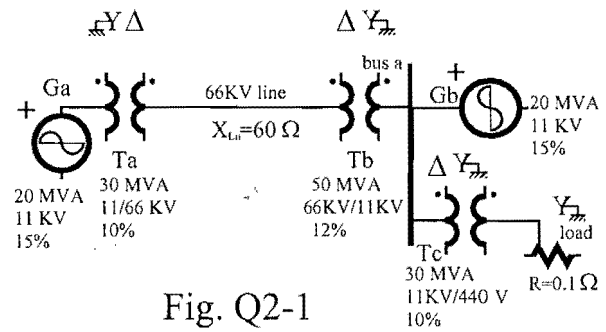


Fig. Q2-1

**Q3: (20 pts)** 3 impedances,  $Z_{ab}=3\angle 0^\circ$ ,  $Z_{bc}=4\angle 60^\circ$ , and  $Z_{ca}=5\angle 90^\circ \Omega$ , are connected in  $\Delta$ . This  $\Delta$ -connected load is supplied by a 60 Hz, balanced positive sequence Y-connected 3-phase source,  $E_a=220\angle 0^\circ$  V. Determine (i)(10 pts). the total line current; (ii)(10 pts). the line current of each phase.

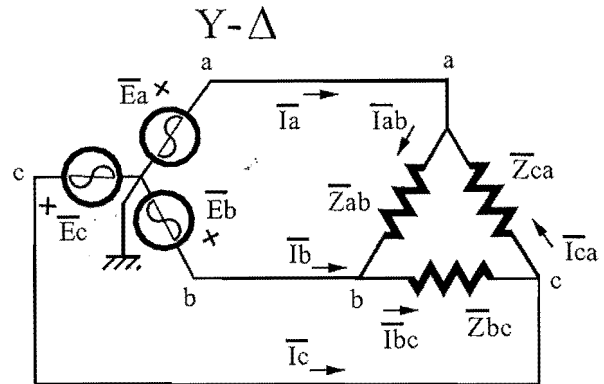


Fig. Q3-1

**Q4(20 pts):**

- (i)(4 pts) Given a 300 rpm, 60 Hz, and 3- $\Phi$  synchronous machine, find how many pairs of poles per phase?
- (ii)(4 pts) Describe the prominent differences between a synchronous generator and a synchronous motor.
- (iii)(12 pts) (a). Draw a complete transformer equivalent circuit.  
(b). Maximize or minimize which components to make a CT.  
(c). Maximize or minimize which components to make a PT.

**Q5(20 pts):** A rotating magnetic field, shown in Fig. Q5-1 has two coils Ch and Cv; each is energized respectively by the current:

$$i_h = I \cdot \sin.\omega_e t \quad i_v = I \cdot \cos.\omega_e t$$

such that  $i_h$  produces a field Bh and  $i_v$  a field Bv. where  $\omega_e$  is electric frequency.

(i)(15 pts). Prove the resultant magnetic field will rotate at a mechanical angular speed  $\omega_m = \pm\omega_e$ . (ii)(5 pts) Find out the rotating is CCW or CW.

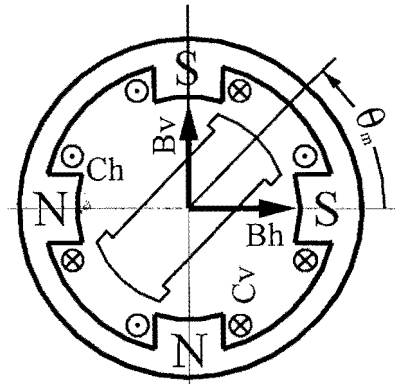


Fig. Q5-1