

UNIVERSITY OF ESWATINI

FACULTY OF SCIENCE & ENGINEERING

DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING

RESIT EXAMINATION

DECEMBER 2018

TITLE OF PAPER: BASIC ELECTRICAL ENGINEERING

COURSE CODE: EEE251

DURATION: 3 HOURS

INSTRUCTIONS:

1. There are five (5) questions in this paper. Answer question 1 and any other three (3) questions.
2. Each question carries equal marks.
3. Start each question in a new page.

This paper should not be opened until permission has been given by the invigilator.

This paper contains six (6) pages including this page.

Question 1

- a. Describe a rheostat and potentiometer. Give two examples where they can be used. [2 Marks]
- b. Using simple circuit diagrams illustrate how each can be connected in a circuit. [4 Marks]
- c. An experimenter building the voltage circuits shown in Figure Q.1c predicted that varying the resistance **R2** and **R3** should give the results shown on the graphs below the circuits.
- (i) Make pairs of each voltage divider circuit (a) or (b) with a corresponding graph (c) or (d). Give reasons for your pairs. Further determine what the axis variables **X** and **Y** should be. [6 Marks]
- (ii) Define the labeling of the graphs by working out, from the circuit variables, expressions for the voltages labelled **A**, **B**, **C**, **D** and **E**. [10 Marks]

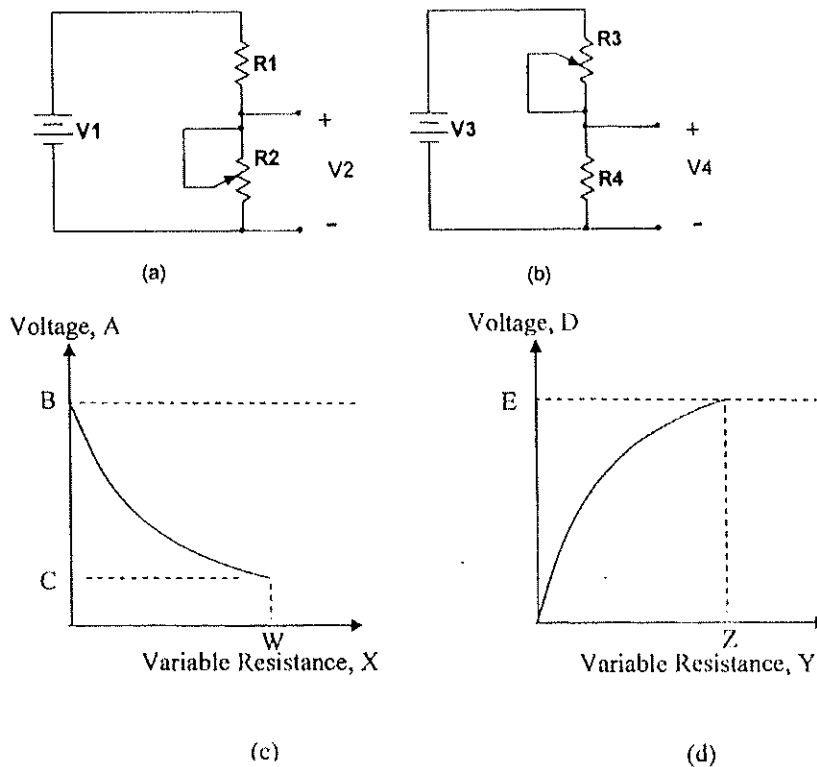


Figure Q.1c

- d. Determine the ratio of powers dissipated in two resistors, each having the same length and each made of copper wire of circular cross section, but one having a diameter twice that of the other, and each being connected across the same voltage. [3 Marks]

Question 2

- a. Use wye-delta or delta-wye transformation to evaluate the current supplied by the source in Figure Q.2a.

[10 Marks]

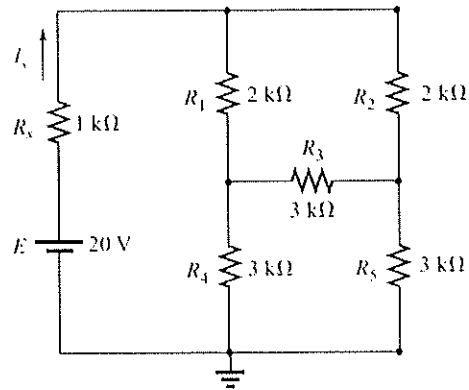


Figure Q.2a

- b. In Figure Q.2b, use the mesh current analysis technique to find;
- The loop and branch currents.
 - The voltage across 1Ω and 4Ω resistor.

[10 Marks]

[5 Marks]

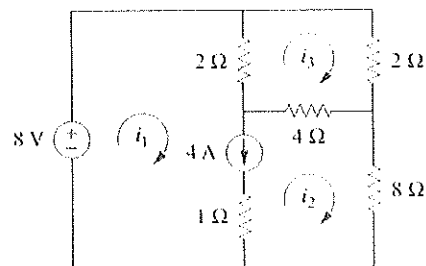


Figure Q.2b

Question 3

- a. Consider the circuit shown in figure Q3a.
- Find the Thevenin equivalent of the circuit across the points a and b. [5 Marks]
 - If a variable resistor were connected between the points a and b, what will be the maximum power dissipated in the variable resistor? [2 Marks]

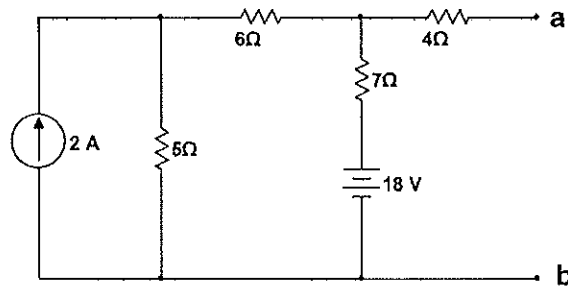


Figure Q.3a

- b. Use nodal analysis to find the voltage through the 4 Ω resistor shown in figure Q3b. [8 Marks]

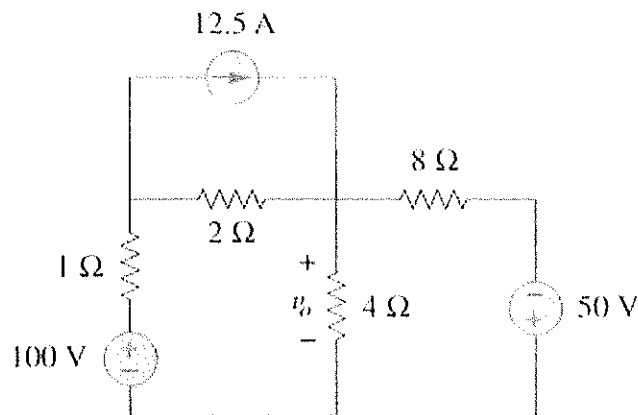


Figure Q.3b

- c. The circuit shown in Figure Q.3c has two current sources one of which is a voltage dependent source. Find the following:
- The voltage across the independent current source. [6 Marks]
 - The power dissipated in each resistor. [2 Marks]
 - The total power supplied by the sources. [2 Marks]

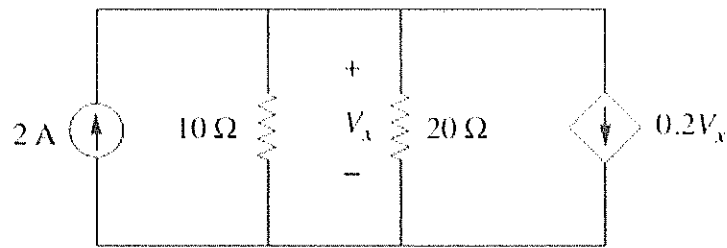


Figure Q.3c

Question 4

- a. A $4\ \Omega$ resistor in series with a $7.96\ \text{mH}$ inductor is connected across a $240\ \text{V}$ $60\ \text{Hz}$ source. Determine:
- The total impedance. [3 Marks]
 - The input current [2 Marks]
 - The voltages across the resistor and the inductor. [4 Marks]
 - Draw a phasor diagram showing the current and the voltages. [4 Marks]
 - The power factor. [2 Marks]
 - The input power. [2 Marks]
- b. Given that an inductor draws $5\ \text{A}$ of current at $230\ \text{V}$ $50\ \text{Hz}$, find the inductive reactance and the inductance. [4 Marks]
- c. Given that a capacitor draws $2\ \text{A}$ of current at $230\ \text{V}$ $50\ \text{Hz}$. Find the capacitive reactance and the capacitance. [4 Marks]

Question 5.

- a. Consider the circuit shown to answer the following. Assume the capacitor has already been fully charged.

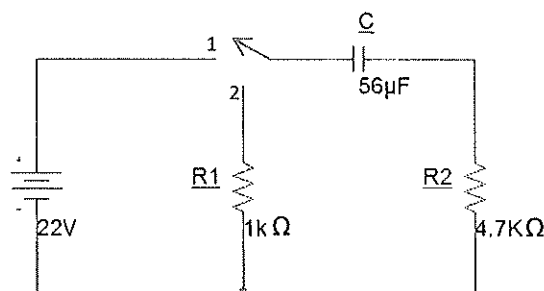


Figure Q.5a

- i. Determine the time it takes for the capacitor to discharge i.e. when the switch is placed at position 2. [2 Marks]
 - ii. Give the mathematical expression for v_c and i_c when capacitor is discharging. [4 Marks]
 - iii. Sketch the transients of v_c and i_c . [4 Marks]
- b.** A coil of inductance 80mH and resistance 120 Ω is connected to a 230 V, 50Hz supply, in parallel with it is a 60 μ F capacitor in series with a 40 Ω resistor as shown in Figure Q.5b Determine:
- iv. The total impedance of the circuit. [6 Marks]
 - v. The power factor of the circuit stating whether it is leading or lagging. [3 Marks]
 - vi. The total Active Power taken from the supply. [2 Marks]
 - vii. The total reactive power supplied. [2 Marks]
 - viii. The apparent power supplied. [2 Marks]

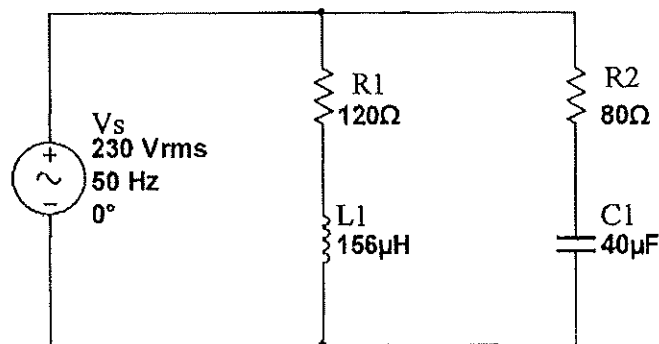


Figure Q.5b

End of Paper