

University Of Eswatini
Faculty of Science and Engineering
Department of Electrical and Electronic Engineering

Main Examination, December 2018

TITLE of Paper: **Analogue Electronics I / Analogue Design I**

Course Number: **EEE321 / EE321**

Time allowed 3 hours

Instructions:

- 1. EE321 Students answer any Four (4) questions in Section A**
- 2. EEE321 students answer any Three (3) questions in Section A and One (1) question in Section B.**
- 3. Each question carries 25 marks.**
- 4. Marks for each question are shown at the right hand margin.**

This paper contains 7 pages including this one.

This paper should not be opened until permission has been granted by the invigilator.

Section A

Question 1

- State the three modes of operation of an NPN transistor and tabulate the bias conditions of the junctions. [6]
- For the circuit **Figure 1** below determine the node currents I_C , I_B and I_E and determine the mode of operation of the transistor for $\beta = 100$. [8]
- Draw the voltage transfer characteristics (VTC) of a MOSFET transistor and explain how the value of v_{GS} in relation to V_t affects the changes in the modes of operation of the transistor. Write the values of V_{DS} and i_D in the saturation region. [5]
- Describe how to find the current i_D of a MOSFET in terms of the charge Q per unit length and the electron drift velocity. Assume a small v_{DS} is applied to the transistor. [6]

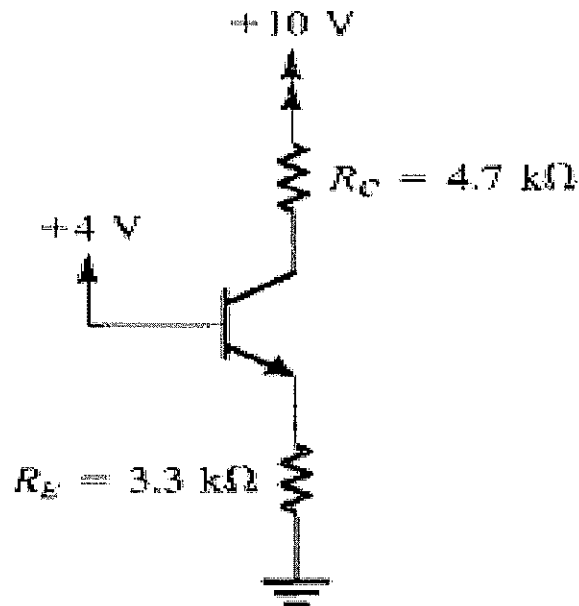


Figure 1

Question 2

a) The circuit **Figure 2(a)** is the Common Gate amplifier

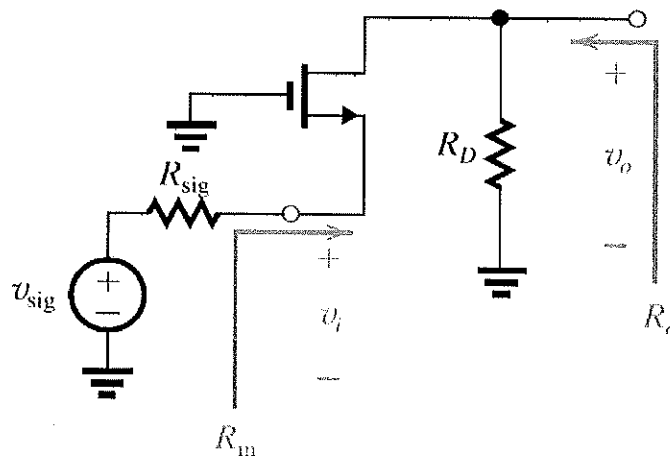


Figure 2 (a)

Find:

- i) Input resistance, R_{in} , the output resistance, R_o , and the open circuit gain A_{vo} [6]
- ii) $G_V = \frac{v_o}{v_{sig}}$, assuming R_L is connected at the output. [6]

b) Given the circuit shown in **Figure 2(b)** below,

- a. Draw the small signal equivalent circuit [3]
- b. Find R_{in} [6]
- c. Show that it has a gain of unity hence the name “Emitter follower” [4]

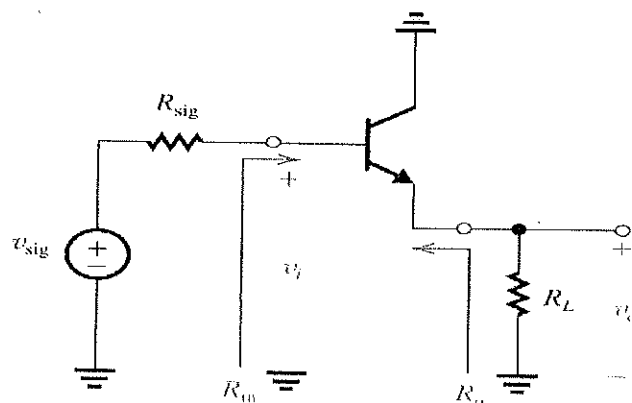


Figure 2 (b)

Question 3

Consider the Common-Source amplifier circuit, **Figure 3** below.

- a) Draw the small signal equivalent circuit. [3]
- b) Find
 - i) The input resistance R_{in} [1]
 - ii) The voltage gain G_V [4]
 - iii) The output resistance R_{out} [2]

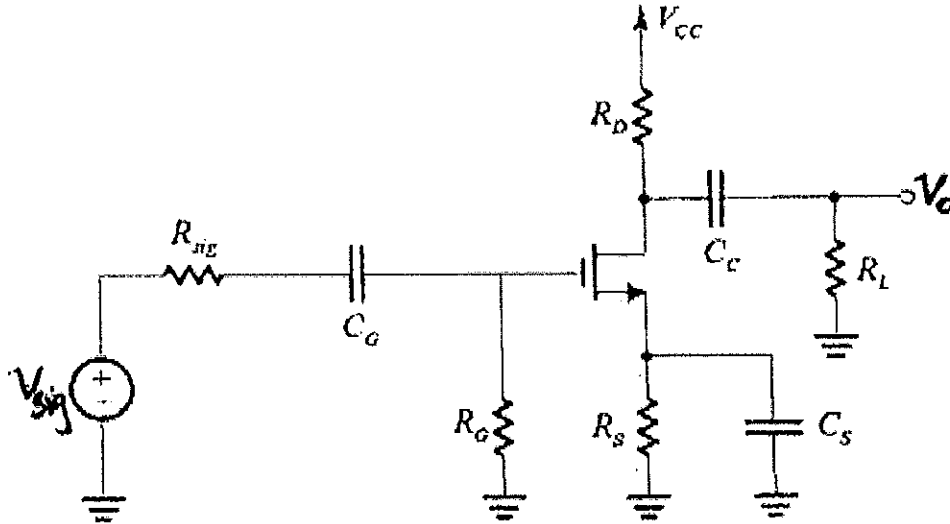


Figure 3

- c) For a Common-Emitter amplifier with Emitter resistance, R_e
 - a. Draw the **circuit diagram** and its **equivalent circuit** after using the *T-model* to replace the transistor. [3]
 - b. Find the following
 - i. The input resistance R_{in} , [4]
 - ii. The output resistance R_{out} and [2]
 - iii. The overall gain G_V given that a load resistance R_L is connected at the output. [6]

Question 4

- a) A BJT operating at $I_C = 2mA$ has $C_\mu = 1pF$ $C_\pi = 10pF$ and $\beta = 150$. Calculate:
 - i) f_T [4]
 - ii) f_β [4]
- b) For the op-amp inverting integrator circuit,
 - i) Draw and label the circuit diagram. [3]
 - ii) Determine the voltage across the capacitor. [4]
 - iii) Determine output voltage. [2]

c) For a $0.08 \mu\text{m}$ process technology for which $t_{ox} = 15\text{nm}$ and $\mu_n = 550\text{cm}^2/\text{V}\cdot\text{s}$. Given that the transistor is operating in saturation with $I_D = 0.2\text{mA}$ with $\frac{W}{L} = 20$, Find

- i) C_{ox} [2]
- ii) k'_n [2]
- iii) V_{ov} [4]

Question 5

Consider the common-emitter amplifier shown in **Figure 5** under the following conditions:

$R_{sig} = 5\text{k}\Omega$, $R_1 = 33\text{k}\Omega$, $R_2 = 22\text{k}\Omega$, $R_E = 3.9\text{k}\Omega$, $R_C = 4.7\text{k}\Omega$, $R_L = 5.6\text{k}\Omega$, $V_{CC} = 5\text{V}$, $r_o = 300\text{k}\Omega$, $\beta = 120$, dc collector current, $I_C = 0.3\text{mA}$, $V_T = 25\text{mV}$, $C_\mu = 1\text{pF}$, $f_T = 700\text{MHz}$, $r_x = 50\Omega$, Find

- a) C_π [5]
- b) The mid-band voltage gain A_M [8]
- c) The input capacitance C_{in} [4]
- d) The effective source resistance R'_{sig} [4]
- e) The upper-3dB frequency f_H [4]

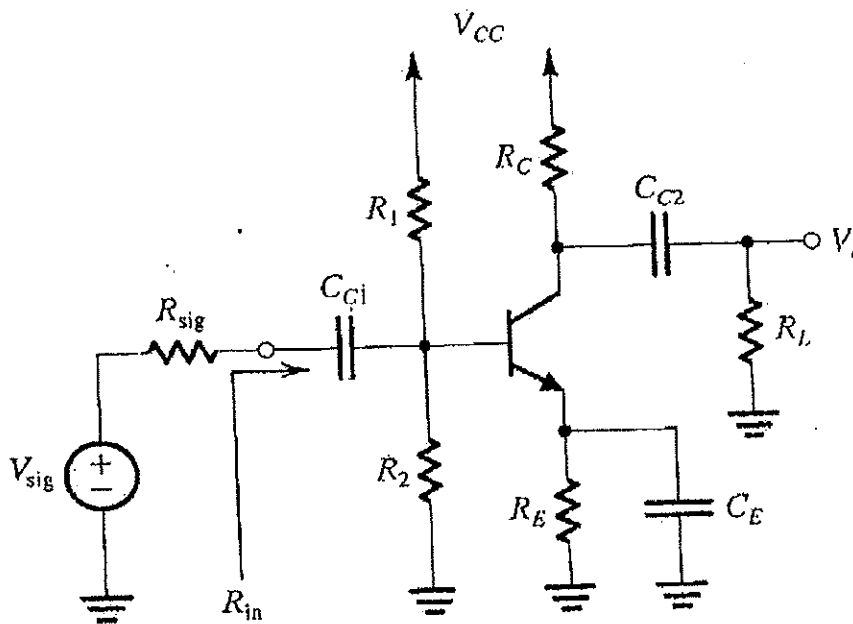


Figure 5

Section B

Question 6

a) Given the half wave rectifier, Figure 6, below

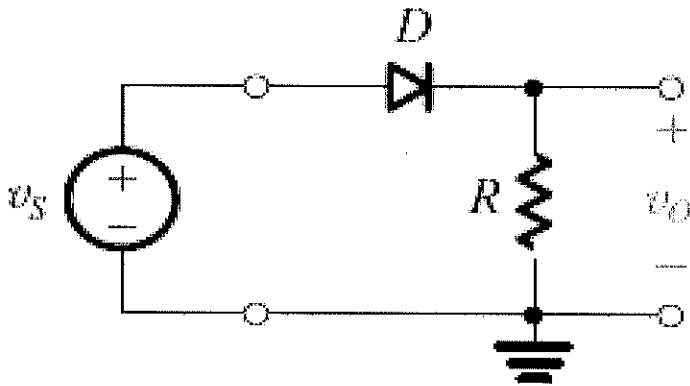


Figure 6

- i) Find the RMS value of the load voltage [4]
- ii) Find the RMS value of the load current [4]
- iii) Given that the current $i(t) = 5 \sin(2\pi 100t)$ and the voltage is $v_o = 10 \sin(2\pi 300t)$ find the values of the RMS voltage and RMS current above. [4]
- iv) Show that the efficiency of the rectifier above $\eta = 0.405$ [4]

- b) State three types of regulators [3]
- c) List and describe three elements of a regulator [6]

Question 7

- a) In the circuit Figure 7 below
 - i) Identify the type of regulator. [2]
 - ii) Identify the four elements that make up a regulator. [4]
 - iii) Find the output voltage. [3]

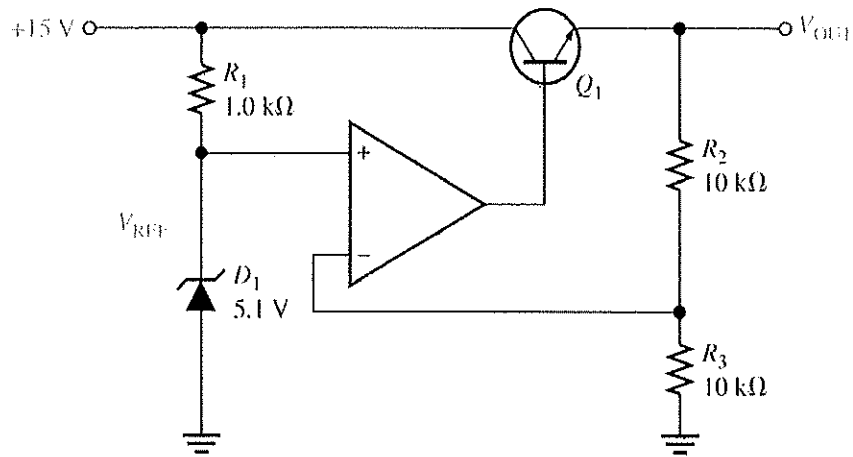


Figure 7

- b) For a full wave rectifier
- i) Find the mean value of the load current and the load voltage [4]
 - ii) Show that its efficiency is 0.81 [6]
- c) Describe the operation of a shunt regulator [6]
-