

UNIVERSITY OF ESWATINI
MAIN EXAMINATION, FIRST SEMESTER
DECEMBER 2018

FACULTY OF SCIENCE AND ENGINEERING

**DEPARTMENT OF ELECTRICAL AND ELECTRONIC
ENGINEERING**

TITLE OF PAPER: ANALOGUE ELECTRONICS II
COURSE CODE: EEE421

TIME ALLOWED: THREE HOURS

INSTRUCTIONS:

1. **There are five questions in this paper. Answer any FOUR questions.
 Each question carries 25 marks.**
2. **If you think not enough data has been given in any question you may
 assume any reasonable values.**
3. **Some useful formulas are given in the last page.**

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION
HAS BEEN GIVEN BY THE INVIGILATOR**

THIS PAPER CONTAINS SEVEN (7) PAGES INCLUDING THIS PAGE

QUESTION ONE (25 marks)

A BJT differential amplifier shown in Figure-Q1 uses matched transistors.

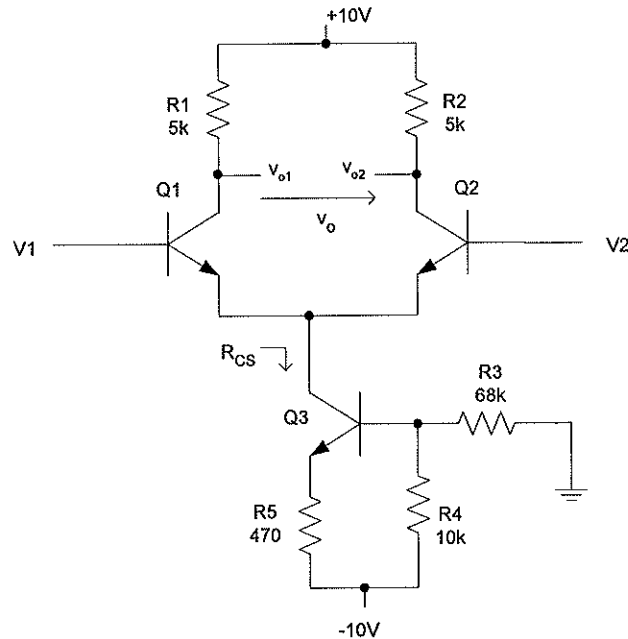


Figure - Q1

- (a) Under no input signal, calculate the collector current of Q_3 and the collector voltages of Q_1 and Q_2 . You may assume that the gains of the transistors are high. (6 marks)
- (b) (i) Draw the common mode half circuits and derive an expression for the common mode gain for a single ended output. (5 marks)
- (ii) Calculate the common mode gain in (i) above if $R_{CS} = 100k$. (4 marks)
- (iii) Find the highest common mode gain if the output is taken differentially. Assume that the tolerance of R_1 and R_2 are $\pm 2\%$. (5 marks)
- (iv) Find an expression for the common mode input impedance and calculate its value. (5 marks)
- $\beta = 100 \quad V_A = 85V \quad r_\mu = \infty$

QUESTION TWO (25 marks)

An enhancement mode NMOS amplifier shown in Figure-Q2. Assume that the devices Q_1 and Q_2 are matched.

 


Figure - Q2

- (a) When no input signal is present, find the differential input voltage $V_D = V_1 - V_2$ required if $V_{D1} = 10V$.

(6 marks)

- (b) Draw the differential half circuits for the ac signals and derive expressions for the voltage gains $\frac{v_{o1}}{v_d}$, $\frac{v_{o2}}{v_d}$, $\frac{v_o}{v_d}$ and calculate their values. The differential input signal voltage $v_d = v_1 - v_2$ and symmetric dc biasing is used at the gates.

(9 marks)

- (c) Find the value of common mode gain for single ended output and calculate the $CMRR$ in dB .

(6 marks)

- (d) Estimate the input offset voltage using following data.

Tolerance of resistors $R_1, R_2 = \pm 3\%$

Tolerance of $\left(\frac{W}{L}\right)$ ratio = $\pm 5\%$

You may assume that the tolerance of other parameters are negligible.

(4 marks)

QUESTION THREE (25 marks)

(a) An integrated circuit amplifier is shown in Figure-Q3(a). Assume that the transistors are matched and $\beta = 100$ and $V_A = 80V$.

- (i) What is the function of Q_1 and Q_3 ? Calculate the collector current of Q_1 at no signal. (3 marks)
- (ii) Derive an expression for the voltage gain $\frac{v_o}{v_{in}}$ and calculate its value. (6 marks)
- (iii) If this amplifier is connected to a load of $75k$, find the resulting voltage gain. (4 marks)
- (iv) Derive the input impedance R_{in} and the output impedance R_o . (4 marks)

 


Figure-Q3(a)

 


Figure-Q3(b)

(b) A current mirror implemented with NMOS devices is shown in Figure-Q3(b). You may use the data given below.

$$L_1 = L_2 = 5\mu m \quad W_2 = 50\mu m \quad |V_t| = 2V \quad \mu C_{OX} = 65 \frac{\mu A}{V^2}$$

$$V_A = 80V \quad I_o = 250\mu A \quad I_{ref} = 50\mu A$$


- (i) Calculate the value of W_1 proving any formula you use. (5 marks)
- (ii) Find the value of the resistance R . (3 marks)

QUESTION FOUR (25 marks)

- (a) Derive the necessary and sufficient condition that must be satisfied by a sinusoidal oscillator to function.

(5 marks)

- (b) Consider the oscillator circuit shown in Figure-Q4.

 **Figure -Q4**

- (i) Derive an expression for loop gain and hence find the frequency of oscillation. How do you determine R_1 and R_2 ?

(10 marks)

- (ii) Calculate component values for a oscillation frequency of 50KHz satisfying the bounds, that any resistor value $> 2k$ and any capacitor value $> 0.5nF$.

(5 marks)

- (iii) Suggest a modification to this circuit to ensure sinusoidal output. You may not need to find any component values.

(5 marks)

QUESTION FIVE (25 marks)

Consider the Class B amplifier shown in Figure-Q5.

 


Figure - Q5

- (a) Derive an expression for power efficiency of the circuit and calculate the maximum efficiency possible. (7 marks)
- (b) Find an expression for the maximum power dissipated by each device and power delivered to the load at that instance. (7 marks)
- (c) The amplifier uses a supply of $\pm 20V$ and delivers $15W$ to an 8Ω load. Find the peak current drawn from the supply, the total supply power, power conversion efficiency and the maximum power dissipation of each transistor. (11 marks)

1. SOME USEFUL MOSFET EQUATIONS

$$i_D = \mu_n C_{ox} \frac{W}{L} \left[(v_{GS} - v_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right] \text{ in triode region}$$

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - v_t)^2 \text{ in saturation region}$$

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - v_t)^2 (1 + \lambda v_{DS}) \text{ in saturation region with Channel Modulation effect}$$

$$V_A = \frac{1}{\lambda}$$

2. Unless otherwise stated $V_{BE(ON)} = 0.6V$ and $V_T = 0.025V$.