

UNIVERSITY OF ESWATINI

FACULTY OF SCIENCE & ENGINEERING

DEPARTMENT OF ELECTRICAL & ELECTRONIC ENGINEERING

RESIT EXAMINATION

JANUARY 2020

TITLE OF PAPER: BASIC ELECTRICAL ENGINEERING

COURSE CODE: EEE251

DURATION: 3 HOURS

INSTRUCTIONS:

1. There are five (5) questions in this paper. Answer question 1 and any other three (3) questions.
2. Each question carries equal marks.
3. Start each question in a new page.

This paper should not be opened until permission has been given by the invigilator.

This paper contains eight (8) pages including this page.

Question 1 [25 Marks]

- a. Consider breakdown strength of an insulator;
- Define breakdown strength of an insulator. [2 marks]
 - Why should we care about breakdown strength of an insulator? [2 marks]
- b. Show the connections required to establish $4k\Omega$ from three terminals of a $10k\Omega$ potentiometer. [2 Marks]
- c. How would you check the status of a fuse with an ohmmeter? [2 Marks]
- d. A short circuit across a current source draws 15A. If a 10Ω resistor across the source draws 13A, what is the internal resistance of the source? [3 Marks]
- e. A copper wire has a resistance of 50Ω at 10^0C . What is the maximum operating temperature if the resistance of the wire is to increase by at most 10 percent? [4 Marks]
- f. Two copper wires each of diameter 0.64mm and length 1.2m are used for connecting the positive and negative terminals of a 5V d.c. supply to an electronic circuit board which takes a current of 0.5A. Calculate the supply voltage appearing across the electronic circuit board. You are given that the resistivity of copper is $1.7 \times 10^{-8} \Omega\text{-m}$. [6 Marks]
- g. What is the greatest voltage and current that can be applied across a $\frac{1}{8}W$, $2.7M\Omega$ resistor without causing it to overheat? [4 Marks]

Question 2 [25 Marks]

- a. Reduce the resistor network between terminals a and b of Figure Q.2a to a single resistor. [9 Marks]

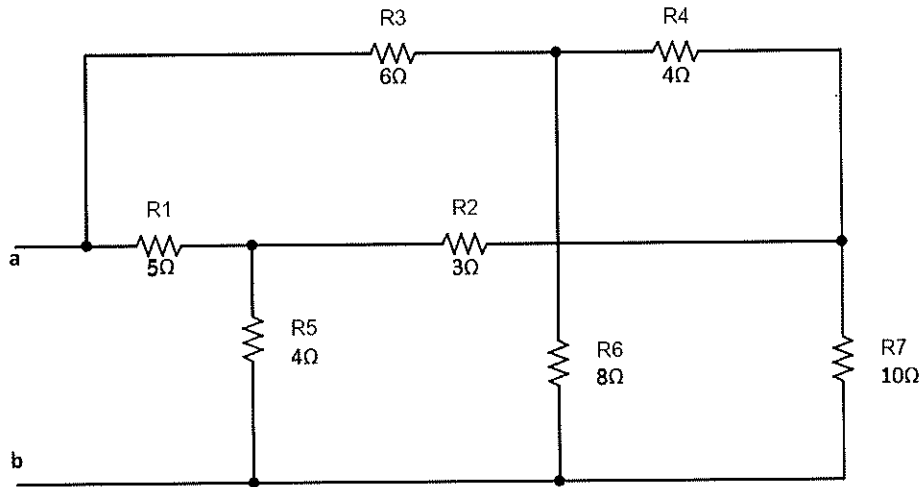


Figure Q.2a

- b. Using mainly source transformation find the current through the 6Ω resistor in Figure Q.2b. [5 Marks]

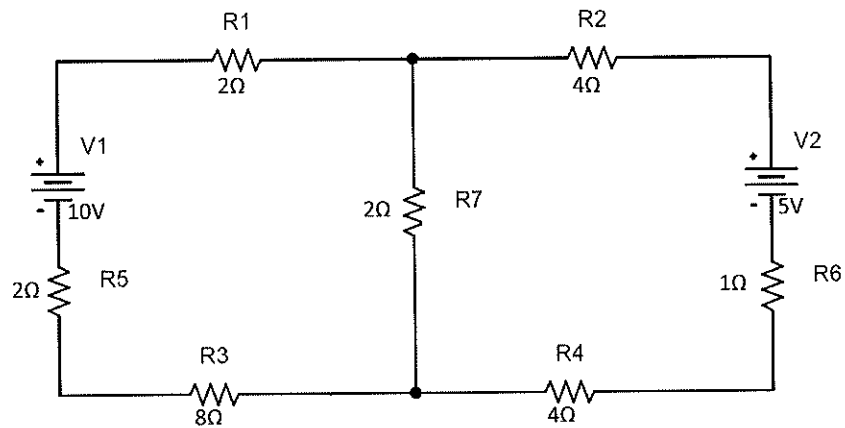


Figure Q.2b.

- c. Consider the circuit of Figure Q.2c, for the following;
- Find all the branch currents in the circuit. [8 Marks]
 - Find the power supplied by the current source. [3 Marks]

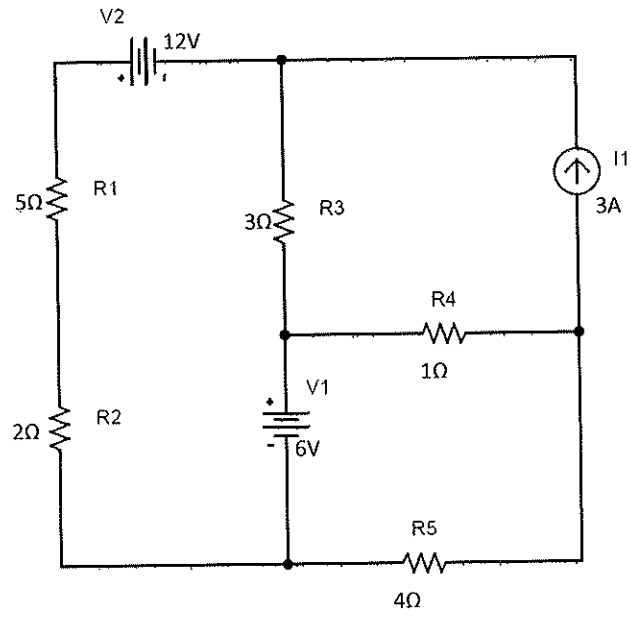


Figure Q.2c

Question 3 [25 Marks]

- a. Use nodal analysis to find current I_1 and I_2 in the circuit shown in Figure Q.3b. [10 Marks]

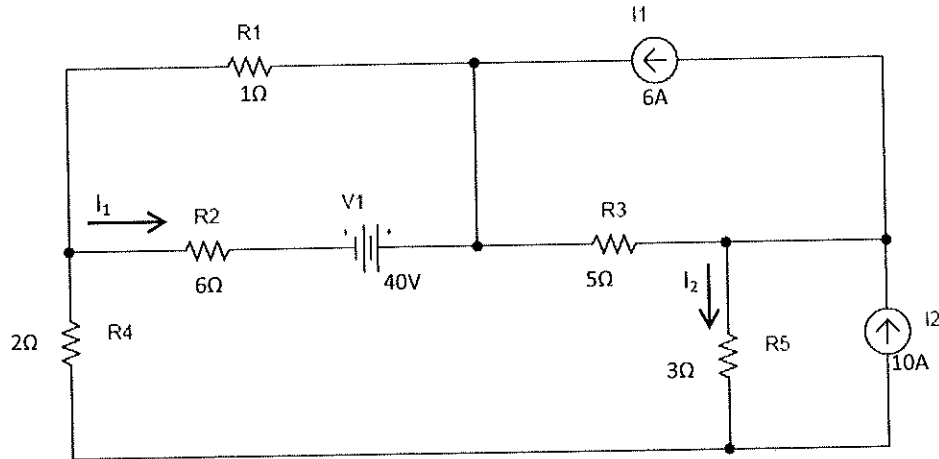


Figure Q.3b.

- b. Find the Thevenin equivalent circuit with respect to terminal a,b for the circuit shown in Figure Q.3b. [7 Marks]

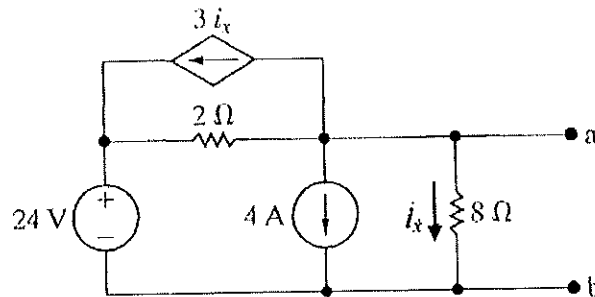


Figure Q.3b

- c. Using superposition find the node voltages V_1 and V_2 in the circuit shown in Figure Q.3c. [8 Marks]

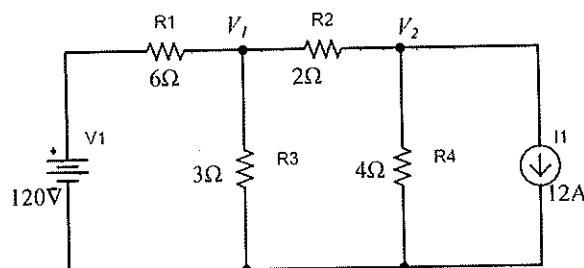


Figure Q.3c

Question 4 [25 Marks]

a. Given the circuit shown in Figure Q.4a, answer the following:

i. Use mesh analysis to determine current I_1 and I_2

[16 Marks]

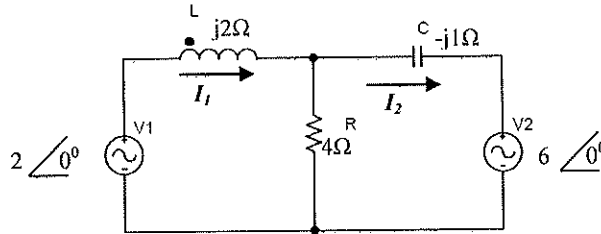


Figure Q.4a

ii. Find the power supplied (or absorbed) by each source of the circuit.

[4 Marks]

b. An impedance $Z_1 = (4 + j4)\Omega$ is connected in parallel with an impedance $Z_2 = (12 + j6)\Omega$. If the input reactive power is 2500VAR (lagging), what is the total active power?

[5 Marks]

Question 5 [25 Marks]

- a. Consider the circuit shown to answer the following. Assume the capacitor has already been fully charged.

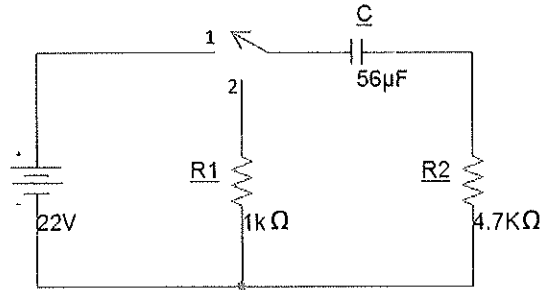


Figure Q.5a

- i. Determine the time it takes for the capacitor to discharge i.e. when the switch is placed at position 2. [2 Marks]
 - ii. Give the mathematical expression for v_c and i_c when capacitor is discharging. [4 Marks]
 - iii. Sketch the transients of v_c and i_c . [4 Marks]
- b. A coil of inductance 0.1 H is connected across a 50 V, 60 Hz supply, in parallel with it is a 100 µF capacitor which is also in parallel with a 30 Ω resistor as shown in Figure Q.5b. Determine:
- i. The total impedance of the circuit. [4 Marks]
 - ii. The branch currents [3 Marks]
 - iii. The total Active Power taken from the supply. [2 Marks]
 - iv. The total reactive power supplied. [2 Marks]
 - v. The apparent power supplied. [2 Marks]
 - vi. The power factor of the circuit stating whether it is leading or lagging. [2 Marks]

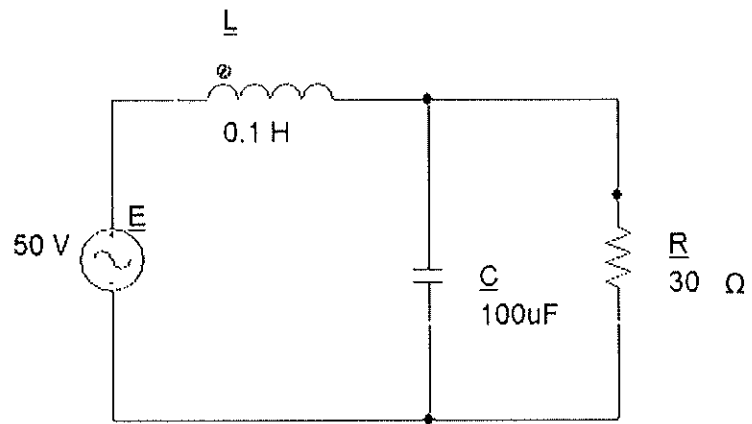


Figure Q.5b.

End of Paper