

UNIVERSITY OF SWAZILAND

FACULTY OF SCIENCE
DEPARTMENT OF PHYSICS

2006 MAIN EXAMINATION

Title of the Paper: **DIGITAL ELECTRONICS**
Course Number: **P411**
Time Allowed: **Three Hours.**

Instructions:

1. To answer, pick any five out of six questions in the following pages.
2. Each question carries 20 points.
3. This paper has 7 pages, including this page.

**DO NOT OPEN THE PAPER
UNTIL PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR.**

QUESTION 1:

(a): Transform the Boolean function, $F(A, B, C, D, E) = AB + D\bar{E}$, into

- (i). a K-map,
- (ii) a function in the following format:

$$F(A, B, C, D, E) = \prod[(n_1, n_2, \dots, n_B, n_C, \dots, n_1F)]_{\text{hex}}$$

The number in the above brackets must be hexadecimal.

(Hint: Expand this function into canonical form first.) (10 marks)

(b): Perform the subtraction with the following numbers, using any complement. Check the answer by straight subtraction.

- (i). $5.25 - 32.1_{\text{dec}}$
- (ii). $11.01 - 110.1_{\text{bin}}$ (10 marks)

QUESTION 2:

Using the tabulation method, simplify the following Boolean function F into the SOP answer:

$$F(v, w, x, y, z) = \Sigma(0, 4, C, D, E, F, 10, 11, 12, 13, 16, 1E)_{\text{hex}}$$

(hex number in the brackets of the above function) (20 marks)

QUESTION 3:

(a): With the help of a K-map, obtain the simplified expressions in (i) SOP and (ii) POS of one of the following two Boolean Functions: (you are allowed to choose only one function and obtain the two expressions of the one you picked). In the equations, d is the don't-care conditions.

$$G(A, B, C, D) = \overline{ABC} + \overline{ABD} + \overline{ABC\bar{D}} + \overline{ABD}, \quad d = ABC$$

$$F(A, B, C, D) = (\overline{A} + \overline{B} + D)(A + B + \overline{D})(A + \overline{B} + C + D), \quad d = (\overline{A} + \overline{D})$$

(10 marks)

(b): Implement the Boolean function, $F(A, B, C, D, E) = (A + \overline{B})(ACD + E)$, with only NAND gates and nothing but NAND gates. Complement in-puts are available only at input terminals, nowhere else. The implement must have its support function. (10marks)

QUESTION 4:


(a): Implement the following function with a multiplexer of 2-bit select address xy (must have this component) and other elementary gates:

$$F(v, w, x, y) = \Sigma(0, 1, 3, 5, 8, 9)_{\text{hex}}$$

(hex number in the brackets of the above function)

(10 marks)

(b): Implement the function given in (a) with a PAL structure. Simplification is required. (10 marks)

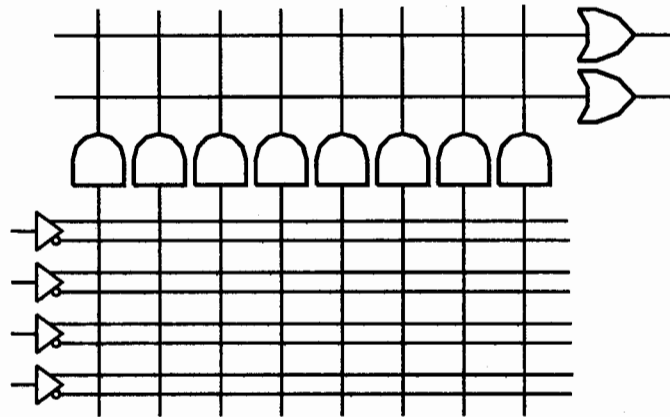

QUESTION 6:

Design, with D-ff's, a clocked sequencer to cycle repeatedly through the states: 0, 1, 2, 2, 0, 3...(repeat). Obtain a logic circuit, a state table, a state diagram, and ff input functions. (Hint: need a hidden unit) (20 marks)