

UNIVERSITY OF SWAZILAND

FACULTY OF SCIENCE

DEPARTMENT OF PHYSICS

MAIN EXAMINATION : MAY 2008

TITLE OF PAPER : ELECTRONICS II

COURSE NUMBER : P312

TIME ALLOWED : THREE HOURS

INSTRUCTIONS : ANSWER ANY FOUR OUT OF FIVE QUESTIONS

EACH QUESTION CARRIES 25 MARKS

**MARKS FOR DIFFERENT SECTIONS ARE SHOWN
IN THE RIGHT-HAND MARGIN.**

THIS PAPER HAS 7 PAGES, INCLUDING THIS PAGE.

**DO NOT OPEN THE PAPER UNTIL PERMISSION HAS BEEN GIVEN BY THE
INVIGILATOR.**

QUESTION 1

- (a) List four characteristics of an amplifier which are modified by negative feedback. (4 marks)
- (b) Draw a feedback amplifier in block-diagram form. Identify each block, and state its function. (5 marks)
- (c) A bipolar transistor has a current gain of -150 , a collector load resistor of 3000Ω and input resistance of 1000Ω .
- (i) Calculate the voltage gain of the circuit. (2 marks)
- (ii) Calculate its voltage gain when negative feedback is applied with a feedback factor of 0.05 . (3 marks)
- (d) An amplifier has a voltage gain of -650 . If 0.5% of the output voltage is fed back to the input as negative feedback, calculate the % change in the gain with negative feedback when the open-loop gain falls by 25% . (11 marks)

QUESTION 2

- (a) State the two conditions that must be satisfied by a circuit to sustain oscillations. (4 marks)
- (b) (i) Sketch the circuit of a phase-shift oscillator that uses a bipolar junction transistor and an RC ladder network. Explain how it works. (8 marks)
- (ii) Derive an expression for the attenuation coefficient of the RC ladder network in terms of the angular frequency ω , as well as the capacitive and resistive components of the network. Assume that the resistors in the network are of the same value. The same applies to the capacitors. (8 marks)
- (c) The Wien bridge network shown in Fig. 2.1 is used to build a frequency-dependent sinusoidal oscillator.
- (i) Mention the distinctive benefits of using this type of oscillator. (3 marks)
- (ii) Calculate the frequency of operation of this oscillator if the frequency-determining resistors are each $10\text{ k}\Omega$ and the frequency-determining capacitors are each $0.01\text{ }\mu\text{F}$. (2 marks)

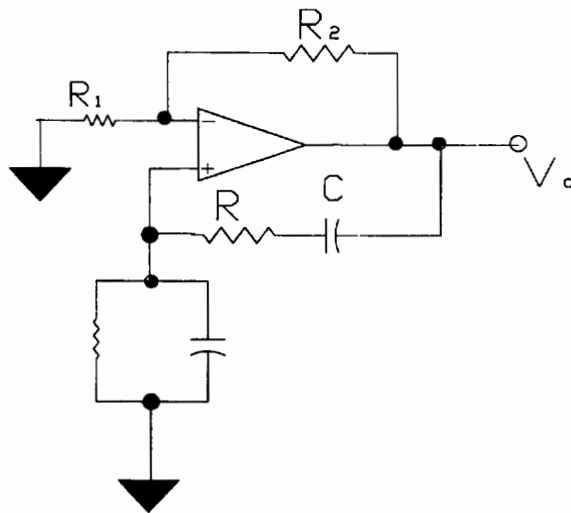


Fig. 2.1

QUESTION 3

- (a) Draw the circuit of an emitter follower, together with its equivalent circuit. Label the diagrams. (5 marks)
- (b) With the aid of labelled block diagrams explain, in detail, the concept of impedance matching for optimum voltage transfer between a signal source and a load, with specific reference to an emitter follower. (12 marks)
- (c) Derive the following expression for the output resistance of an emitter follower:

$$r_{out} = \frac{R_G + r_x}{1 + h_{fe}}$$

where R_G represents the internal resistance of the voltage source. The other symbols have the usual meaning. (8 marks)

QUESTION 4

- (a) Describe four important characteristics of an ideal operational amplifier. (4 marks)
- (b) A Darlington pair is a useful device in operational amplifiers. It consists of transistors Q1 and Q2 of current gain h_{fe1} and h_{fe2} respectively, as shown in Fig. 4.1. Show that the current gain of the pair is given by

$$h_{fe} \approx h_{fe1} \times h_{fe2} \quad (5 \text{ marks})$$

- (c) Calculate and sketch v_{out} as a function of time for the waveform given in Fig. 4.2 which represents an input to an operational differentiator. (9 marks)
- (d) Calculate the voltage gain of the circuit shown in Fig. 4.3. (3 marks)
- (e) For the circuit shown in Fig. 4.4 calculate the output voltage when $R_1 = R_2 = R_3 = 10\text{k}\Omega$, $R_4 = 100\text{k}\Omega$, $V_1 = 0.1\text{ V}$, $V_2 = 0.5\text{ V}$ and $V_3 = 0.25\text{ V}$. (4 marks)

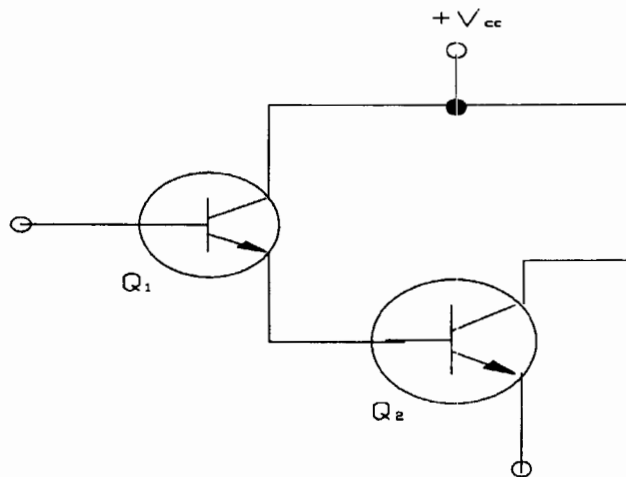


Fig. 4.1

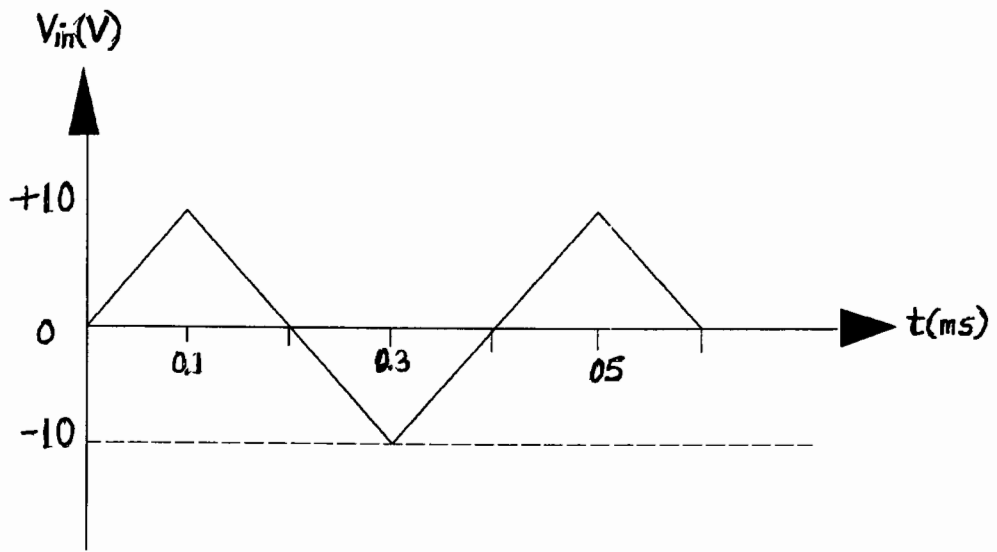


Fig. 4.2

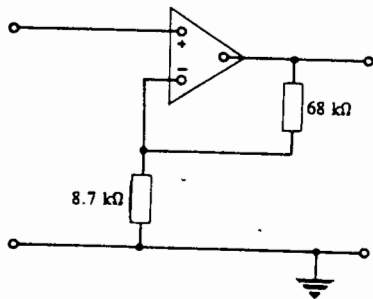


Fig. 4.3

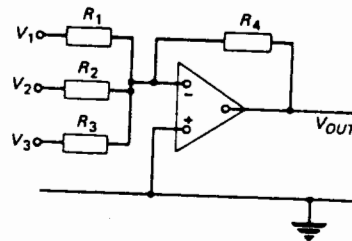


Fig. 4.4

QUESTION 5

- (a) (i) Find the inductance of the high-pass filter circuit shown in Fig. 5.1, if $T(s) = 0.50$ at a frequency of 50 MHz. (7 marks)
- (ii) What is the phase difference between V_i and V_o at this frequency? (2 marks)
- (b) The diagram in Fig. 5.2 represents a bandreject filter.

- (i) Show that the magnitude of the transfer function of the bandreject filter is given by the following relationship:

$$|T(s)| = \left[1 + \frac{1}{\left(\frac{\omega L}{R} - \frac{1}{\omega RC} \right)^2} \right]^{-\frac{1}{2}} \quad (5 \text{ marks})$$

- (ii) Use the equation in (b)(i) to derive an expression for the resonant frequency of the filter. (4 marks)
- (c) (i) What is the function of a bandpass filter? Sketch a graph of $|T(s)|$ against f to illustrate your point. Label it. (5 marks)
- (ii) Use a block diagram to demonstrate how you can build a bandpass filter using a lowpass filter and a highpass filter. (2 marks)

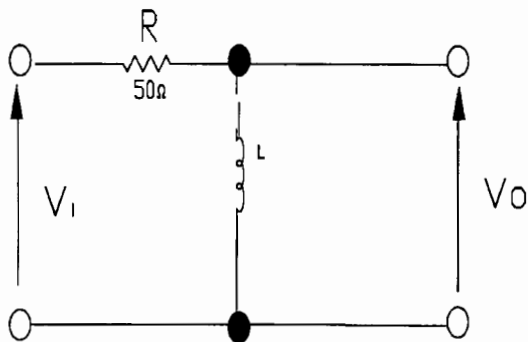


Fig. 5.1

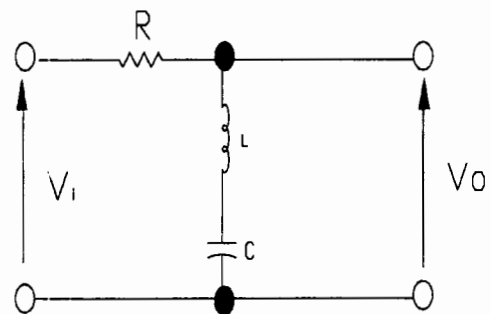


Fig. 5.2