

UNIVERSITY OF SWAZILAND

98

FACULTY OF SCIENCE

DEPARTMENT OF PHYSICS

MAIN EXAMINATION : 2010/2011

TITLE OF PAPER : ELECTRONICS I

COURSE NUMBER : P311

TIME ALLOWED : THREE HOURS

INSTRUCTIONS : ANSWER ANY FOUR OUT OF FIVE QUESTIONS

EACH QUESTION CARRIES 25 MARKS

**MARKS FOR DIFFERENT SECTIONS ARE SHOWN
IN THE RIGHT-HAND MARGIN.**

THIS PAPER HAS 8 PAGES, INCLUDING THIS PAGE.

**DO NOT OPEN THE PAPER UNTIL PERMISSION HAS BEEN GIVEN BY THE
INVIGILATOR.**

QUESTION 1

- (a) Consider the simplified voltage regulator circuit shown in Fig. 1.1. Explain, briefly, how the circuit works and state the conditions to be satisfied in order for the circuit to give a constant d.c. voltage as well as ensure that the Zener diode is not damaged. (10 marks)
- (b) The input voltage of the regulator has a minimum value of 24 V and the peak-to-peak ripple voltage is 2 V. The Zener voltage is 6.2 V and the maximum power allowed in the diode is 0.9 W.
 - (i) Calculate the load current. (2 marks)
 - (ii) Calculate the current through the series resistor when the input voltage is maximum. (3 marks)
 - (iii) Calculate the maximum current that should be allowed through the diode. (2 marks)
- (c) Fig. 1.2 is an illustration of a bridge rectifier. Derive an expression for the average current through the load resistor, with the aid of a labelled diagram. (8 marks)

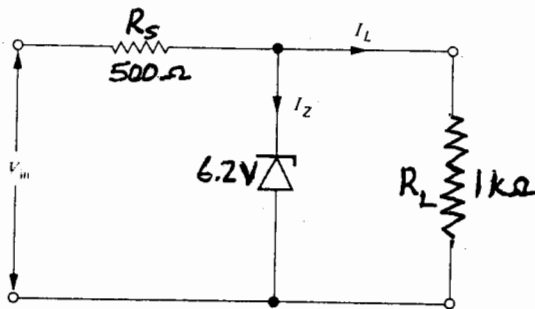


Figure 1.1

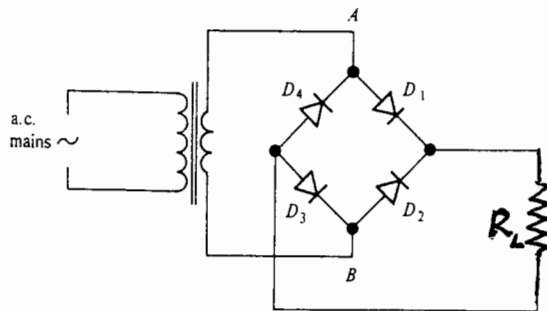


Figure 1.2

QUESTION 2

100

- (a) Consider a pnp (bipolar junction) transistor that is connected in the forward-active mode. Use a suitable diagram to explain how it works. (10 marks)

- (b) Fig. 2.1 shows a simple bipolar junction transistor amplifier circuit. The specifications of the circuit are as follows:

Collector current, $I_C = 1.5 \text{ mA}$
Collector-emitter voltage, $V_{CE} = 4.5 \text{ V}$
Transistor dc current gain, $h_{FE} = 200$
Supply voltage, $V_{CC} = 9 \text{ V}$
Base-emitter voltage, $V_{BE} = 0.6 \text{ V}$

Calculate the following:

- (i) The base-bias resistance, R_B . (4 marks)
- (ii) The load resistance, R_L . (2 marks)
- (c) The element values of the circuit shown in Fig. 2.2 are: $R_1 = 150 \text{ k}\Omega$, $R_2 = 37.5 \text{ k}\Omega$, $R_L = 7 \text{ k}\Omega$, $R_3 = 3 \text{ k}\Omega$ and $V_{CC} = 9 \text{ V}$. The d.c. current gain of the transistor is $\beta = 100$. Let $V_{BE} = 0.6 \text{ V}$.
- (i) Calculate the base voltage, V_B . (4 marks)
- (ii) Calculate the collector current, I_C . (3 marks)
- (iii) Calculate the collector-emitter voltage, V_{CE} . (2 marks)

Assume that $I_C \approx I_E$ and that the current through resistor R_2 is approximately the same as the current through R_1 , since I_B is very small.

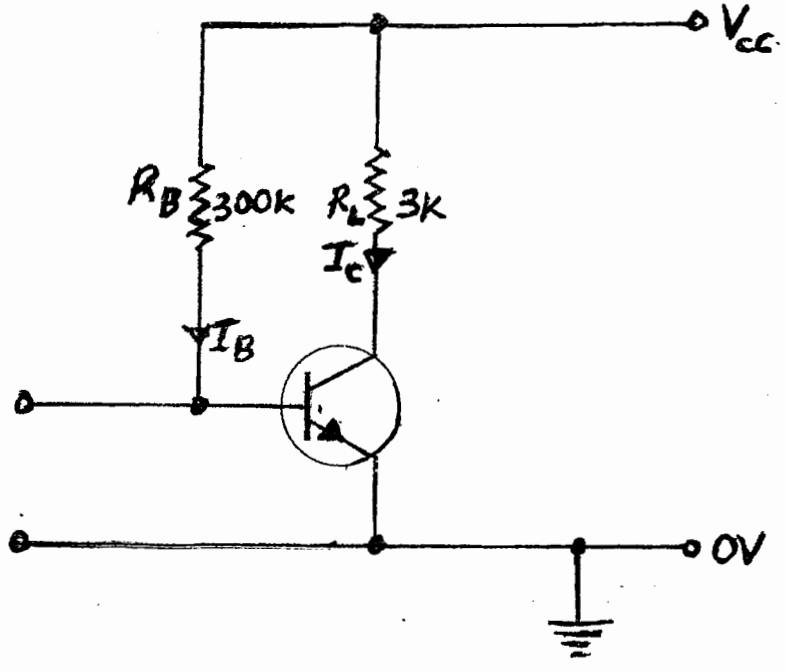


Figure 2.1

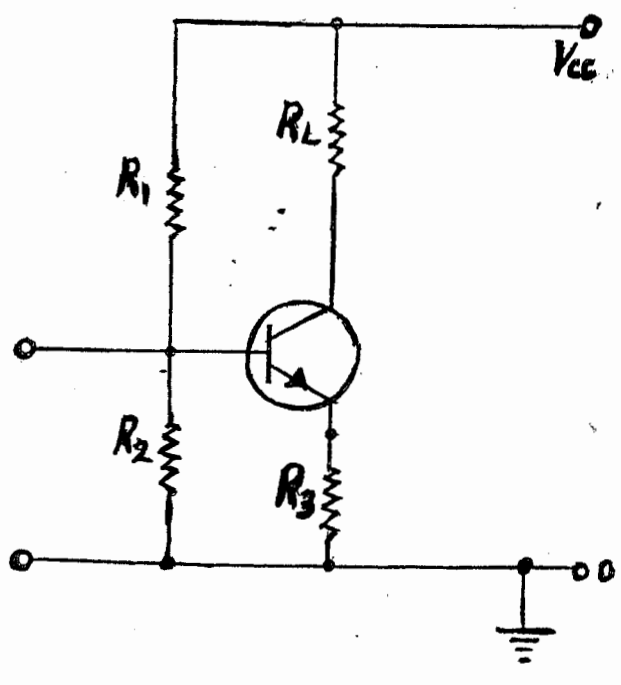


Figure 2.2

QUESTION 3

102

- (a) Discuss the principle of operation of a p-channel JFET, with reference to a schematic diagram of the JFET and its characteristics. (10 marks)
- (b) (i) Draw the circuit diagram of a common-source amplifier stage in which the dc bias is obtained by means of a source resistor, R_S . The amplifier utilises an n-channel JFET. Label the amplifier circuit. (3 marks)
- (ii) In what way is the dc bias influenced by R_S ? (3 marks)
- (c) An n-channel JFET has the data

Table 1. Data for an n-channel JFET

V_{DS} (V)	I_D (mA)	
	$V_{GS} = 0$ V	$V_{GS} = -2$ V
0	0	0
1	2	1
3	5.8	2.2
5	8.0	2.6
9	9.9	2.9
13	10.2	3.1
17	10.3	3.3

- (i) Plot the drain characteristics. (3 marks)
- (ii) Use the characteristics to determine the transconductance, g_m of the device at $V_{DS} = 12$ V and to calculate the drain resistance, r_d , for $V_{GS} = -2$ V. (6 marks)

QUESTION 4

- (a) Consider the diode equation given below

$$I_D = I_S \left\{ \exp\left(\frac{qV_D}{\eta k_B T}\right) - 1 \right\}, \text{ where the symbols have the usual meaning.}$$

For a forward-biased diode $\exp(qV_D/\eta k_B T) \gg 1$.

Present the values of the diode current and voltage given in Table 2 in the form of a graph that would enable you to calculate the values of the constant η and the reverse saturation current, I_S .

Table 2. Current and voltage data for a forward-biased p-n diode

Forward voltage, V_D (V)	0.10	0.15	0.20	0.25	0.30
Forward current, I_D (mA)	0.005	0.02	0.10	0.40	1.5

(13 marks)

- (b) The characteristics of the diode in the circuit shown in Fig. 4.1 are shown in Fig. 4.2.

- (i) With the aid of a d.c. loadline, find the current flowing in the circuit. The applied d.c. voltage, V_S is 0.8 V. (7 marks)
- (ii) Estimate the voltage across R_L . (2 marks)
- (iii) Find the value of R_L that will allow 5 μA to flow in the circuit. (3 marks)

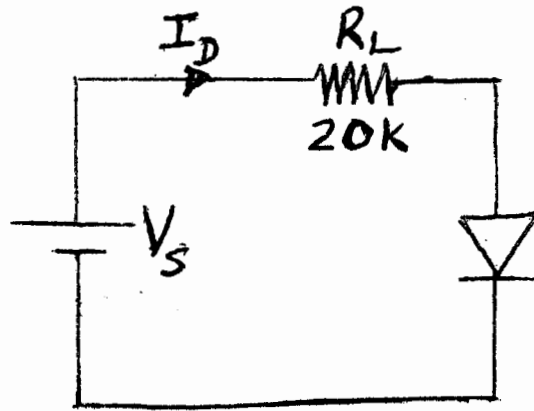


Figure 4.1

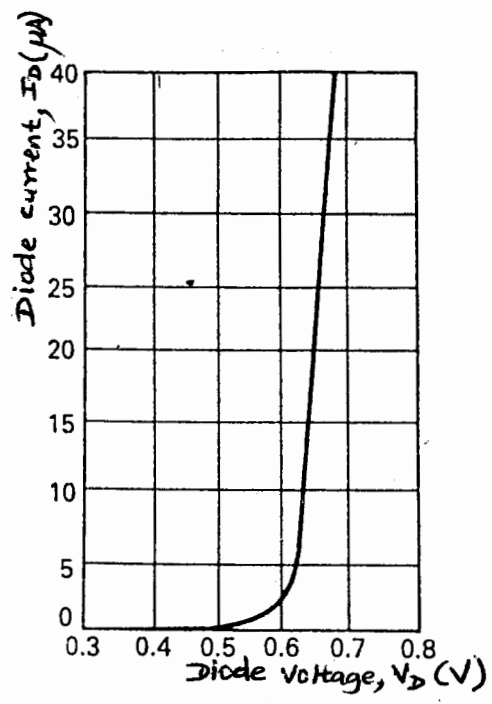


Figure 4.2

QUESTION 5

105

- (a) (i) Draw the circuit diagram of a full-wave rectifier which utilises a centre-tap transformer. (3 marks)
- (ii) Explain how the rectifier works, with the aid of the input and output waveforms. (7 marks)
- (b) Fig. 5.1 shows a half-wave rectifier with a reservoir capacitor of capacitance $10\ \mu\text{F}$. The peak value of the transformer secondary voltage is 30V (60 Hz) and the average current through the load is 10 mA .
 - (i) With reference to the transformer secondary voltage, show how the output voltage of the circuit varies with time. Label the waveforms. (3 marks)
 - (ii) Calculate the peak value of the ripple voltage. (4 marks)
 - (iii) Calculate the d.c. output voltage. (2 marks)
- (c) In the USA, the a.c. power-line supplies $115\text{ V}_{\text{rms}}$. This voltage is connected to the primary of a transformer with a turns ratio of $1/40$.
Calculate the peak-to-peak value of the transformer secondary voltage. (6 marks)

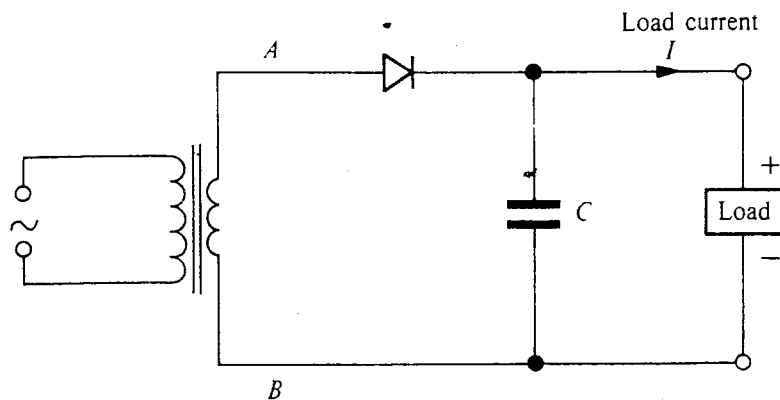


Figure 5.1