

UNIVERSITY OF SWAZILAND

106

FACULTY OF SCIENCE

DEPARTMENT OF PHYSICS

SUPPLEMENTARY EXAMINATION 2011

TITLE OF PAPER : ELECTRONICS I

COURSE NUMBER : P311

TIME ALLOWED : THREE HOURS

INSTRUCTIONS : ANSWER ANY FOUR OUT OF FIVE QUESTIONS

EACH QUESTION CARRIES 25 MARKS

MARKS FOR DIFFERENT SECTIONS ARE SHOWN IN THE RIGHT-HAND MARGIN.

THIS PAPER HAS 7 PAGES, INCLUDING THIS PAGE.

DO NOT OPEN THE PAPER UNTIL PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR.

QUESTION 1

107

(a) An ac power-line supplies $240V_{rms}$ to the primary of a transformer with a secondary:primary turns ratio of 30. Calculate the peak voltage across the secondary of the transformer. (4 marks)

(b) Figure 1.1 shows a Zener diode regulator. The maximum power rating of the Zener diode is 250 mW and the Zener voltage is 9.1 V.

Calculate the value of R_s required to ensure that the power dissipated in the Zener diode is to be less than 100 mW when the supply voltage, V is 12 V and the load resistance, R_L is 100Ω . (8 marks)

(c) Consider the half-wave rectifier shown in Figure 1.2.

(i) Calculate the average current through R_L . (3 marks)

(ii) Calculate the average voltage across R_L . (2 marks)

(iii) What would be the average voltage when $R_L = 100 \Omega$? (2 marks)

(iv) What would be the average voltage when the rectifier is used with a smoothing capacitor equal to $100 \mu F$? (6 marks)

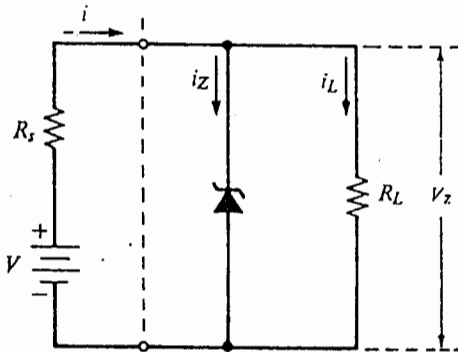


Figure 1.1

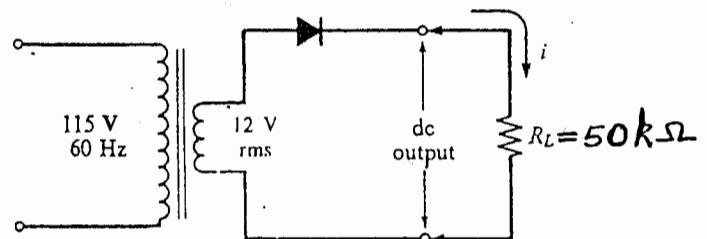


Figure 1.2

QUESTION 2

108

- (a) Describe the principle of operation of a pnp (bipolar junction) transistor connected in the forward-active mode. Use a schematic diagram for illustration. (10 marks)
- (b) Consider the common-emitter amplifier shown in Fig. 2.1. If $I_E = 2\text{ mA}$, $V_{CE} = 12\text{ V}$, $V_E = 5\text{ V}$ and $V_{BE} = 0.65\text{ V}$, calculate values of R_E , R_C and V_B . (8 marks)
- (c) The characteristics of a typical bipolar junction transistor (npn) are given in Fig. 2.2.
- (i) Draw the loadline for supply voltage $V_{CC} = 8\text{ V}$ and collector resistor $R_C = 500\Omega$. (4 marks)
- (ii) Choose an operating point on the characteristics and estimate the quiescent values of I_B , V_{CE} and I_C . Justify your choice of the operating point. (3 marks)

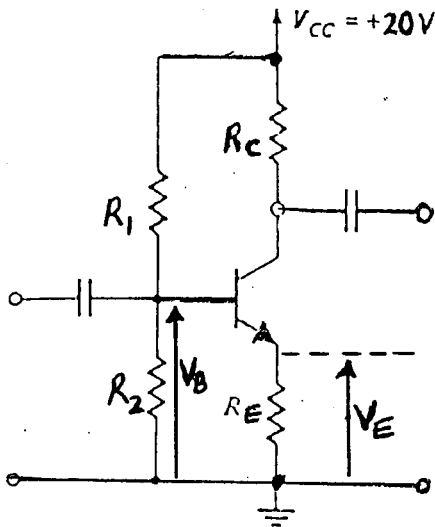


Fig. 2.1

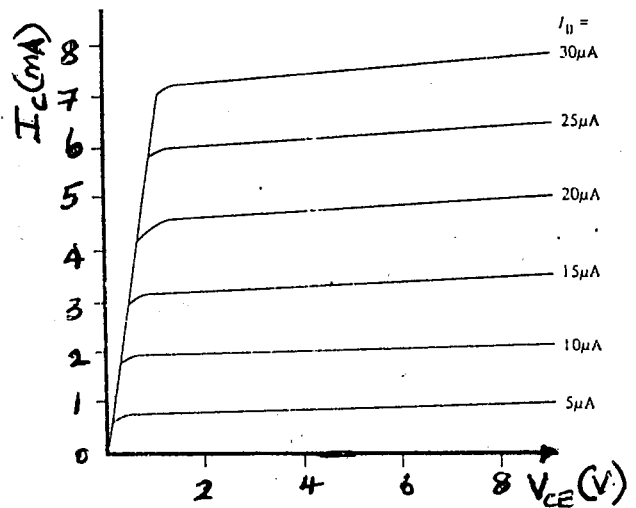


Fig. 2.2

QUESTION 3

109

- (a) With the aid of a diagram as well as the drain and mutual characteristics, explain how a p-channel JFET works. (8 marks)
- (b) Use appropriate diagrams to explain how you would manufacture a p-channel JFET from a p- or n-type material. (7 marks)
- (c) (i) Draw the small signal model of a JFET common source amplifier. (3 marks)
(ii) Show that the gain of this amplifier is

$$A_v = -g_m \left[\frac{1}{R_D} + \frac{1}{r_d} \right]^{-1} \quad (4 \text{ marks})$$

- (d) In a JFET source follower, the transistor used has a mutual conductance equal to 10 mS. The resistor connected between the source and common is 5kΩ. Calculate the voltage gain of the follower. (3 marks)

QUESTION 4

110

- (a) A $10\ \mu\text{F}$ capacitor is used to reduce the ripple voltage at the output of a half-wave rectifier. The amplitude of the voltage at the transformer secondary is $25\ \text{V}$ ($50\ \text{Hz}$) and on average the current through the load is $5\ \text{mA}$.
- (i) Calculate the peak-to-peak value of the ripple voltage (4 marks)
 - (ii) Calculate the average output voltage. (2 marks)
- (b) A voltage regulator circuit utilises a $4.1\ \text{V}$, $500\ \text{mW}$ Zener diode. The minimum current requirement of the diode is $10\ \text{mA}$. The supply voltage is $15\text{V} \pm 10\%$ and the constant current through the load is $20\ \text{mA}$.
- (i) Draw the circuit diagram of the voltage regulator circuit and label it; (2 marks)
 - (ii) Calculate the series resistance; (7 marks)
 - (iii) Calculate the power dissipated in the diode when the supply voltage is $18\ \text{V}$. (5 marks)
- (c) A half-wave rectifier circuit consists of a diode and a load resistor R_L . It operates on an a.c. mains supply of $240\ \text{V}_{\text{rms}}$ with a step-down transformer that has a turns ratio T of $1/3$. Calculate
- (i) the peak value of the secondary voltage and (3 marks)
 - (ii) the d.c. voltage across R_L . (2 marks)

QUESTION 5

///

- (a) (i) Explain how you would obtain the transfer and drain characteristics of an n-channel JFET. Use a suitable diagram to support your explanation. (3 marks)
 - (ii) Sketch and label typical transfer and drain characteristics. (4 marks)
 - (iii) Use the characteristics explain how the use of a JFET as a voltage controlled resistor and how you would determine the mutual conductance. (7 marks)
- (b) Consider a JFET connected in the common-source mode. If the gate-source voltage is kept constant and a change in the drain-source voltage of 4 V produces a corresponding change of 1 mA in the drain current, what would be the drain resistance, r_d of the FET. (5 marks)
- (c) Consider the JFET amplifier in Fig. 5.1. The transconductance, g_m of the transistor used is $20 \text{ m}\Omega^{-1}$.
- (i) What would be the values of I_D and V_D when V_{GS} is -1.5V ? (4 marks)
 - (ii) Find the voltage gain of the amplifier. (2 marks)


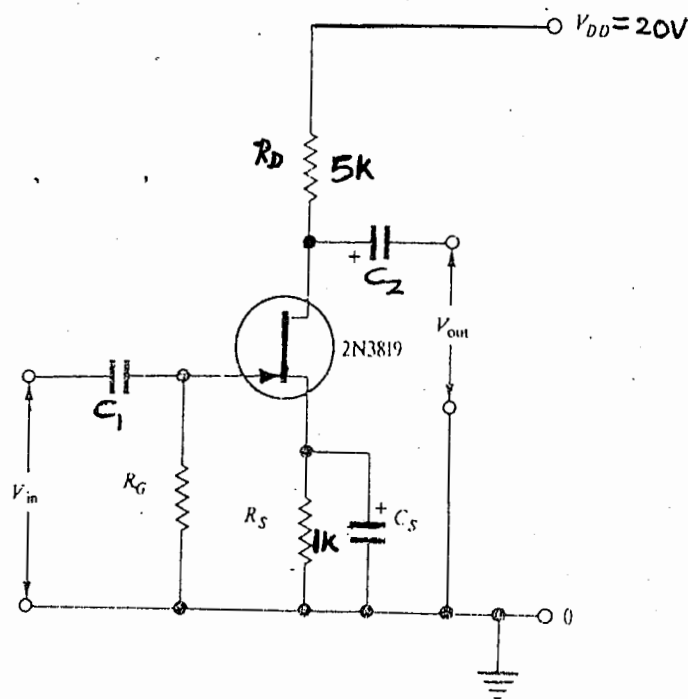


Fig. 5.1

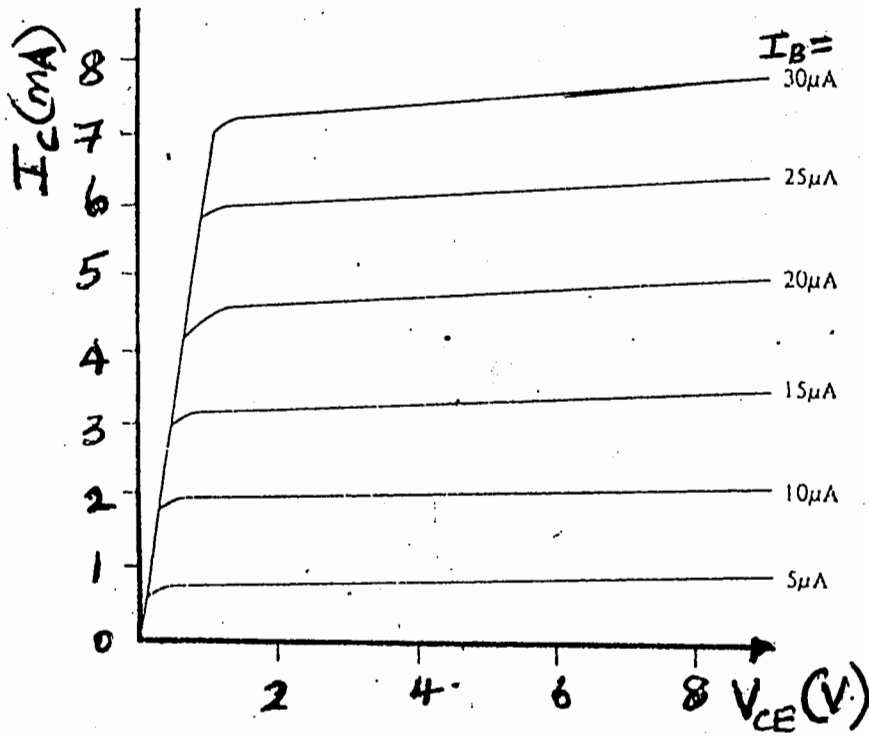USE THE GRAPH BELOW TO ANSWER QUESTION 2(c)



The graph should be handed in together with your answer book(s).