

UNIVERSITY OF SWAZILAND

155

FACULTY OF SCIENCE

DEPARTMENT OF PHYSICS

MAIN EXAMINATION

2010/2011

TITLE OF PAPER:

DIGITAL ELECTRONICS

COURSE NUMBER:

P411

TIME ALLOWED:

3 HOURS

INSTRUCTIONS:

ANSWER ANY FOUR OUT OF SIX QUESTIONS.

EACH QUESTION CARRIES 25 MARKS.

MARKS FOR DIFFERENT SECTIONS ARE SHOWN ENCLOSED IN SQUARE BRACKETS.

THIS PAPER HAS 6 PAGES INCLUDING THIS PAGE.

DO NOT OPEN THE PAPER UNTIL PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR.

- 156
- 1 (a) Find the equivalent Hex value for the BCD coded number  
10101110101<sub>BCD</sub>. [7]
- (b) What is bus fight of logic gates and how can it be avoided? [2]
- (c) Draw the circuit of a basic two-input TTL NAND gate with an open collector. [2]
- (d) Explain what a wired-AND is, using an example. [4]
- (e) Show that the output of three shorted open-collector NOR gates acts as a six input NOR gate. [4]
- (f) What is the logic function, F, of the circuit in Fig. 1 of the Appendix A? [6]
- 2 (a) Use any Karnaugh map as an example to distinguish between an implicant, a prime implicant and an essential prime implicant. [6]
- (b) Use the Quine-McCluskey method to find the output function, F, in the truth table given in Fig. 2 of the Appendix B; A,B,C and D are inputs. [13]
- (c) Explain what a comparator does and how the two-input XNOR gate acts as a simple one-bit magnitude comparator. [6]
- 3 (a) Implement the function  

$$f(x, y, z) = \sum m(1, 2, 6, 7),$$
using a 4 to 1 multiplexer. [6]
- (b) Implement the adder carry function  $C(X, Y, Z)$  using a multiplexer. [7]
- (c) Implement the adder sum function  $S(X, Y, Z)$  using a multiplexer. [8]
- (d) Design a Dual 4 to 1 Multiplexer-based full adder. [4]
- 4 (a) Explain what a parity bit is and make a truth table with three input bits, x, y and z producing one output odd parity bit P. [5]
- (b) Show how you can implement P in (a) with a three-variable XNOR gate. [5]
- (c) Make a truth table for a parity checker circuit which will have four inputs x, y, z and P with one output, E (error), which will be 1 whenever there is a parity error; E will be 1 whenever P is not the odd parity bit for the values of x, y and z. [5]
- (d) Show that the function, E, in (c) can be implemented as an XNOR of the four input variables. [7]

(e) Make a figure in which a parity generator and parity checker are represented with block diagrams to show how data with a parity bit is transmitted and received. Include LEDs that indicate the values of P and E. [3]

5 (a) Design a 2 to 4 binary decoder with inputs S1, S0 and EN, where EN is an enable input. The outputs should be labeled Q0, Q1, Q2 and Q3. [7]

(b) Make a truth table for a 3 to 8 decoder and design one using 2 to 4 decoders. [7]

(c) Draw the logic circuit of a master-slave SR flip flop using NAND gates. [5]

(d) Construct a modulus 10 asynchronous decade counter and use it to explain what truncated states are. Use logic symbols for the flip flops without including their logic circuits. [6]

6 (a) Distinguish between volatile and non-volatile memory. [2]

(b) (i) What is the memory capacity of a cell with 8 bit locations from 000H to FFFH in Hex? [5]

(ii) How many address lines are required for the memory cell in (i)? [3]

(c) Most microprocessor units have a group of single bit registers called condition code registers or flags. Name three flags; you do not have to explain how they function. [3]

(d) (i) Explain, using an example, how repeated subtraction may be used to accomplish division. [4]

(ii) Draw a flowchart which shows the sequence of steps to be taken in accomplishing division by repeated subtraction on a microprocessor. Use **Appendix C** to write the corresponding assembly language mnemonics along side the flowchart for each step. You do not need to include the operation codes in Hex. [8]

APPENDIX A – DIAGRAM

158

 


Figure 1

APPENDIX B – TRUTH TABLE

No.	A	B	C	D	F
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	1
12	1	1	0	0	0
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	1

Figure 2

## APPENDIX C – 8085 MNEMONICS

JUMP	CALL	RETURN	MOVE	
C3 JMP	CD CALL	C9 RET	40 MOV B,B	60 MOV H,B
C2 JNZ	C4 CNZ	C0 RNZ	41 MOV B,C	61 MOV H,C
CA JZ	CC CZ	C8 RZ	42 MOV B,D	62 MOV H,D
D2 JNC	D4 CNC	D0 RNC	43 MOV B,E	63 MOV H,E
DA JC	DC CC	D8 RC	44 MOV B,H	64 MOV H,H
E2 JPO	E4 CPO	E0 RPO	45 MOV B,L	65 MOV H,L
EA JPE	EC CPE	E8 RPE	46 MOV B,M	66 MOV H,M
F2 JP	F4 CP	F0 RP	47 MOV B,A	67 MOV H,H
FA JM	FC CM	F8 RM		
E9 PCHL			48 MOV C,B	68 MOV L,B
			49 MOV C,C	69 MOV L,C
MOVE	Acc	LOAD	4A MOV C,D	6A MOV L,D
IMMEDIATE	IMMEDIATE	IMMEDIATE	4B MOV C,E	6B MOV L,E
			4C MOV C,H	6C MOV L,H
06 MVI B	C6 ADI	01 LXI B,	4D MOV C,L	6D MOV L,L
0E MVI C,	CE ACI	11 LXI D,	4E MOV C,M	6E MOV L,M
16 MVI D,	D6 SUI	21 LXI H,	4F MOV C,A	6F MOV L,A
1E MVI E,	DE SBI	31 LXI SP,		
26 MVI H,	E6 ANI			
2E MVI L,	EE XRI		50 MOV D,B	70 MOV M,B
36 MVI M,	F6 ORI	DOUBLE ADD	51 MOV D,C	71 MOV M,C
3E MVI A,	FE CPI		52 MOV D,D	72 MOV M,D
			53 MOV D,E	73 MOV M,E
INCREMENT	DECREMENT		54 MOV D,H	74 MOV M,H
			55 MOV D,L	75 MOV M,L
04 INR B	05 DCR B	09 DAD B	56 MOV D,M	
0C INR C	0D DCR C	19 DAD D	57 MOV D,A	77 MOV M,A
14 INR D	15 DCR D	29 DAD H		
1C INR E	1D DCR E	39 DAD SP		
24 INR H	25 DCR H			
2C INR L	2D DCR L	LOAD/STORE	58 MOV E,B	78 MOV A,B
34 INR M	35 DCR M	0A LDAX B	59 MOV E,C	79 MOV A,C
3C INR A	3D DCR A	1A LDAX D	5A MOV E,D	7A MOV A,D
		2A LHLD	5B MOV E,E	7B MOV A,E
		3A LDA	5C MOV E,H	7C MOV A,H
			5D MOV E,L	7D MOV A,L
03 INX B	0B DCX B	02 STAX B	5E MOV E,M	7E MOV A,M
13 INX D	1B DCX D	12 STAX D	5F MOV E,A	7F MOV A,A
23 INX H	2B DCX H	22 SHLD		
33 INX SP	3B DCX SP	32 STA	ACCUMULATOR	
			80 ADD B	A0 ANA B
RESTART	ROTATE	SPECIALS	81 ADD C	A1 ANA C
			82 ADD D	A2 ANA D
C7 RST 0	07 RLC	EB XCHG	83 ADD E	A3 ANA E
CF RST 1	0F RRC	27 DAA	84 ADD H	A4 ANA H
D7 RST 2	17 RAL	2F CMA	85 ADD L	A5 ANA L
DF RST 3	1F RAR	37 STC	86 ADD M	A6 ANA M
E7 RST 4		3F CMC	87 ADD A	A7 ANA A

EF RST 5	CONTROL		88 ADC B	A8 XRA B
F7 RST 6		INPUT/OUTPUT	89 ADC C	A9 XRA C
FF RST 7	00 NOP	D3 OUT	8A ADC D	AA XRA D
	20 RIM	DB IN	8B ADC E	AB XRA E
	30 SIM		8C ADC H	AC XRA H
	76 HLT	STACK OPS	8D ADC L	AD XRA L
	F3 DI		8E ADC M	AE XRA M
	FB EI		8F ADC A	AF XRA A
	2B BMI	C5 PUSH B		
		D5 PUSH D	90 SUB B	B0 ORA B
		E5 PUSH H	91 SUB C	B1 ORA C
		F3 PUSH PSW	92 SUB D	B2 ORA D
			93 SUB E	B3 ORA E
		C1 POP B	94 SUB H	B4 ORA H
		D1 POP D	95 SUB L	B5 ORA L
		E1 POP H	96 SUB M	B6 ORA M
		F1 POP PSW	97 SUB A	B7 ORA A
		E3 XTHL	98 SBB B	B8 CMP B
		F9 SPHL	99 SBB C	B9 CMP C
			9A SBB D	BA CMP D
			9B SBB E	BB CMP E
			9C SBB H	BC CMP H
			9D SBB L	BD CMP L
			9E SBB M	BE CMP M
			9F SBB A	BF CMP A

END OF P411 EXAMINATION