

**UNIVERSITY OF SWAZILAND**

**FACULTY OF SCIENCE**

**DEPARTMENT OF PHYSICS**

**SUPPLEMENTARY EXAMINATION 2012**

**TITLE OF PAPER : ELECTRONICS I**

**COURSE NUMBER : P311**

**TIME ALLOWED : THREE HOURS**

**INSTRUCTIONS : ANSWER ANY FOUR OUT OF FIVE QUESTIONS**

**EACH QUESTION CARRIES 25 MARKS**

**MARKS FOR DIFFERENT SECTIONS ARE SHOWN IN THE RIGHT-HAND MARGIN.**

70218

115

**THIS PAPER HAS 7 PAGES, INCLUDING THIS PAGE.**

**DO NOT OPEN THE PAPER UNTIL PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR.**

### QUESTION 1

- (a) Consider an n-p-n transistor connected in the common-emitter configuration. Sketch a circuit that you would use to measure the characteristics of the transistor. (2 marks)
- (b) Sketch the output characteristics of an n-p-n transistor and show the active, saturation, and cutoff regions. (4 marks)
- (c) The element values in the circuit shown in Fig. 1 are  $R_1 = 150 \text{ k}\Omega$ ,  $R_2 = 37.5 \text{ k}\Omega$ ,  $R_C = 2 \text{ k}\Omega$  and  $R_E = 3 \text{ k}\Omega$ . The transistor has  $h_{FE} = 100$  and negligible reverse saturation current.  $V_{BE} = 0.7 \text{ V}$ .

Calculate  $I_C$  and  $V_{CE}$  when  $V_{CC} = 9 \text{ V}$ . (11 marks)

- (d) A C-E amplifier is based on an n-p-n silicon transistor with the following parameters:

$$h_{ie} = 5 \text{ k}\Omega, \quad h_{fe} = 250, \quad h_{oe} = 2.0 \times 10^{-4} \text{ Siemen and } h_{re} = 10^{-5}.$$

The collector resistor is  $R_C = 2 \text{ k}\Omega$ .

With the aid of a small signal model of the amplifier,

- (i) Derive the exact (rather than approximate) expression of the current gain,  $A_i$  of the amplifier (6 marks)
- (ii) Calculate the exact value of the current gain. (2 marks)

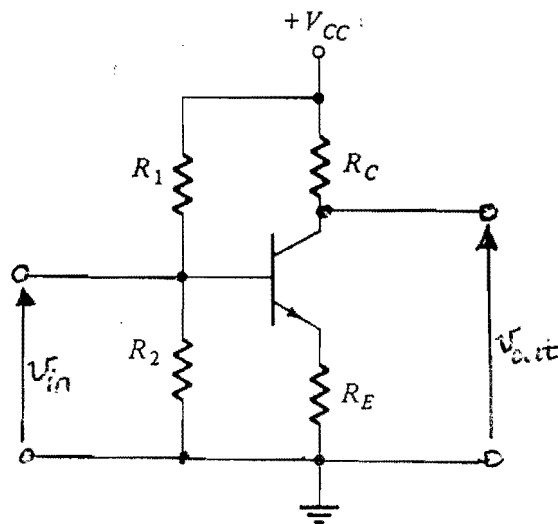


Fig. 1

## QUESTION 2

- (a) With reference to a junction field effect transistor, define the following terms:
- (i) *Mutual conductance* (2 marks)
  - (ii) *Drain resistance*. (2 marks)

- (b) Plot the mutual characteristic of a JFET with the aid of the equation below for  $I_{DSS} = 20 \text{ mA}$  and  $V_p = -2 \text{ V}$ . (5 marks)

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_p} \right)^2$$

- (c) Sketch the circuit of a self-biasing common-source amplifier which utilises an p-channel junction field effect transistor. (3 marks)
- (d) With the aid of a small signal model, derive an expression for the voltage gain of a common-source amplifier. (9 marks)
- (e) The drain characteristics shown on page 7 are based on the JFET amplifier illustrated in Fig. 2 below. The supply voltage  $V_{DD}$  is 30 V and  $I_D = 2.5 \text{ mA}$ . Use these drain characteristics to find  $R_D$ . (4 marks)

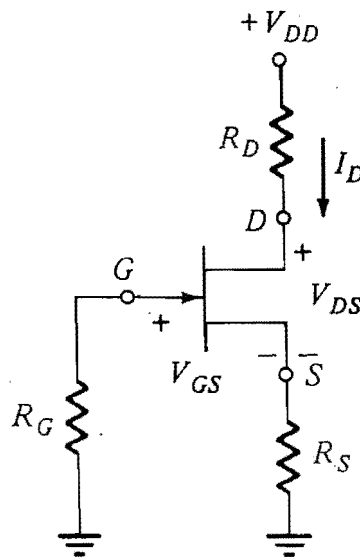


Fig. 2

### **QUESTION 3**

- (a) Define
- (i) *donor* impurities in semiconductors; (2 marks)
  - (ii) *acceptor* impurities in semiconductors. (2 marks)
- (b) Explain, with the aid of simple diagrams, how n-type silicon is produced. (6 marks)
- (c) Show (in two dimensions) the crystal structure of silicon containing a donor impurity atom. Explain, briefly, the effect of donor impurities on the conductivity of the material. (5 marks)
- (d) Sketch and comment on the energy-band diagrams representing
- (i) *n*-type silicon that is produced using phosphorous and show the donor energy level; (5 marks)
  - (ii) *p*-type silicon that is produced using boron and show the acceptor energy level. (5 marks)
- Label both diagrams.

**QUESTION 4**

- (a) Write the Shockley equation for a  $p-n$  diode and state the meaning of each symbol. (6 marks)
- (b) Plot the diode characteristics for germanium and silicon on the same graph and show the turn-on voltage for each of the semiconductors. (2 marks)
- (c) The current,  $I_D$  in the circuit shown in Fig. 3.1 and the diode voltage,  $V_D$  can be estimated, theoretically, with the aid of the diode characteristics in Fig. 3.2. Given that  $V_{AA} = 0.8\text{ V}$  and  $R = 10\ \Omega$ ,
- (i) Use the diode characteristics to find approximate values of the diode current and the diode voltage. (7 marks)
- (ii) If  $V_{AA}$  is increased from 0.8 V to 1 V, what will be the new value of  $R$  when the diode current is to remain at the value obtained in (i) above? (5 marks)
- (d) Consider a Zener diode with a Zener voltage of 5.2 V and a maximum power rating of 250mW. The diode is used in the simple regulator circuit illustrated in Fig. 3.3 to provide a maximum load current of 12 mA. The voltage supply varies from 9 V to 11 V.

Calculate the value of the series resistance,  $R_S$  required for this circuit. (5 marks)

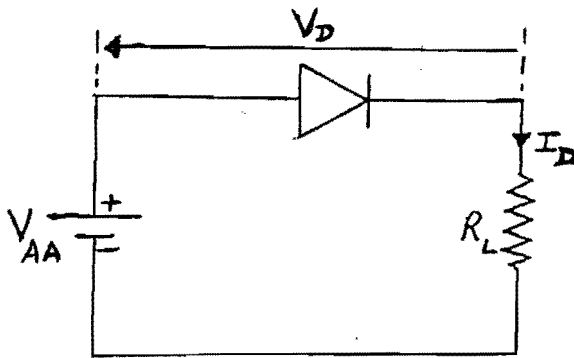


Fig. 3.1

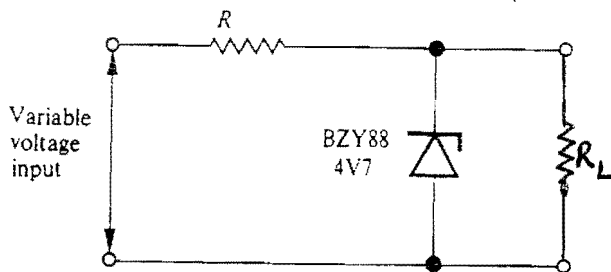


Fig. 3.3

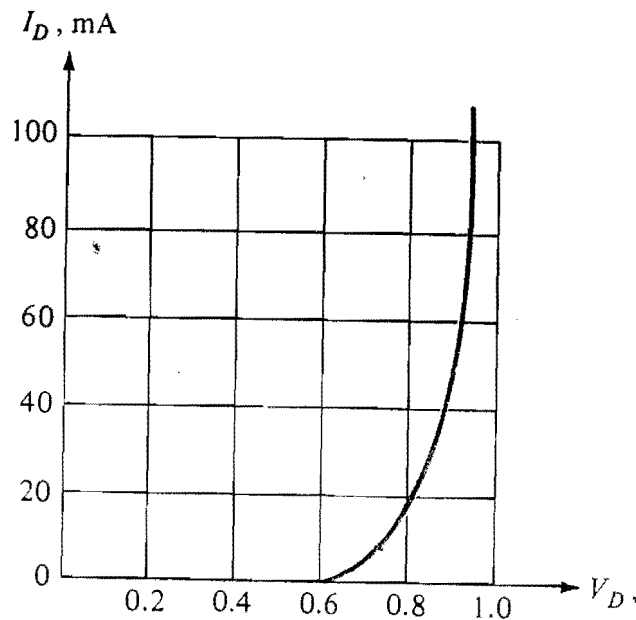


Fig. 3.2

### **QUESTION 5**

- (a) (i) What type of circuit is referred to as a source follower? (3 marks)  
(ii) Show that the output resistance of a source follower is given by

$$r_{out} = \frac{1}{g_m}$$

where  $g_m$  represents the transconductance of the JFET used. (7 marks)

- (b) The equations below provide information about the relationship between the currents and voltages associated with a difference amplifier.

$$g_m v_{in}(1) = i_{d2} g_m R_s + i_{d1} (1 + g_m R_s)$$

$$g_m v_{in}(2) = i_{d1} g_m R_s + i_{d2} (1 + g_m R_s)$$

where  $g_m$  is the transconductance;

$v_{in}(1)$  and  $v_{in}(2)$  are the input voltages to transistors  $T_1$  and  $T_2$  respectively;

$i_{d1}$  and  $i_{d2}$  are the drain currents associated with transistors  $T_1$  and  $T_2$  respectively;

$R_s$  is the source resistance.

- (i) Draw the circuit diagram of a difference amplifier and label it; (4 marks)  
(ii) Show that  $i_{d1} = -i_{d2}$ . Assume that  $R_s$  is large. (8 marks)  
(iii) Show that the output voltages are equal in magnitude but out of phase by  $180^\circ$ . (3 marks)

STUDENT NUMBER:.....

**PLEASE SUBMIT THE GRAPH BELOW TOGETHER WITH YOUR ANSWER SHEETS**

