

UNIVERSITY OF SWAZILAND

FACULTY OF SCIENCE

122

DEPARTMENT OF PHYSICS

MAIN EXAMINATION : 2011/2012

TITLE OF PAPER : ELECTRONICS II

COURSE NUMBER : P312

TIME ALLOWED : THREE HOURS

INSTRUCTIONS : ANSWER ANY FOUR OUT OF FIVE QUESTIONS

EACH QUESTION CARRIES 25 MARKS

MARKS FOR DIFFERENT SECTIONS ARE SHOWN IN THE RIGHT-HAND MARGIN.

THIS PAPER HAS 6 PAGES, INCLUDING THIS PAGE.

DO NOT OPEN THE PAPER UNTIL PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR.

QUESTION 1

- (a) Fig. 1.1 shows a bandpass filter.
- (i) Derive an expression for the magnitude of the transfer function of this filter. (5 marks)
 - (ii) Derive an expression for the resonant frequency, f_0 in terms of the inductance and capacitance. (4 marks)
 - (iii) Calculate the resonant frequency. (2 marks)
 - (iv) Calculate the Q-factor. (2 marks)
 - (v) Calculate the cut-off frequencies, f_1 and f_2 . (6 marks)
 - (vi) Calculate the bandwidth of the filter. (1 mark)
- (b) Calculate the phase difference between v_{in} and v_{out} for the high-pass filter shown in Fig. 1.2, when v_{in} has a frequency of 10 kHz. (5 marks)

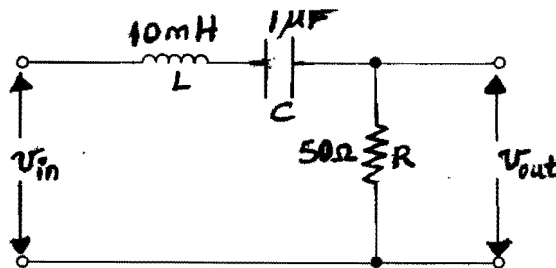


Fig. 1.1

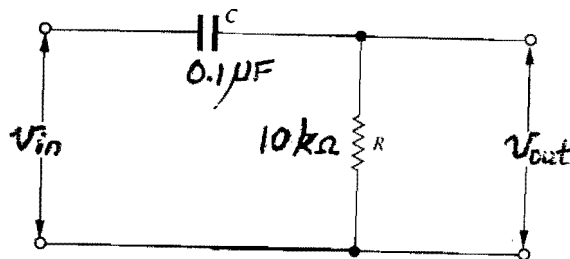


Fig. 1.2

QUESTION 2

- (a) (i) Draw the circuit diagram of an astable multivibrator which utilises two bipolar junction transistors, T_1 and T_2 and label it. (3 marks)
- (ii) Explain how this multivibrator works. Assume that when the d.c. power supply is turned ON, current rises faster in T_1 in comparison with T_2 . (4 marks)
- (iii) With the aid of a suitable table, write down the voltages at the base and collector of each of the two transistors. Sketch the waveforms observed at these points and label them. (12 marks)
- (b) Fig. 2.1 shows the circuit diagram of a phase-shift oscillator.
- (i) Write an expression for the frequency of oscillation of this oscillator. (2 marks)
- (ii) Explain why the open-loop gain of the amplifier used in the phase shift oscillator must be greater than or equal to 29. (4 marks)

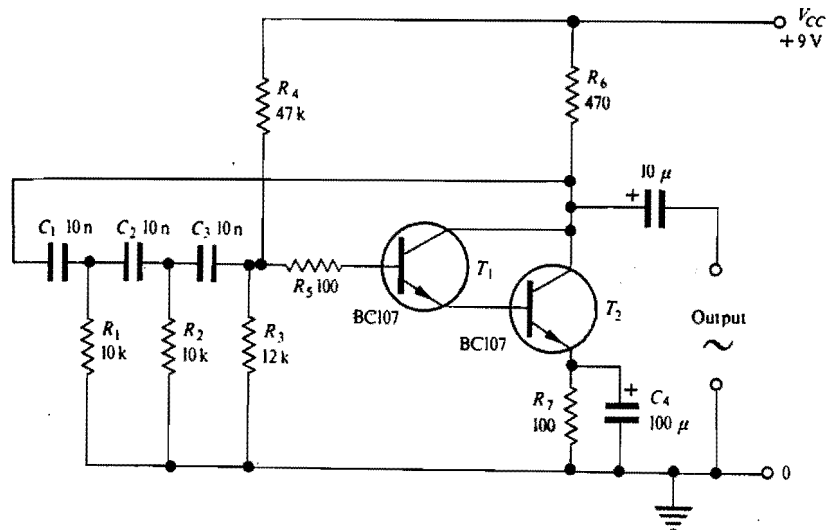


Fig. 2.1

QUESTION 3

- (a) What is meant by the following terms:
- (i) Barkhausen criterion? (3 marks)
 - (ii) Degenerative feedback? (3 marks)
- (b) Mention three advantages of applying negative feedback to an amplifier. (3 marks)
- (c) Consider a voltage amplifier with an open-loop gain of magnitude A . With the aid of a schematic diagram, derive an expression for the overall voltage gain of the amplifier when a fraction B of its output voltage, that is 180° out of phase with the input, is fed back to the input. (5 marks)
- (d) An amplifier has an open-loop gain of -300 . Negative feedback is applied to the amplifier with a feedback factor of 0.4 .
- (i) Calculate the loop gain. (2 marks)
 - (ii) Calculate the voltage gain when negative feedback is applied (to three decimal places). (2 marks)
 - (iii) Calculate the percentage increase in gain with feedback when the open-loop gain of the amplifier increases by 10% as a result of replacing a faulty transistor. (7 marks)

QUESTION 4

(a) Fig. 4.1 shows an operational integrator.

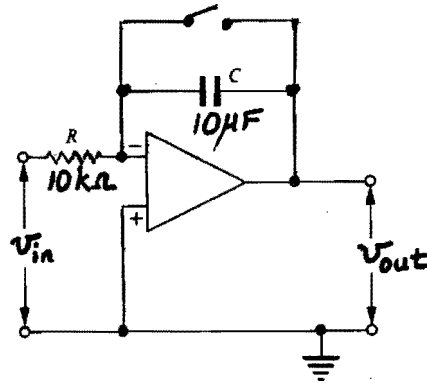


Fig. 4.1

- (i) State the relationship between v_{in} and v_{out} for an operational integrator. (1 mark)
- (ii) Determine an expression for v_{out} as a function of time when $v_{in} = 15 \text{ mV}$. Sketch graphs of v_{in} and v_{out} against time, on the same axes. Label the graphs. (5 marks)
- (iii) If v_{in} is a sinusoidal waveform with a frequency of 200 Hz and a peak value of 5 V, determine an expression for v_{out} in terms of time. Sketch graphs of v_{in} and v_{out} against time, on the same axes, and label them. (9 marks)

(b) Use operational amplifiers and other appropriate components to design a circuit which corresponds to the following (ideal) relationship between the input and output voltage, v_1 and v_0 , respectively:

$$v_0 = -(v_1 - 4 \times 10^{-3} \int v_1 dt) \quad (10 \text{ marks})$$

QUESTION 5

- (a) (i) Calculate v_{out} as a function of time for the circuit shown in Fig. 5.1, given that $v_{in} = A\cos\omega t$, $\omega = 200 \text{ rad.s}^{-1}$ and $A = 0.2 \text{ V}$. (4 marks)
- (ii) Sketch graphs of v_{in} and v_{out} as a function of time, on the same axes, and label them. (4 marks)
- (b) Use appropriate circuit diagrams and equations to explain how you would measure the input resistance of a device, such as a voltage amplifier. (5 marks)
- (c) Given the low-pass filter shown in Fig. 5.2,
- (i) Calculate the cut-off frequency of the filter. (2 marks)
- (ii) Find the magnitude of v_{out} when v_{in} has a frequency of 4 kHz. (3 marks)
- (d) Fig. 5.3 shows a circuit consisting of a voltage source. The source has an internal resistance, R_s , and generates a voltage V_s . It is connected to an emitter follower which acts as an impedance buffer. The output of the follower is, in turn, connected to a sink with an input resistance, R_i .

With the aid of a detailed circuit diagram of the emitter follower, and mathematical analysis, derive an expression to show the relationship between V_s and V_i . (7 marks)

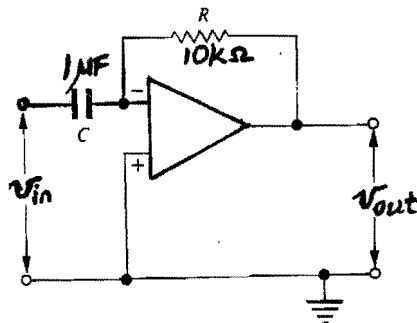


Fig. 5.1

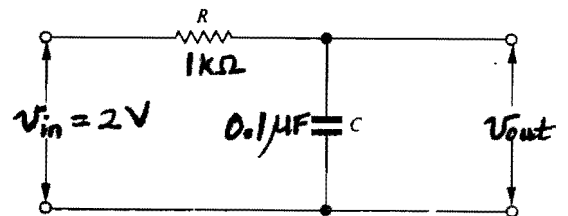


Fig. 5.2

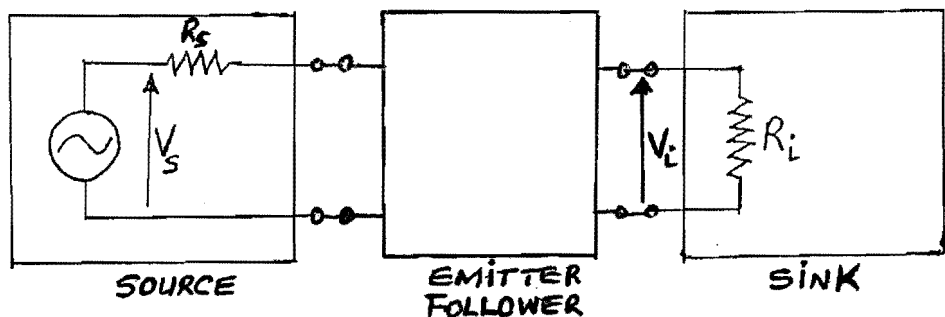


Fig. 5.3